

# **Blocker Tolerant Software Defined Receivers**

---

**Hooman Darabi**

**7/25/13**


# Receiver Noise and Linearity

- Receiver NF sets the sensitivity, range:

$$\text{Sensitivity} = -174 + \text{NF} + 10\text{Log}(\text{BW}) + \text{SNR}$$



$10\text{Log}(KT)$ , dBm/Hz

Set by the standard

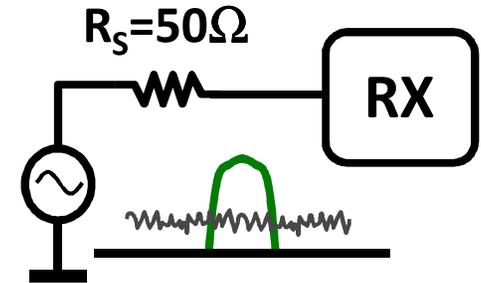


Blockers: In/Out-Band

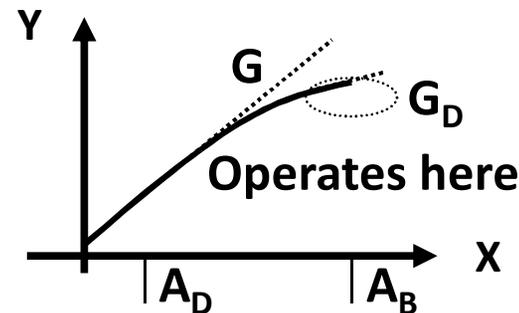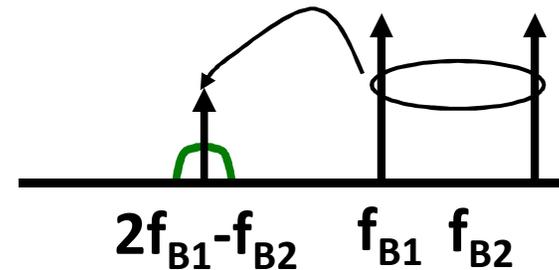- Small signal linearity:
  - $IIP_2$ ,  $IIP_3$
- Large signal linearity:
  - Gain compression
- Reciprocal mixing
- Harmonic mixing




# Reciprocal Mixing

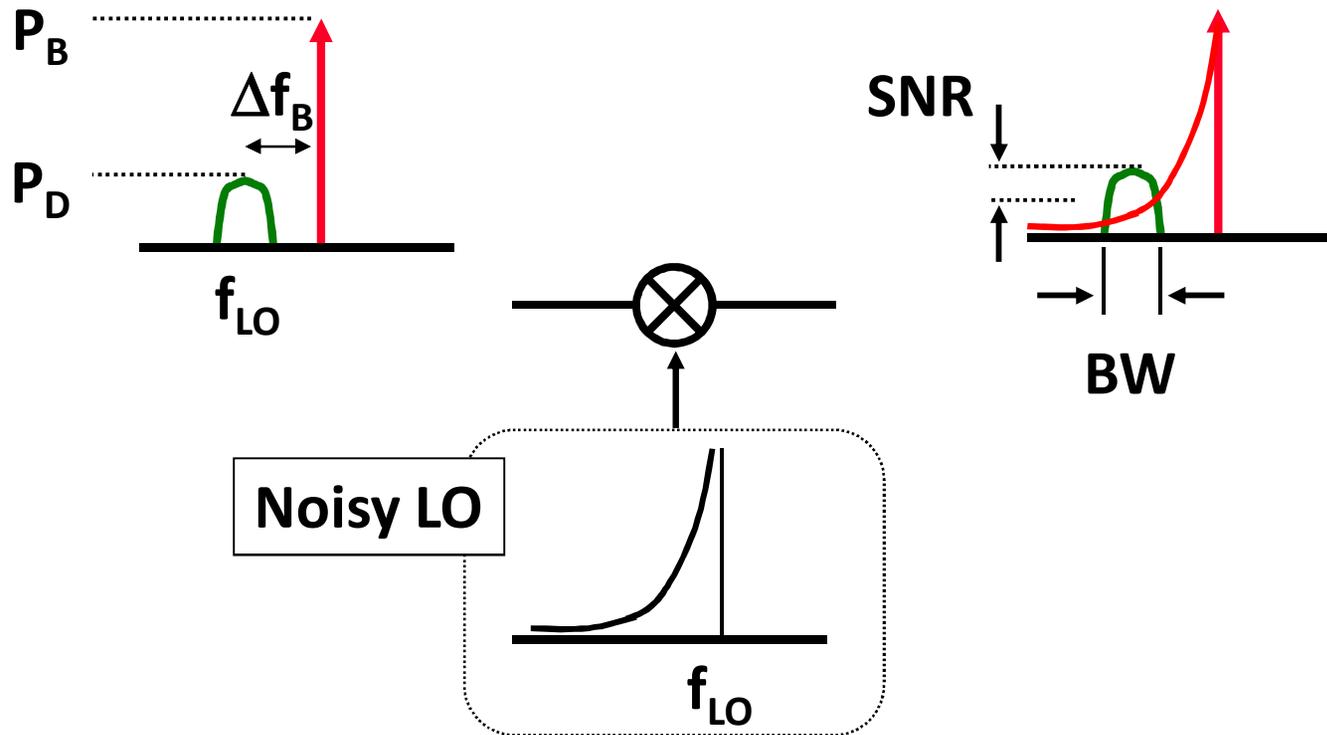


- $P_B + PN(\Delta_B) + 10 \times \text{LOG}(BW) = P_D - SNR$
- $BNF = 174 + PB + PN$
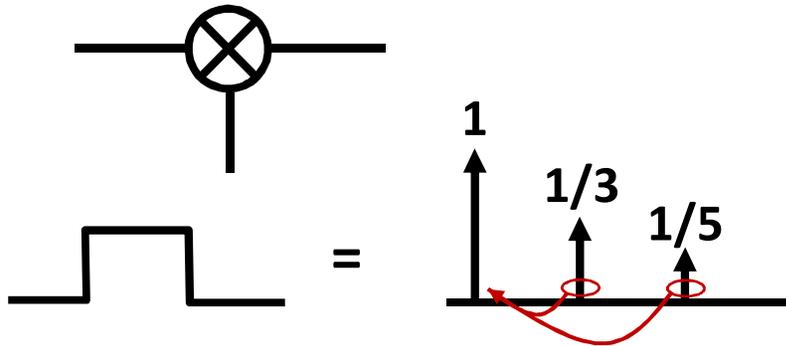
# Harmonic Rejection & Aliasing in Mixers




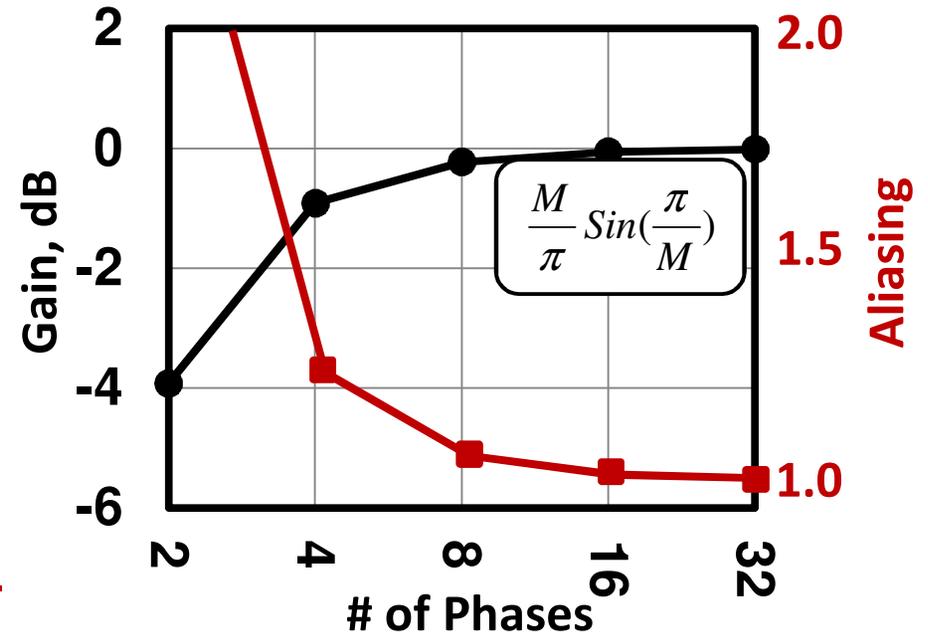Aliasing =  $1 + 1/3^2 + 1/5^2 + \dots = \pi^2/2$





- Square-wave LO harmonically rich
- More phases alleviates the issue
- More energy in main, less in higher harmonics

# 3/4G Full-Duplex Problem

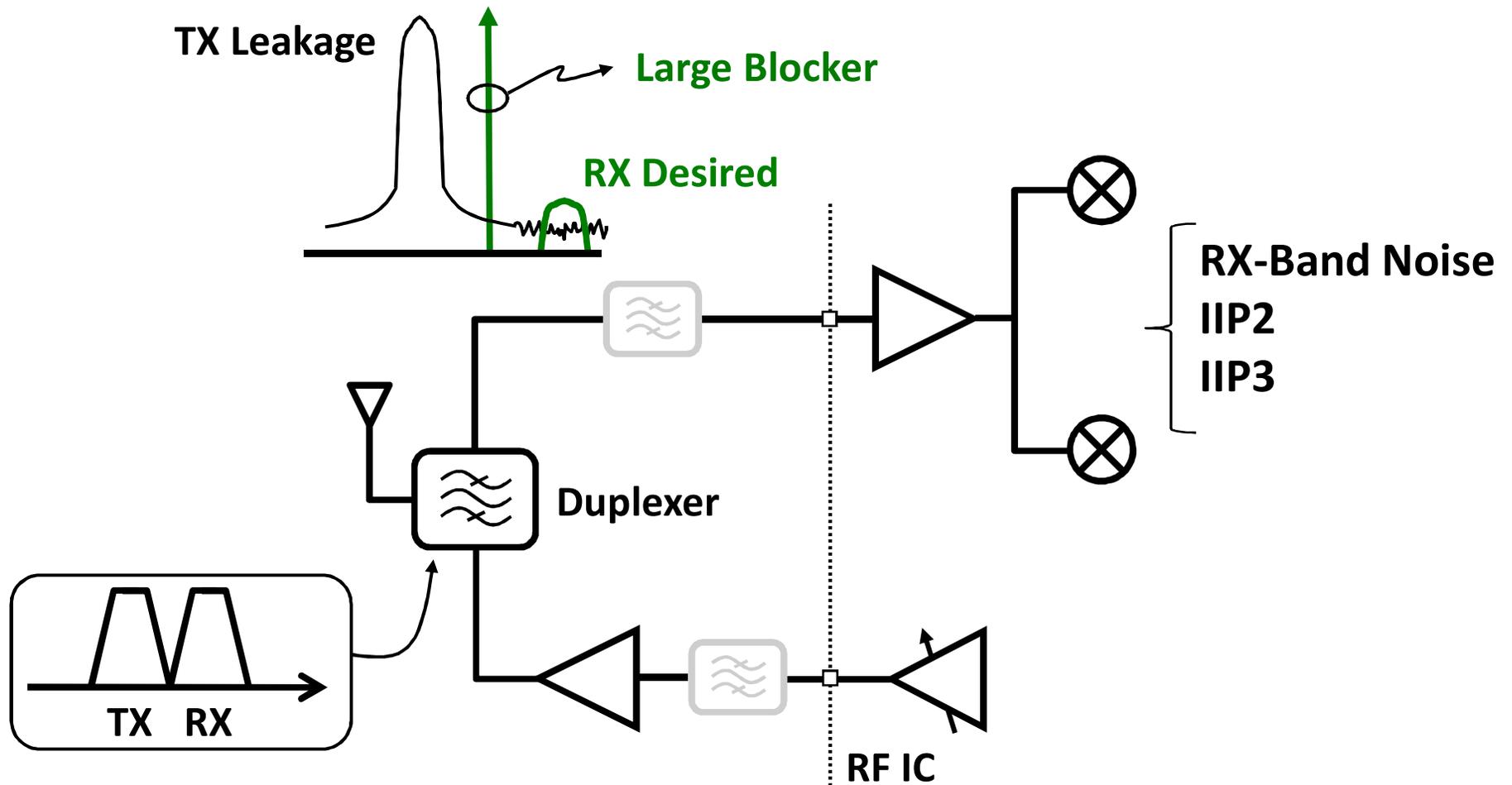

- Duplexer is a dual-band filter
- Similar issue due to co-existence


# Ideal Receiver

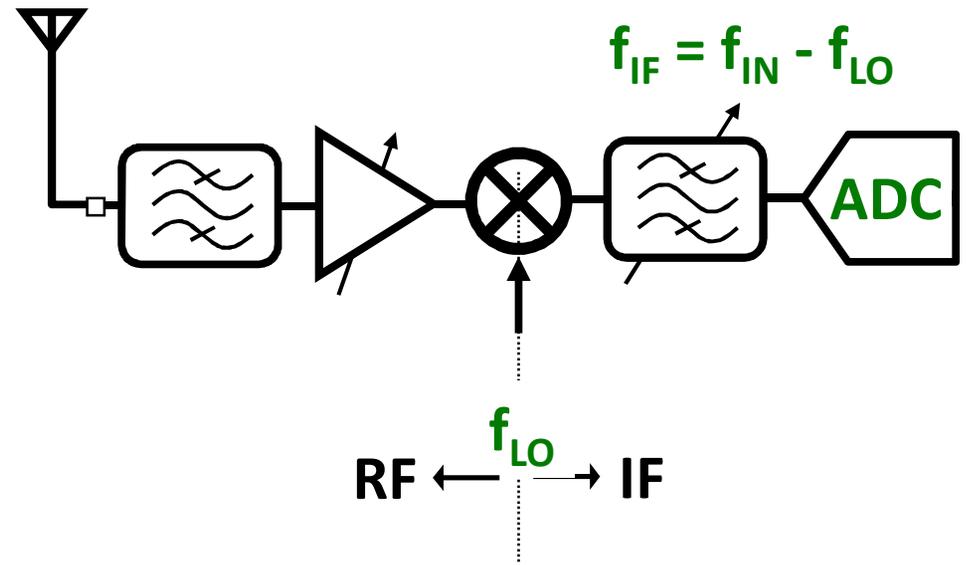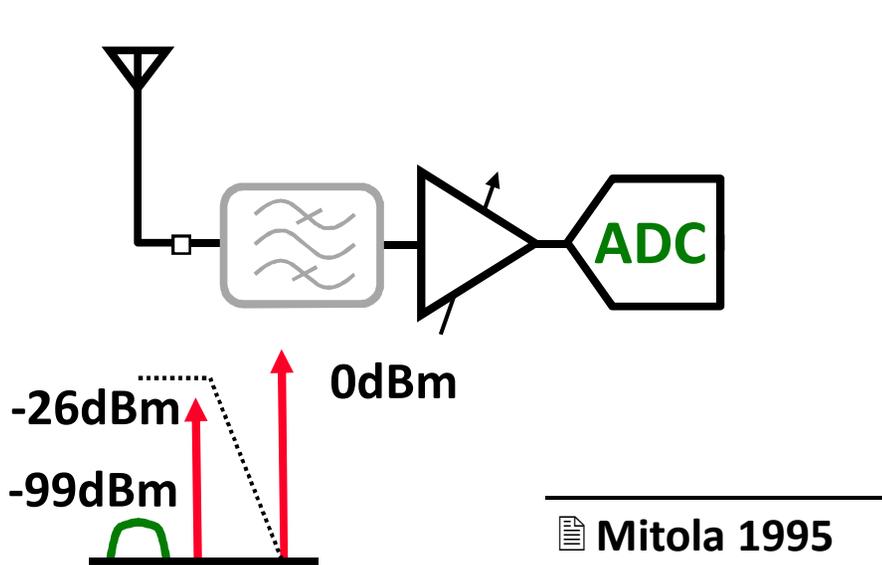


- Filter only rejects out-of-band blockers
- In-band blockers require a high-resolution ADC
- Power hungry

- Invented by Armstrong in 1918
- *Down-conversion* relaxes IF signal processing
- Lower power

# Ideal Receiver – Challenges

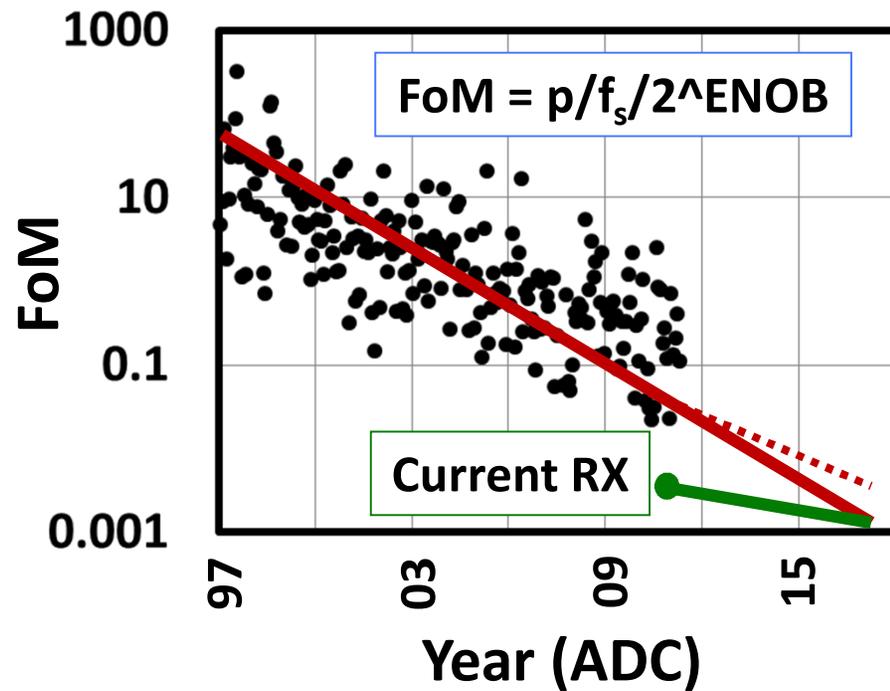


📄 Murmann

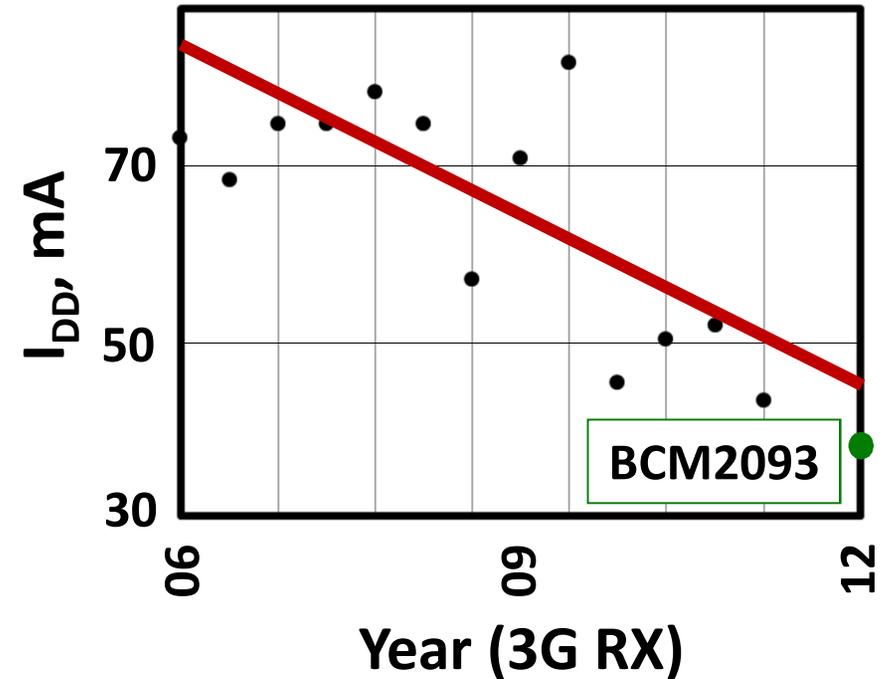

📄 Mikhemar


- Scalable
- Broad-band: Low-noise, Blocker tolerant
- Low-power

# Narrow-Band Filtering Concerns

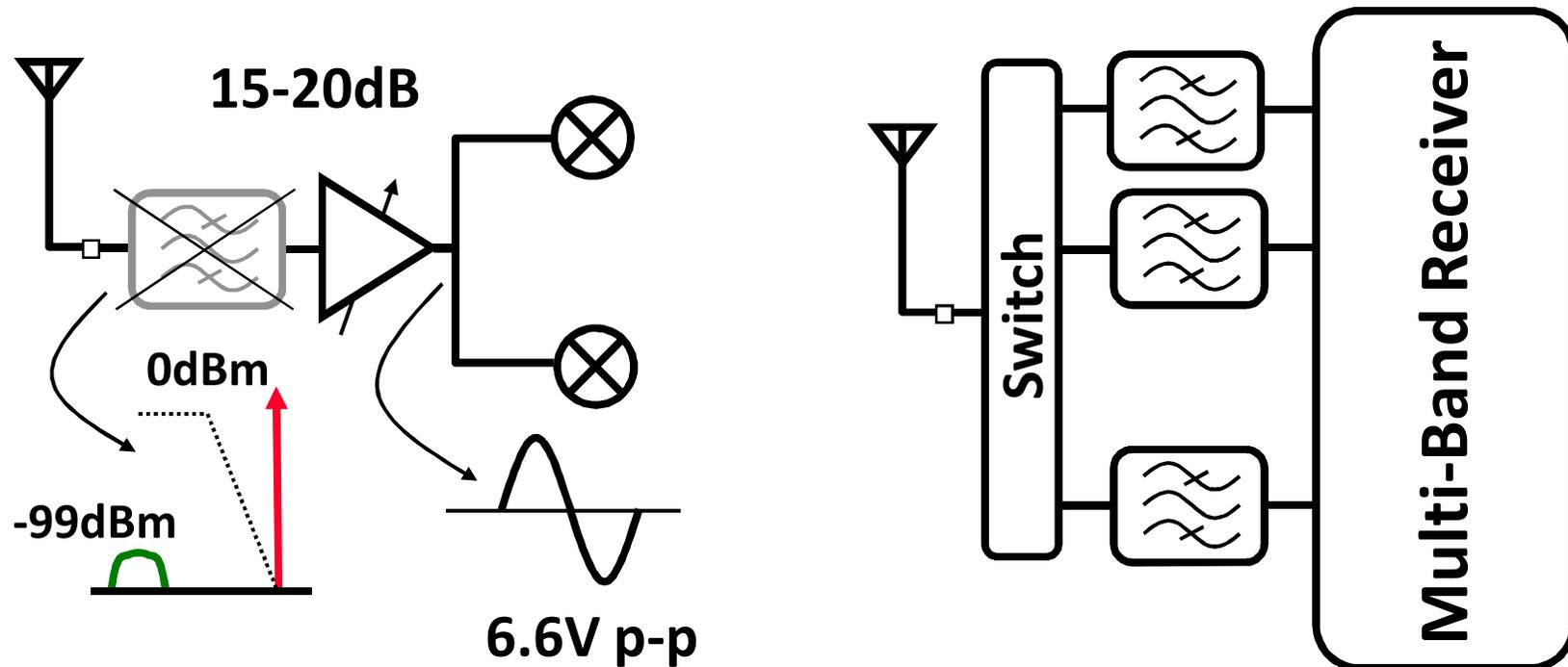

- Large blockers compress the receiver
- External filtering is narrow-band and costly




# N-Path Filtering Concept

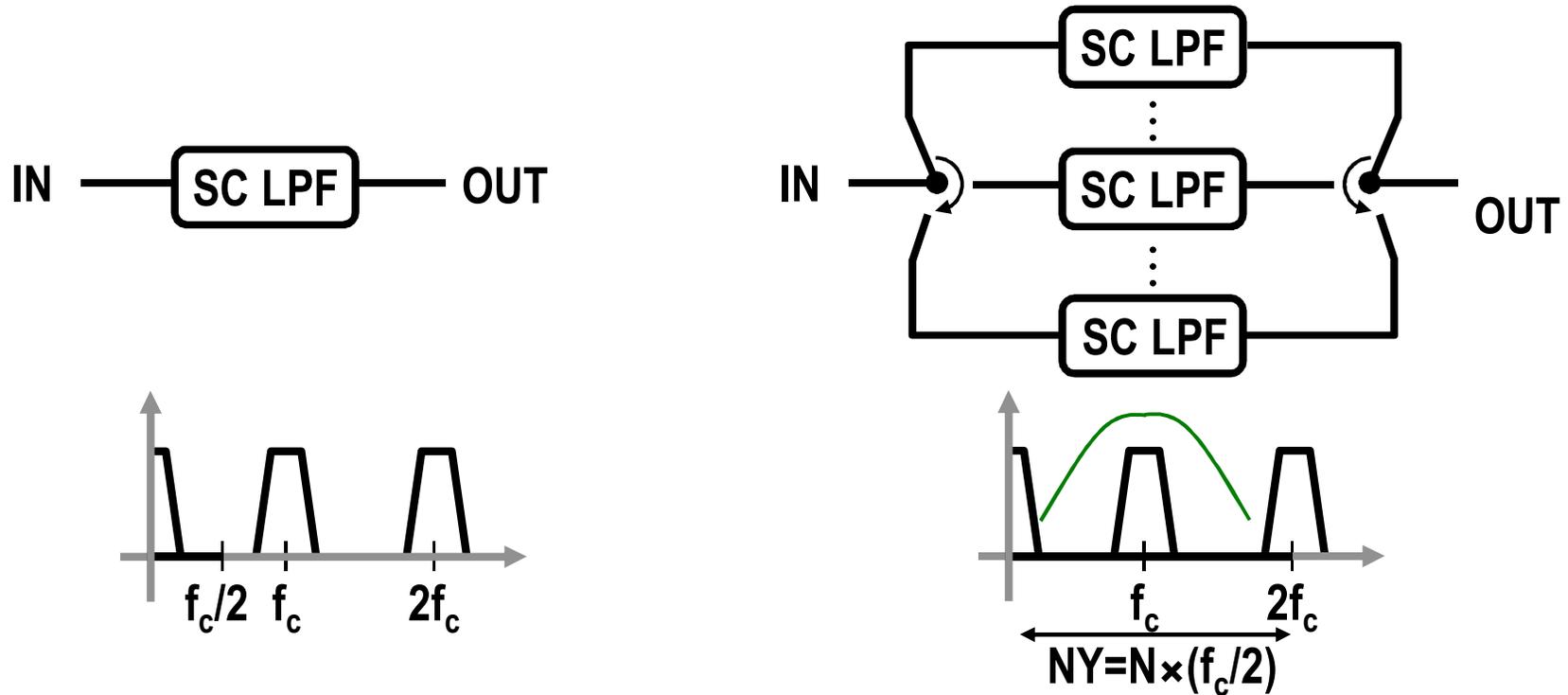

- Very high-Q passives needed
- *N-path filtering* extends Nyquist rate<sup>1</sup>

<sup>1</sup> L. Franks, Bell Syst. Tech. J., 1960


# Passive Mixers as High-Q Filters

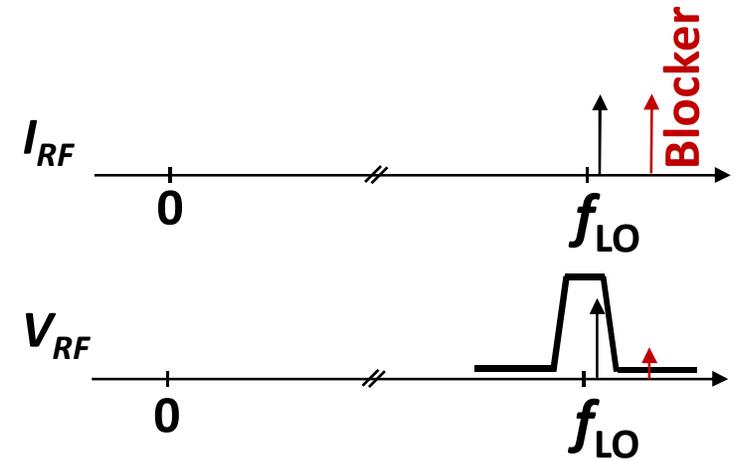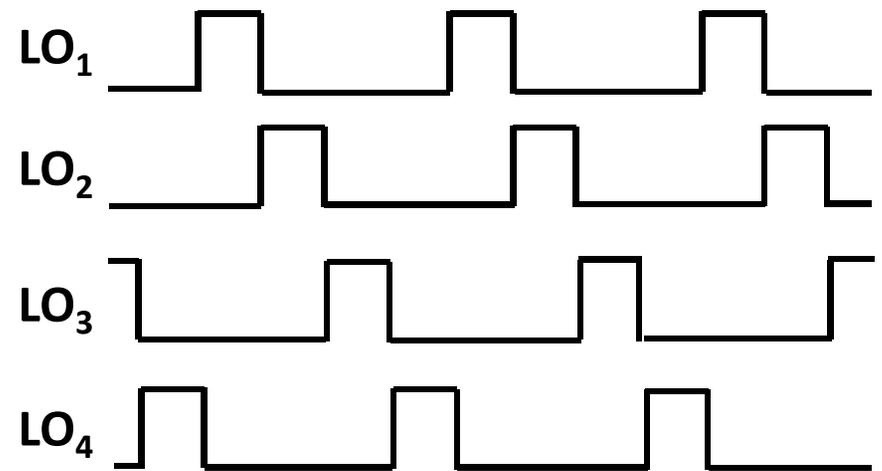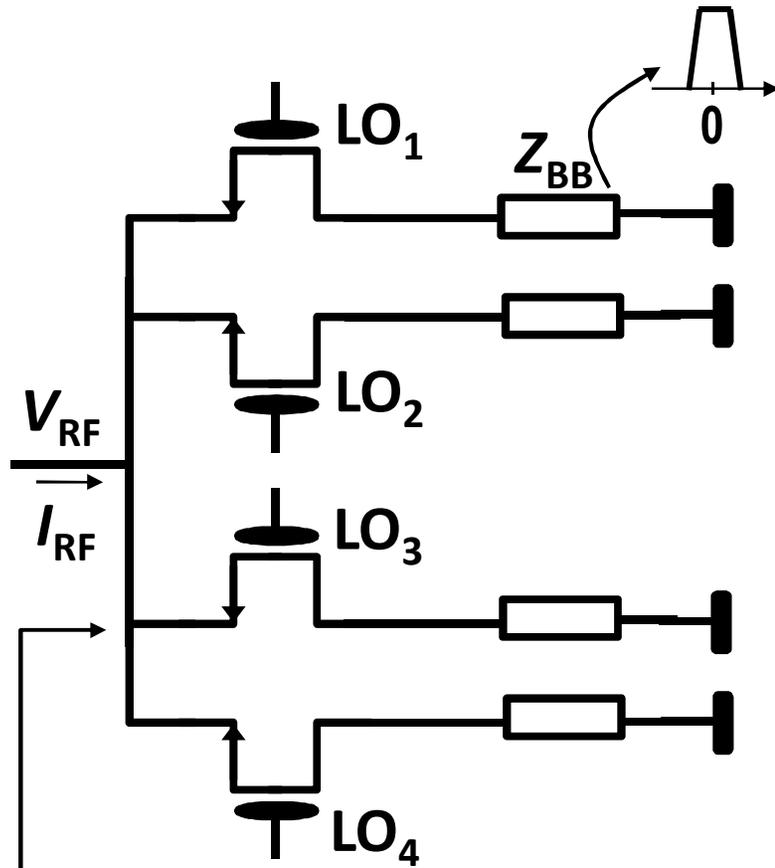

**High-Q BPF from low-Q LPF**


$$Z_{in}(s) \approx R_{SW} + \frac{2}{\pi^2} \{ Z_{BB}(s - j\omega_{LO}) + Z_{BB}(s + j\omega_{LO}) \}$$

# Current-Mode Receivers

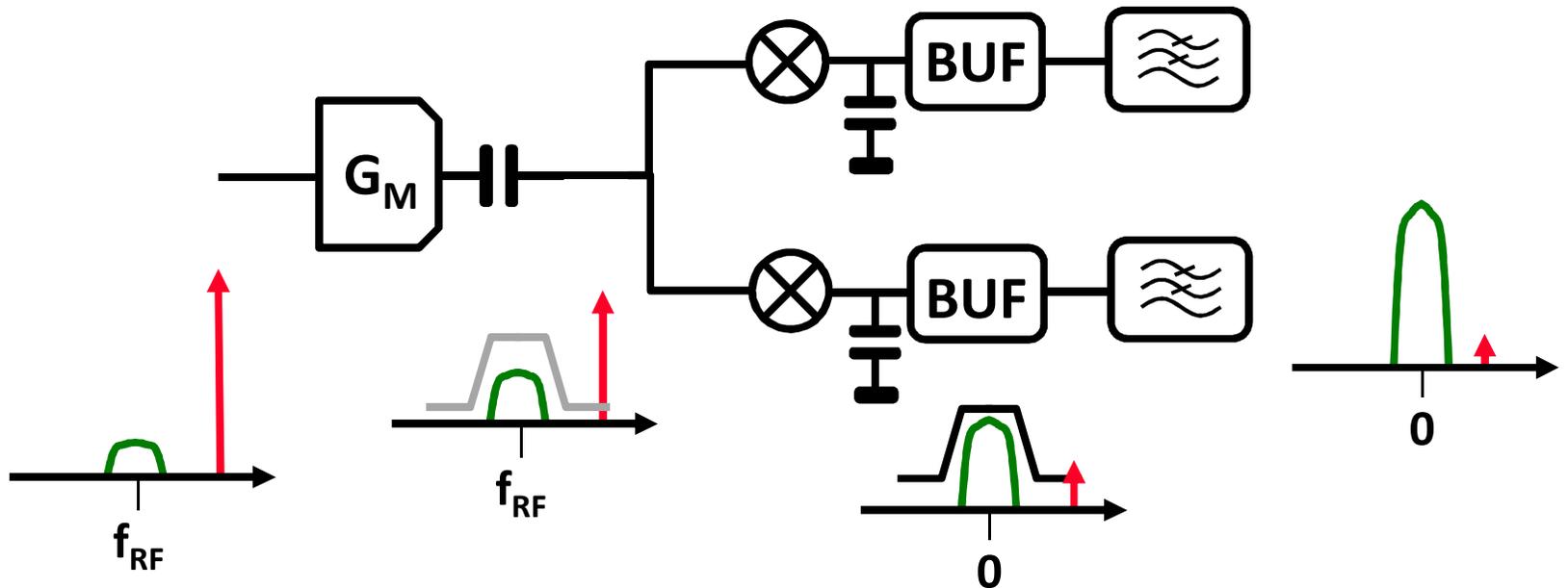


- **Passive mixers to achieve high-Q filtering**
- **Current mode LNA: LNTA**
- **Enhance the blocker tolerance**

# Front-End Matching Concerns

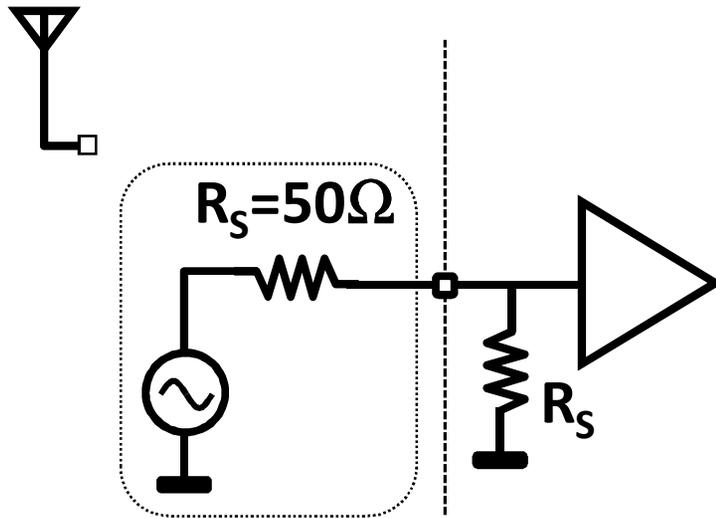



NF > 3dB

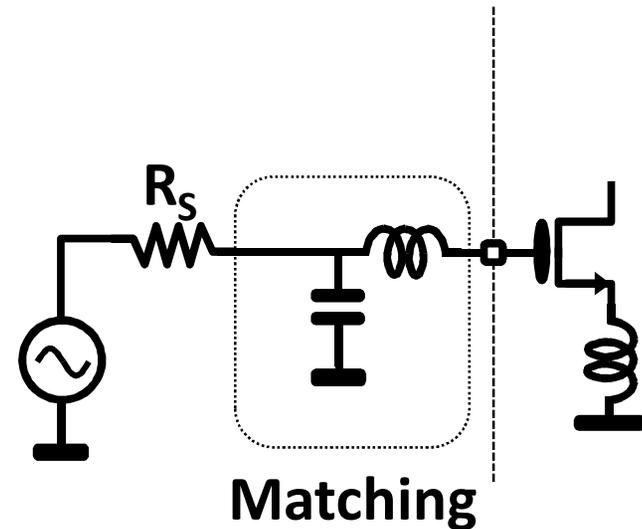- Wide-band matching
- Good linearity
- NF suffers




- Narrow-band matching
- Good NF
- Modest linearity

# Mixer-First Receivers

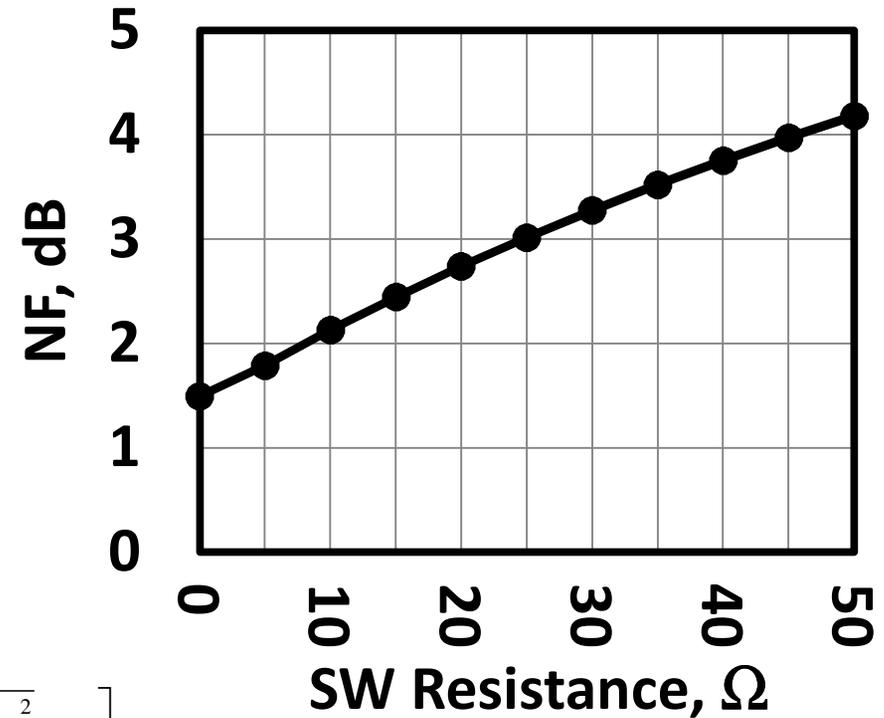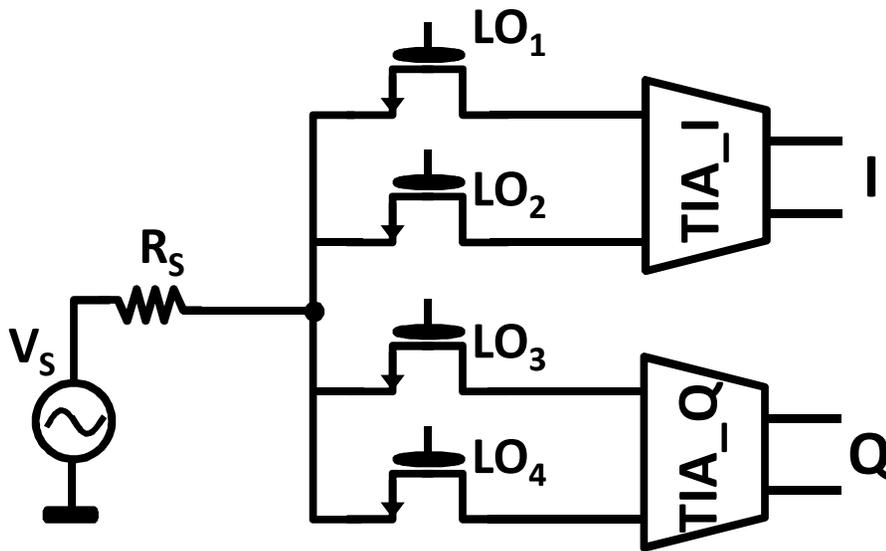

- For M phases: 
$$F = \left[ 1 + \frac{r_{DS}(ON)}{R_S} + \frac{\overline{v_{bb}^2}}{M(4KTR_S)} \right] \times N_{Aliasing}$$
- $N = 1 / (\text{sinc}(\pi/M))^2 > 1$
- **NF > 3dB in practice at GHz frequencies**


# Noise Cancelling Concept

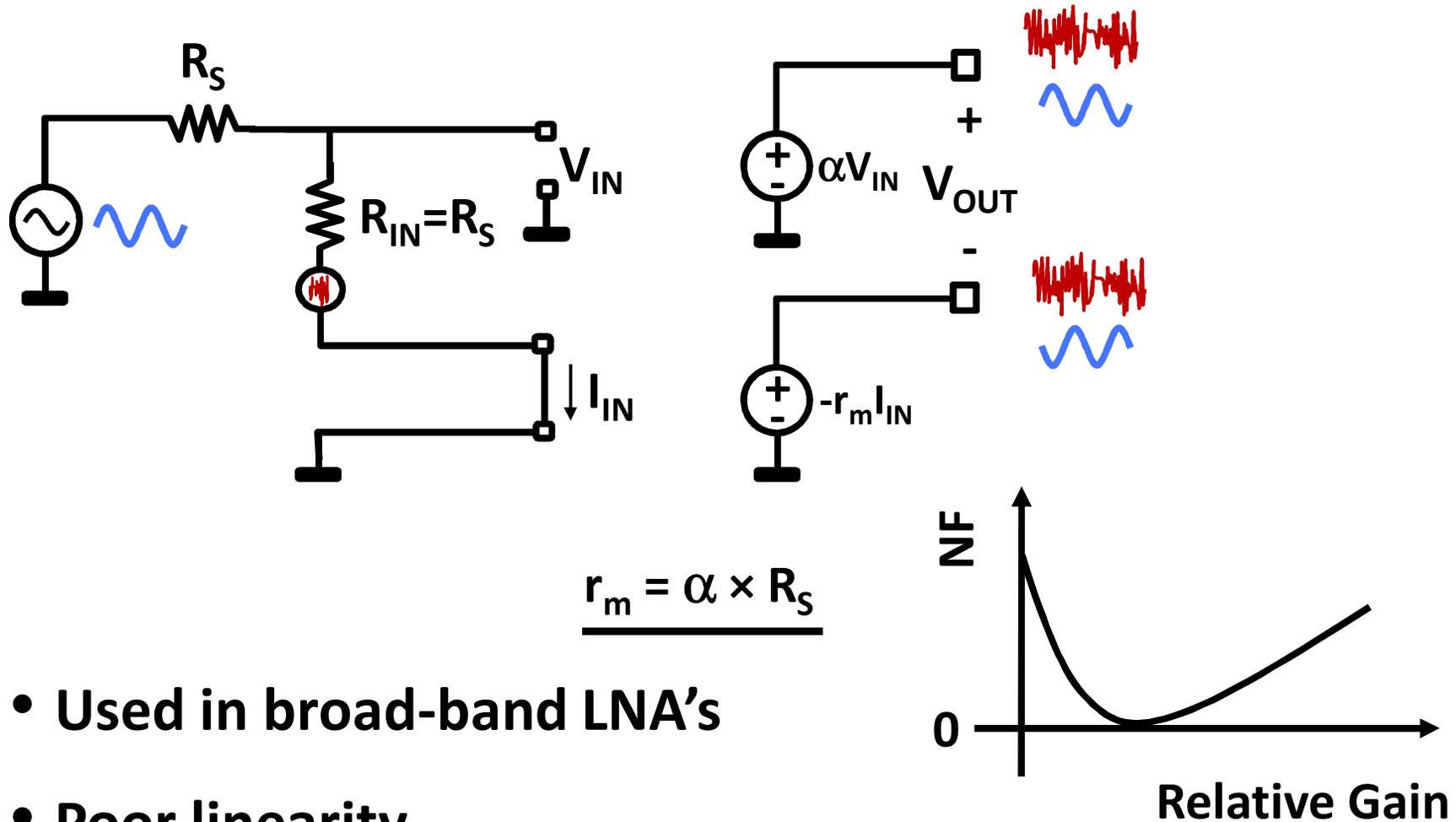

- Used in broad-band LNA's
- Poor linearity


# Noise Cancelling RX Architecture

Noise and linearity bottleneck

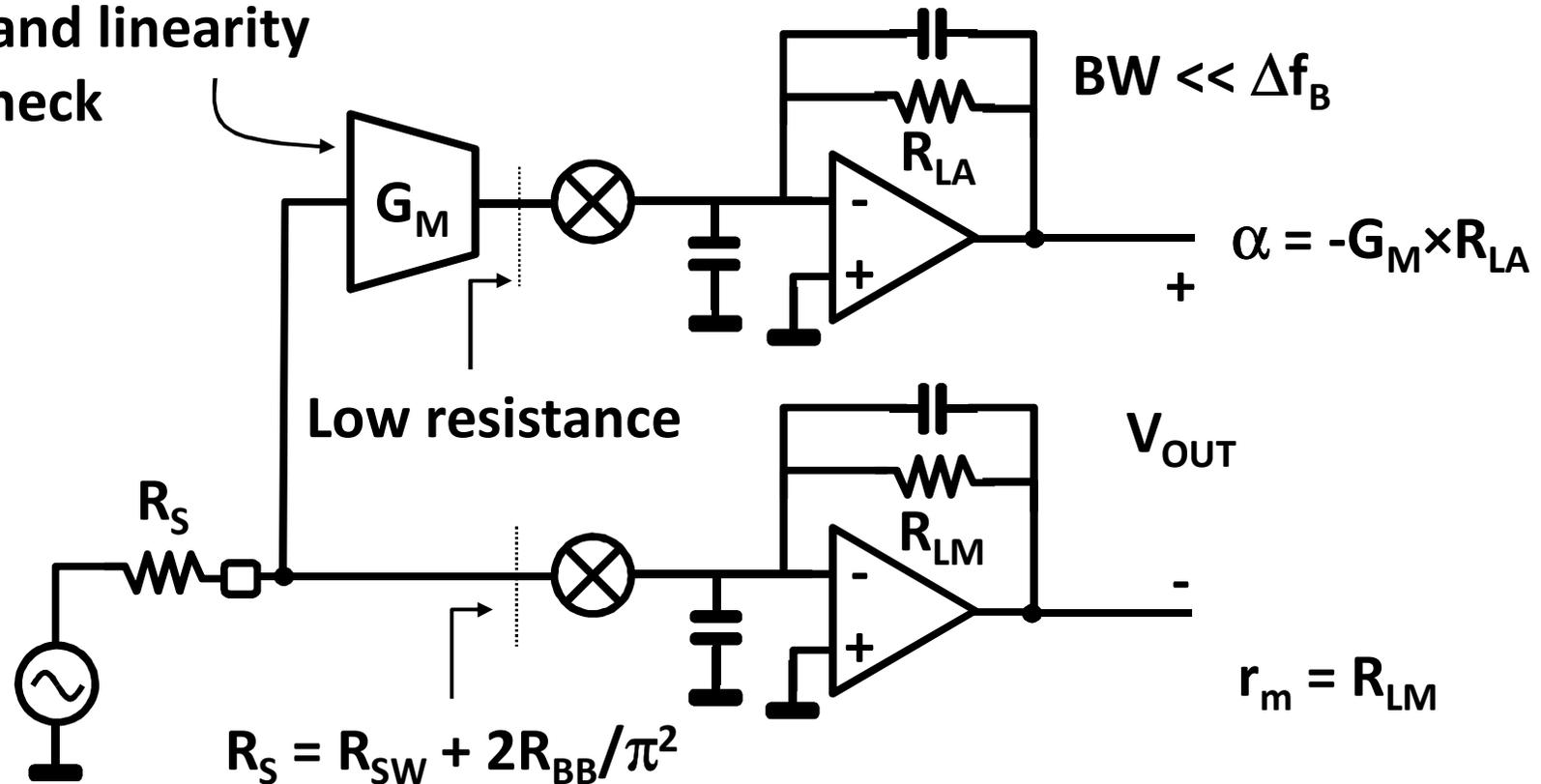



- Low noise and linear
- No Balun required

# Noise & Linearity Performance of NC RX

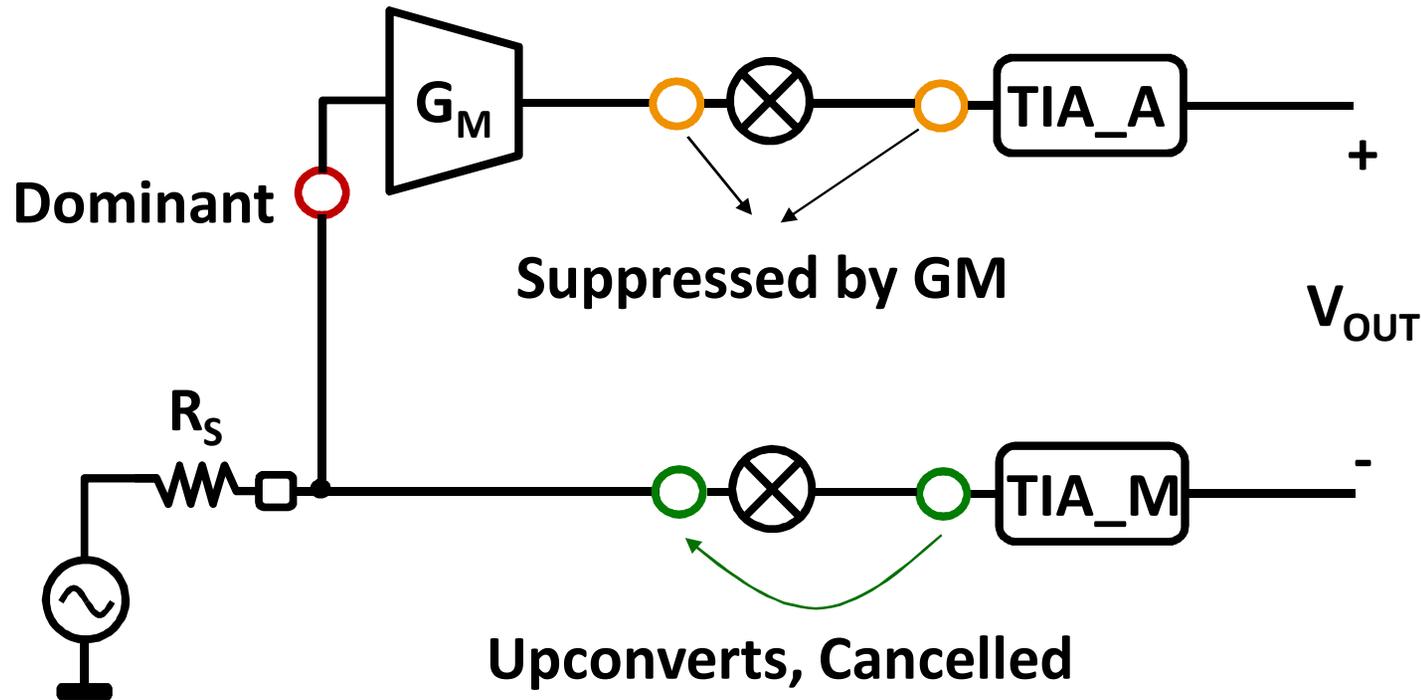


- $G_M$  noise dominant, no need to provide matching
  - $F \cong (1 + v_{GM}^2 / 4KTR_S) \times N$
- Similarly main path distortion cancelled:
  - $IIP_3 \cong (1 + R_S / R_{IN})^{3/2} \times IIP_{3\_AUX}$

# Over-Sampling Mixer Architecture

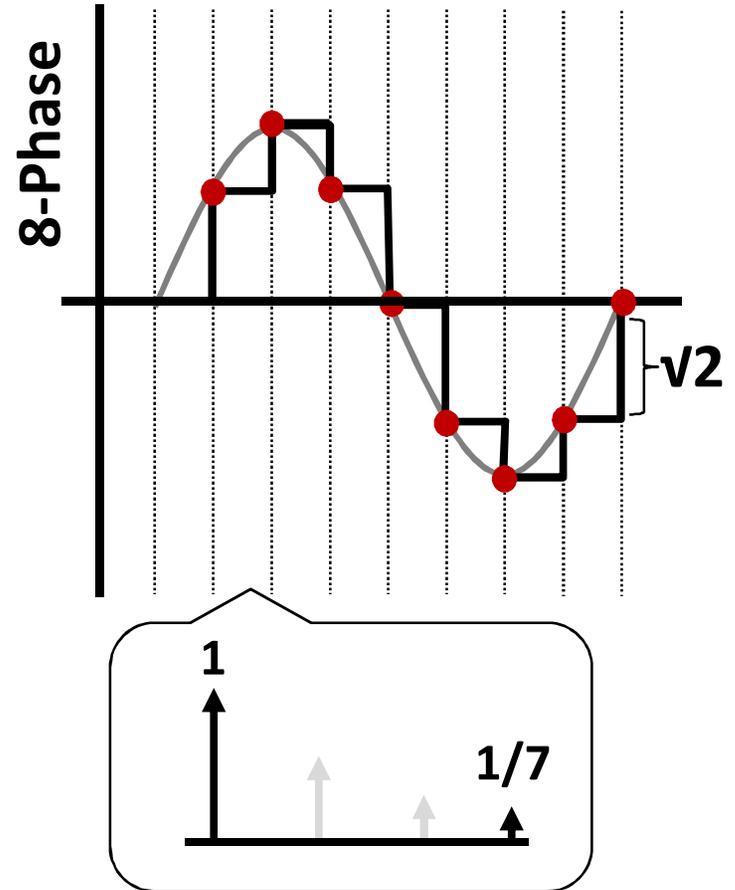
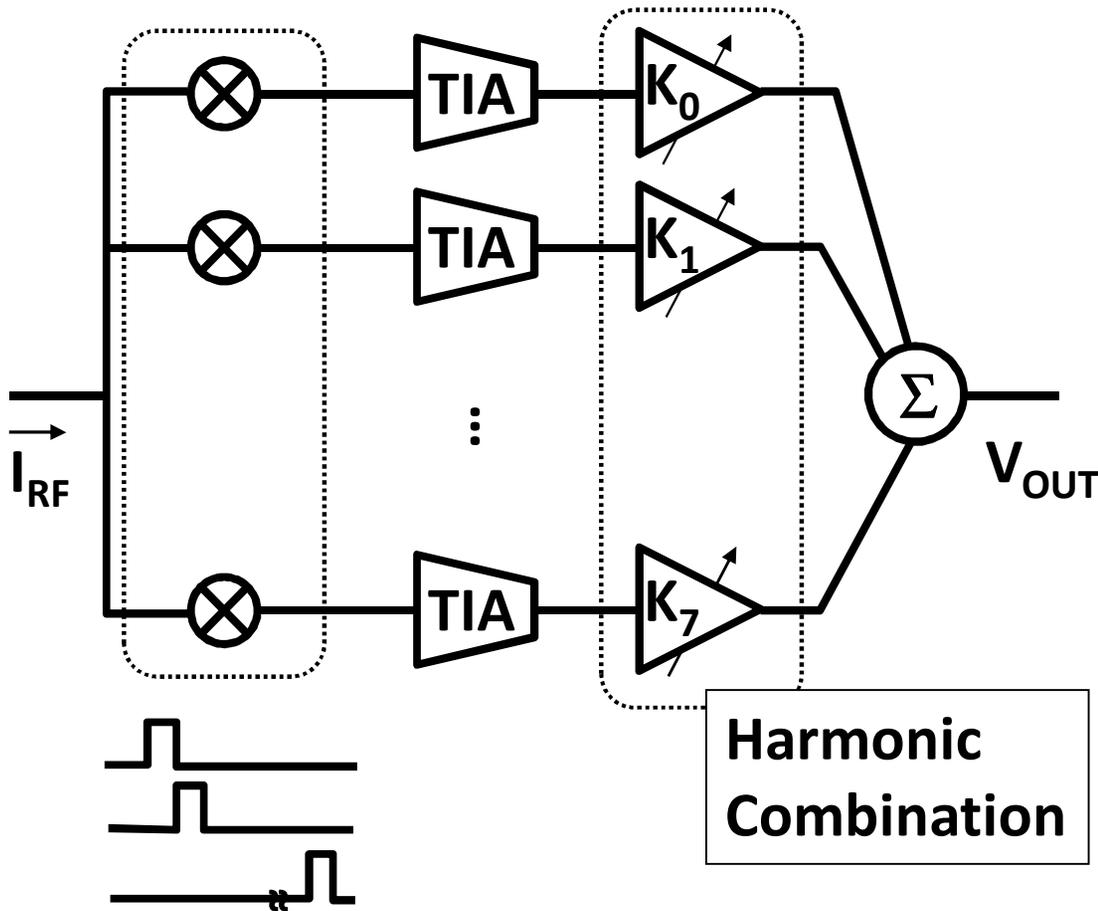


- Synthesizes arbitrary 8-phase LO: 
$$V_{OUT} = i_{RF}(t) \sum_{x=0}^7 K_x SW(t - \frac{x}{8T})$$

# Complete NC Receiver Architecture

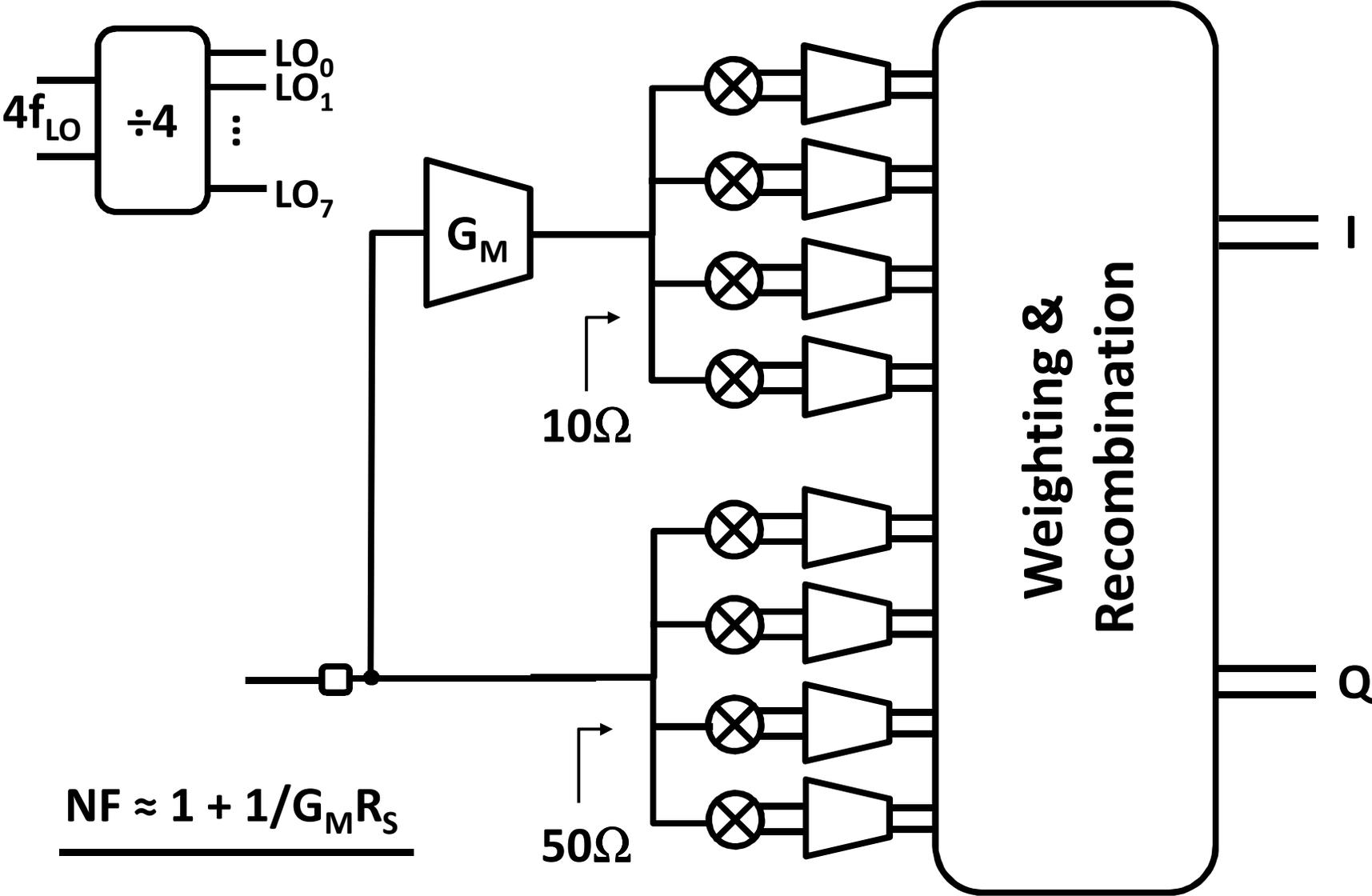



# RF $G_M$ Cell

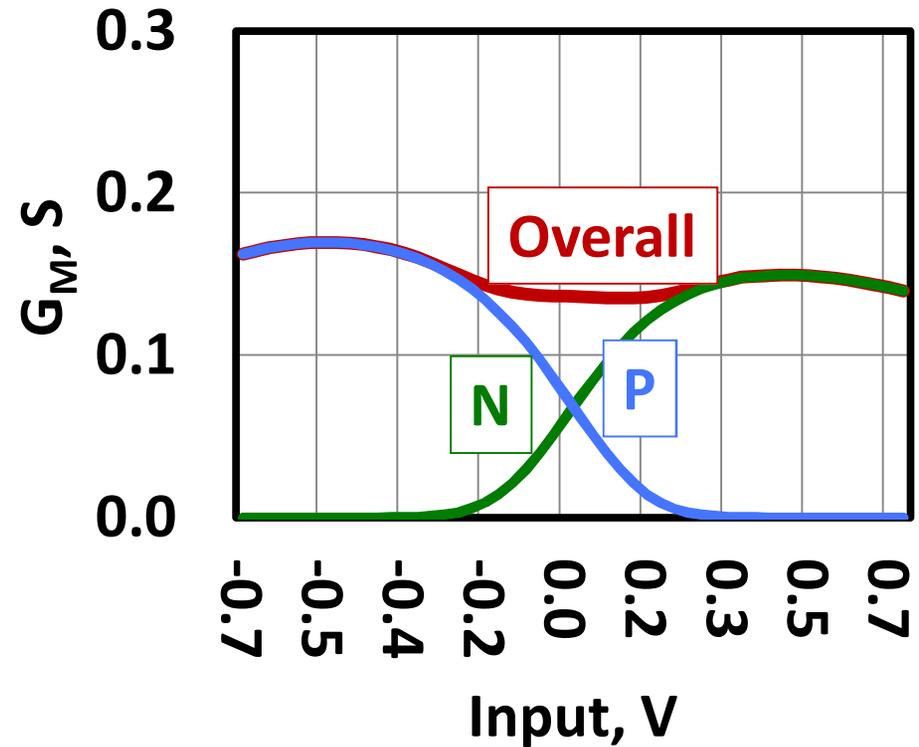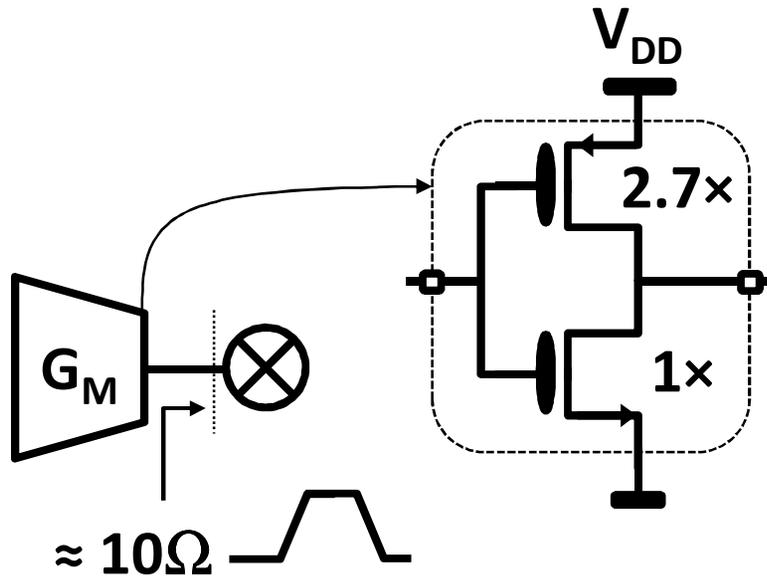

- Class AB transconductance
- Scalable
- Linear due to class AB and low-impedance loading

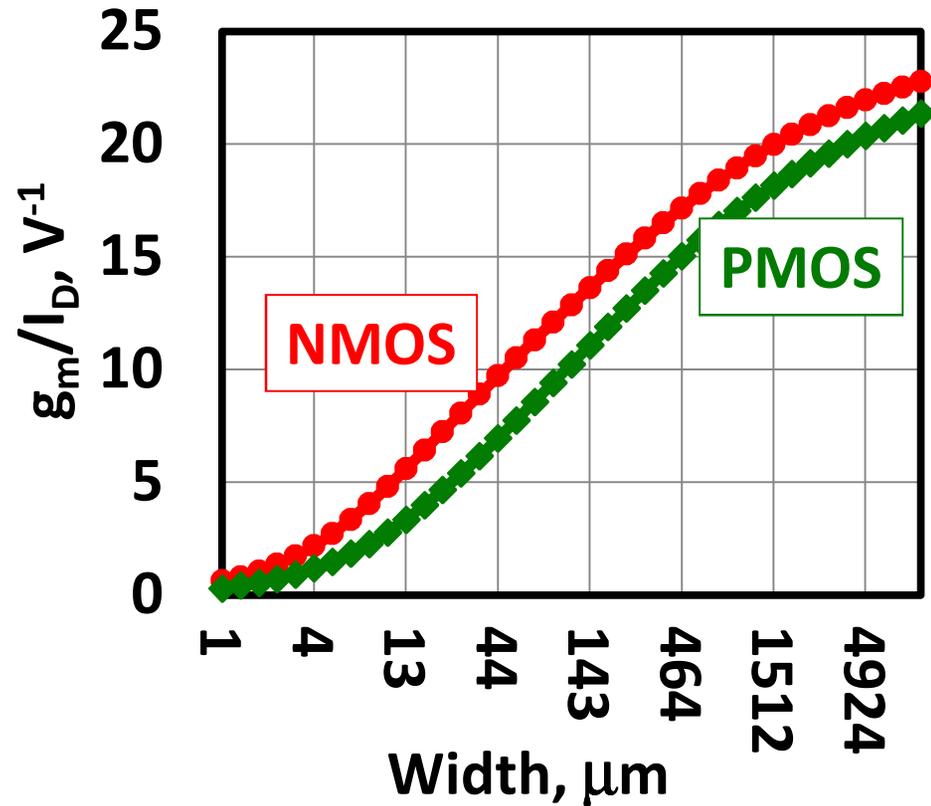
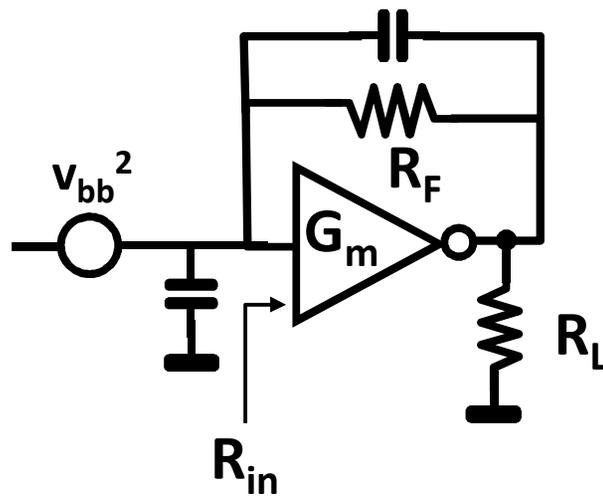
# Baseband TIA

$$\underline{G_m = g_{mn} + g_{mp} \approx 40 \times I_D}$$




- Most power efficient
- Noise:  $v_{bb}^2 \approx 4KT\gamma/G_m \approx 4KT/40I_D$
- Input resistance:  $R_{in} \approx R_F / A_{OPEN} \approx R_F / (G_m(R_F || R_L))$

# Receiver Scalability

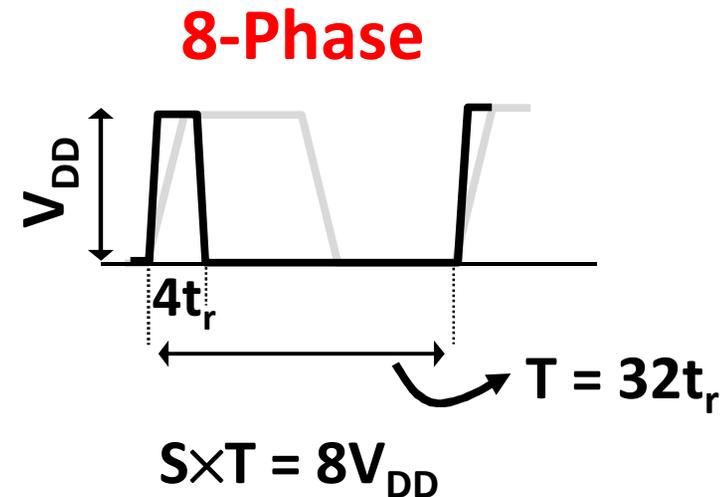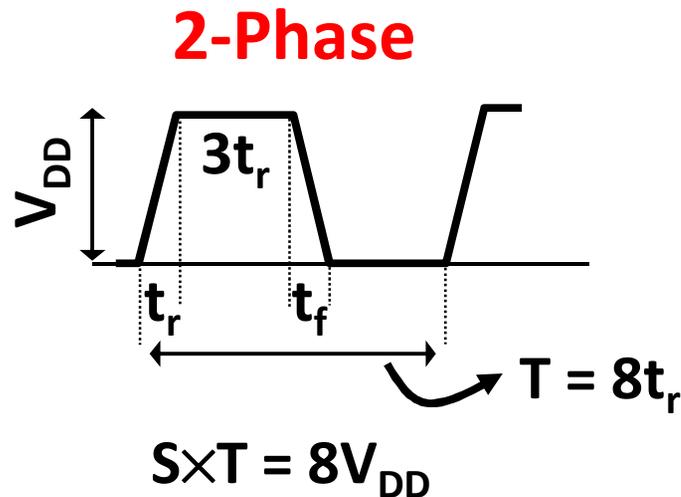


- Inherently relies on high-speed logic, switches
- In 40nm,  $t_r \approx 10\text{pS}$ :
  - 12.5GHz for 2-phase (overlapping)
  - 3.12GHz for 8-phase
- Scales w/ technology

# Noise Figure

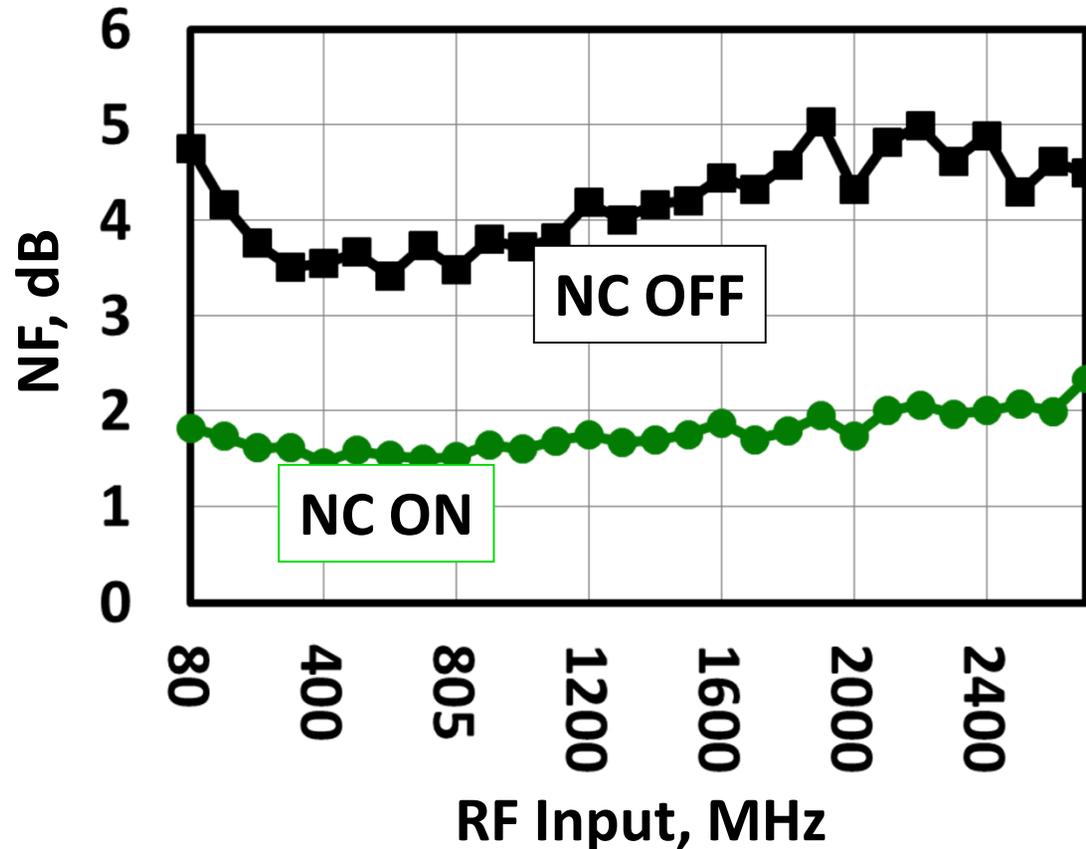


- 1/f corner reduces from 100kHz to less than 10kHz
- Corresponds to <-113dBm GSM sensitivity

# Blocker Noise Figure

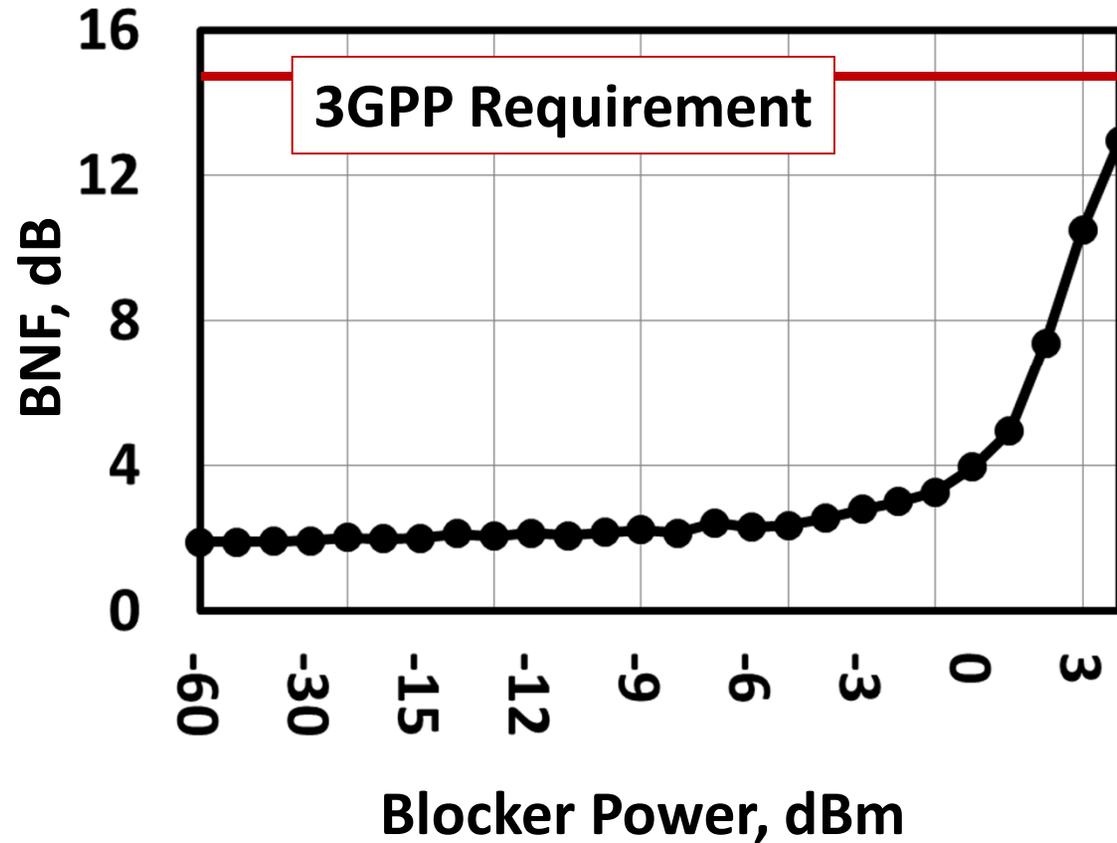


- 4.1dB 0dBm BNF, mostly limited by reciprocal mixing

# Linearity

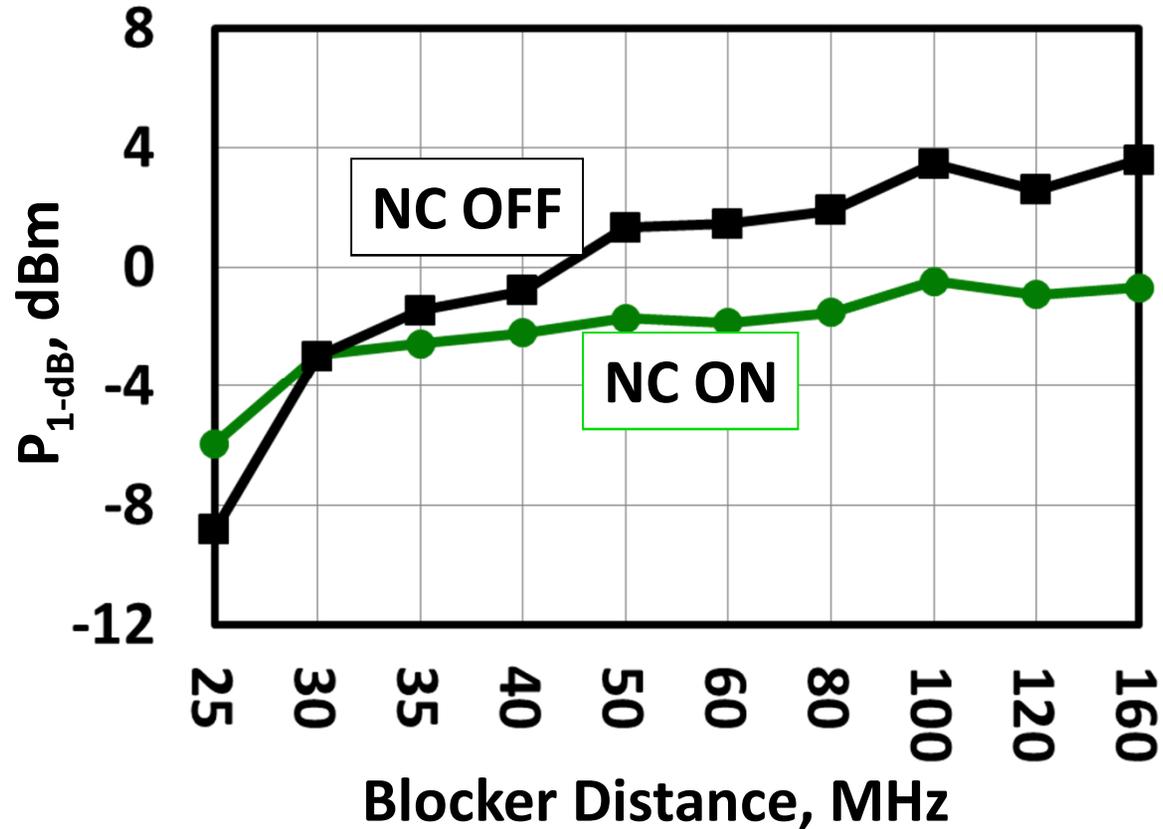

- Close to 0dBm 1dB compression at maximum gain

# NF vs. Relative Phase Correction

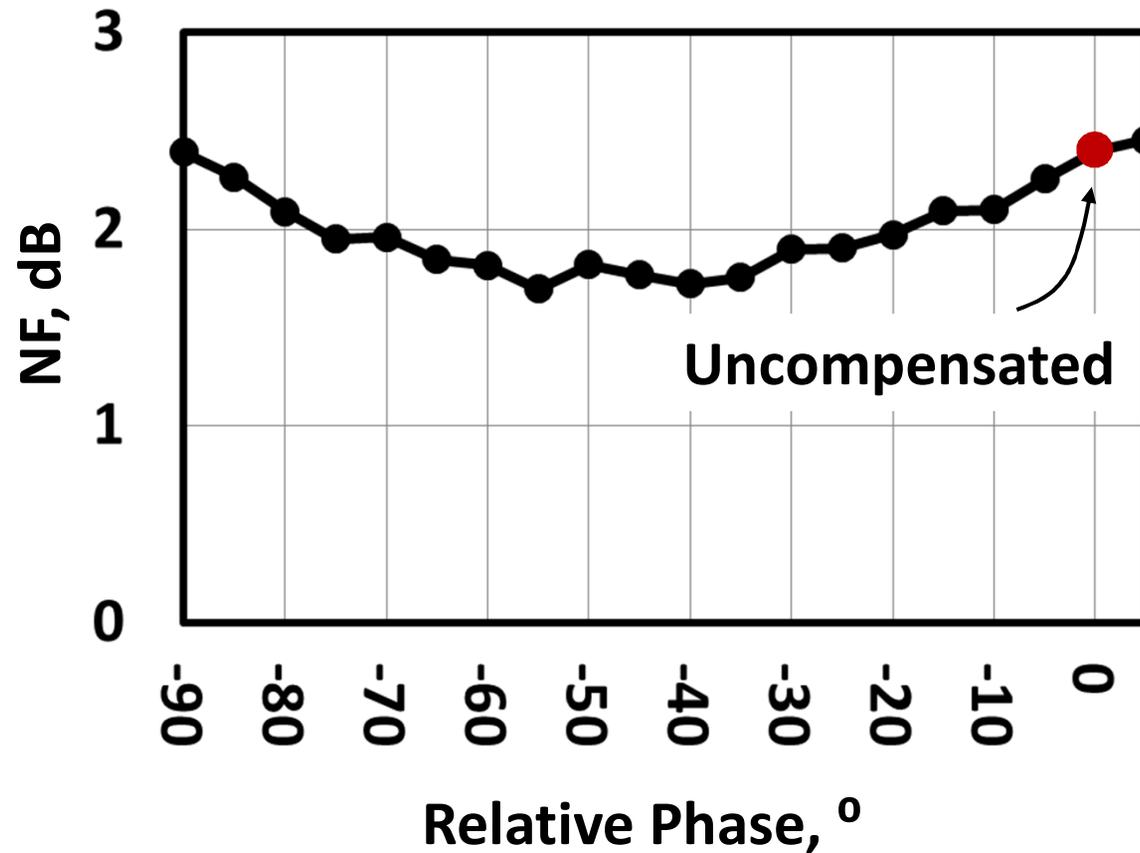


- Robust at optimum point

# Summary of Performance


---

Architecture	Mixer first	NC LNA	NB SAW-Less	NC RX
RF Range	0.1-2.4GHz	0.4-6GHz	900/1800	0.1-2.7GHz
Input	SE	Differential	Differential	SE
NF at 2GHz	7dB	4.4dB	4.1dB	1.8dB
0dBm BNF	NA	13dB	7dB	4.1dB
3 <sup>rd</sup> /5 <sup>th</sup> HR	35/43dB	None	None	42/45dB
OB IIP3	25dBm	10dBm	NA	14dBm
RX Current	12mA	12mA	37mA	12mA
Area	2mm <sup>2</sup>	2mm <sup>2</sup>	1.4mm <sup>2</sup>	1.2mm <sup>2</sup>
Technology	65nm	40nm	65nm	40nm

# NC RX Die Photo

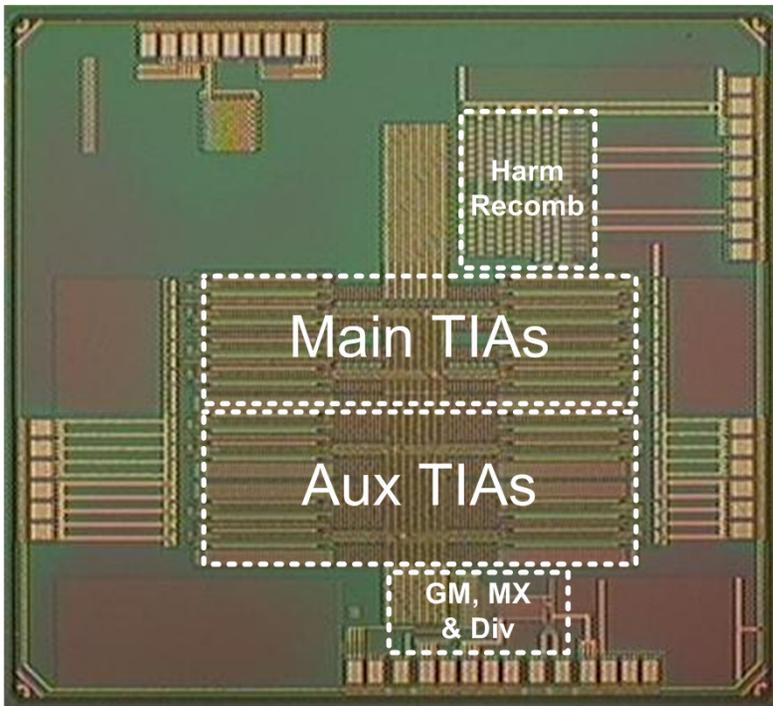

**Differential**

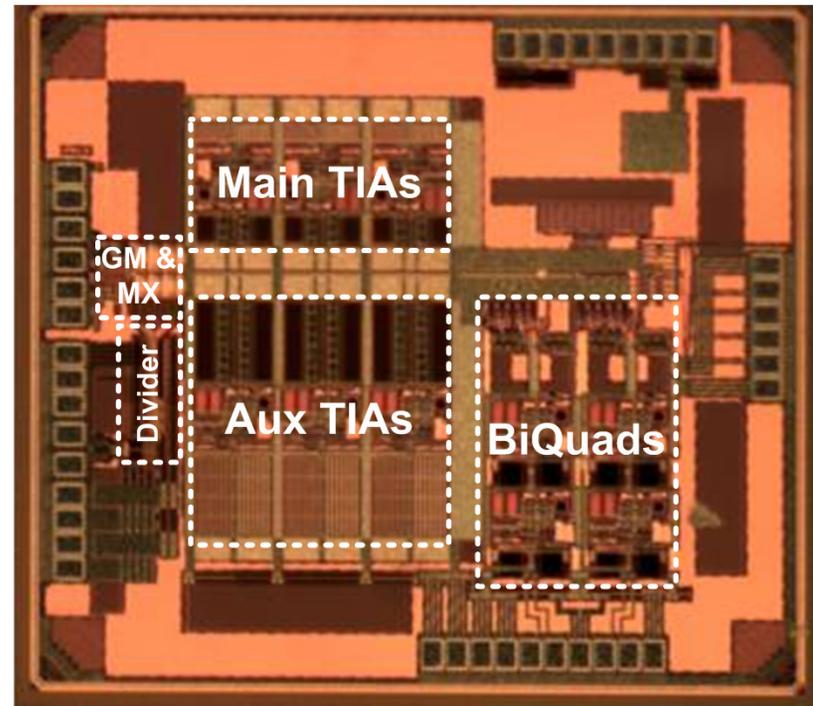


**Single-Ended**

- Die area:  $1.2\text{mm}^2$
- Inductor-less

# Reciprocal Mixing Issue – System Approach


---

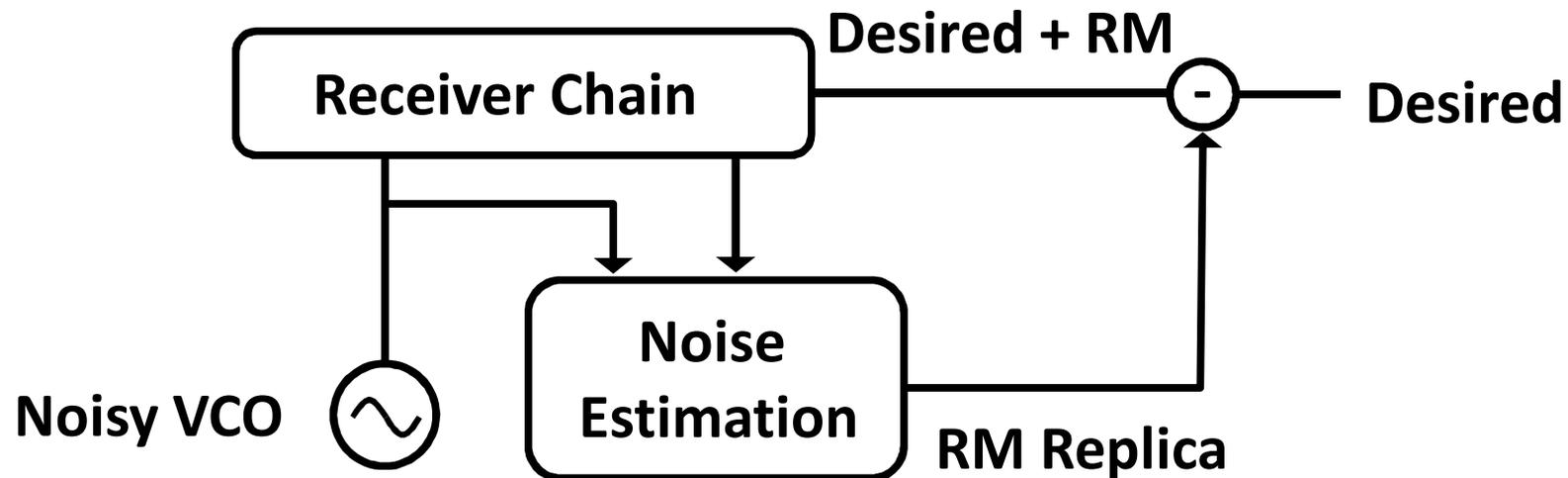


Reciprocal mixing NF = 174 - P<sub>B</sub> - PN

- Start w/ a low-power/cost VCO
- Deal with its consequences in system level
- Proper phase noise estimation is key

# Symmetry of Reciprocal Mixing

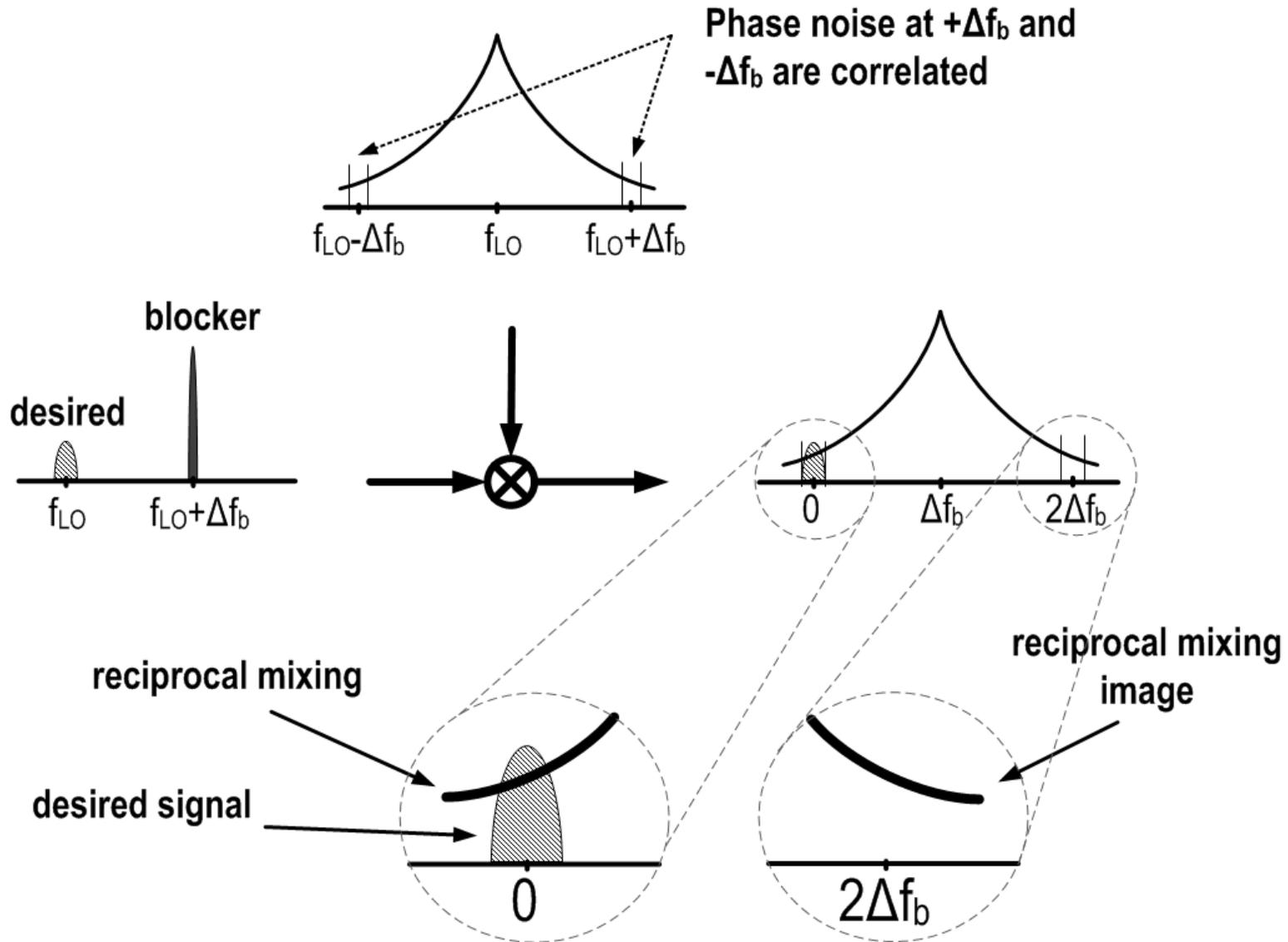


# RM Cancellation Architecture


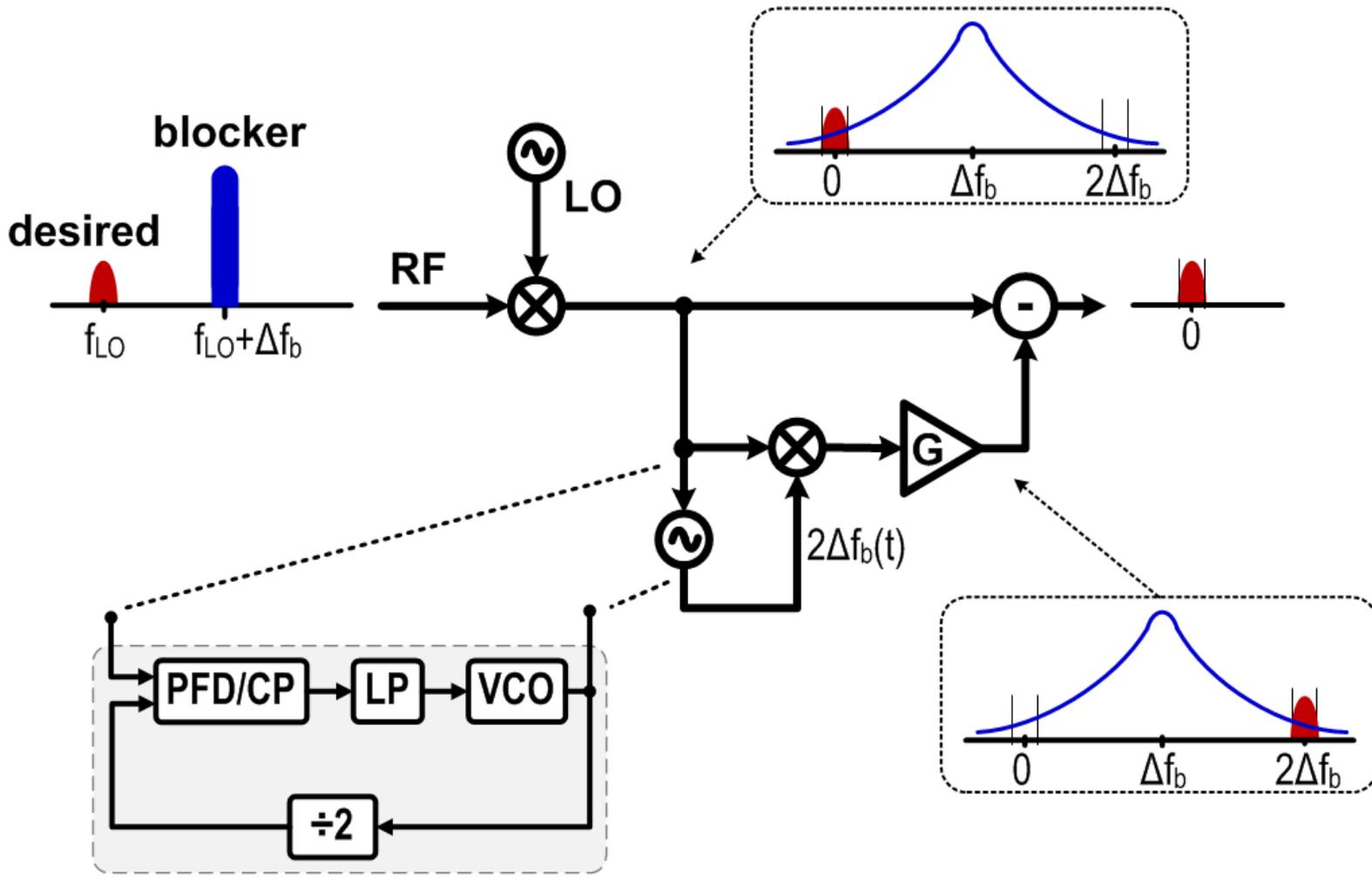


**Wideband PLL**  
(Low Frequency & Low Power, >20dB spec relaxation)


# Limiter Based Architecture

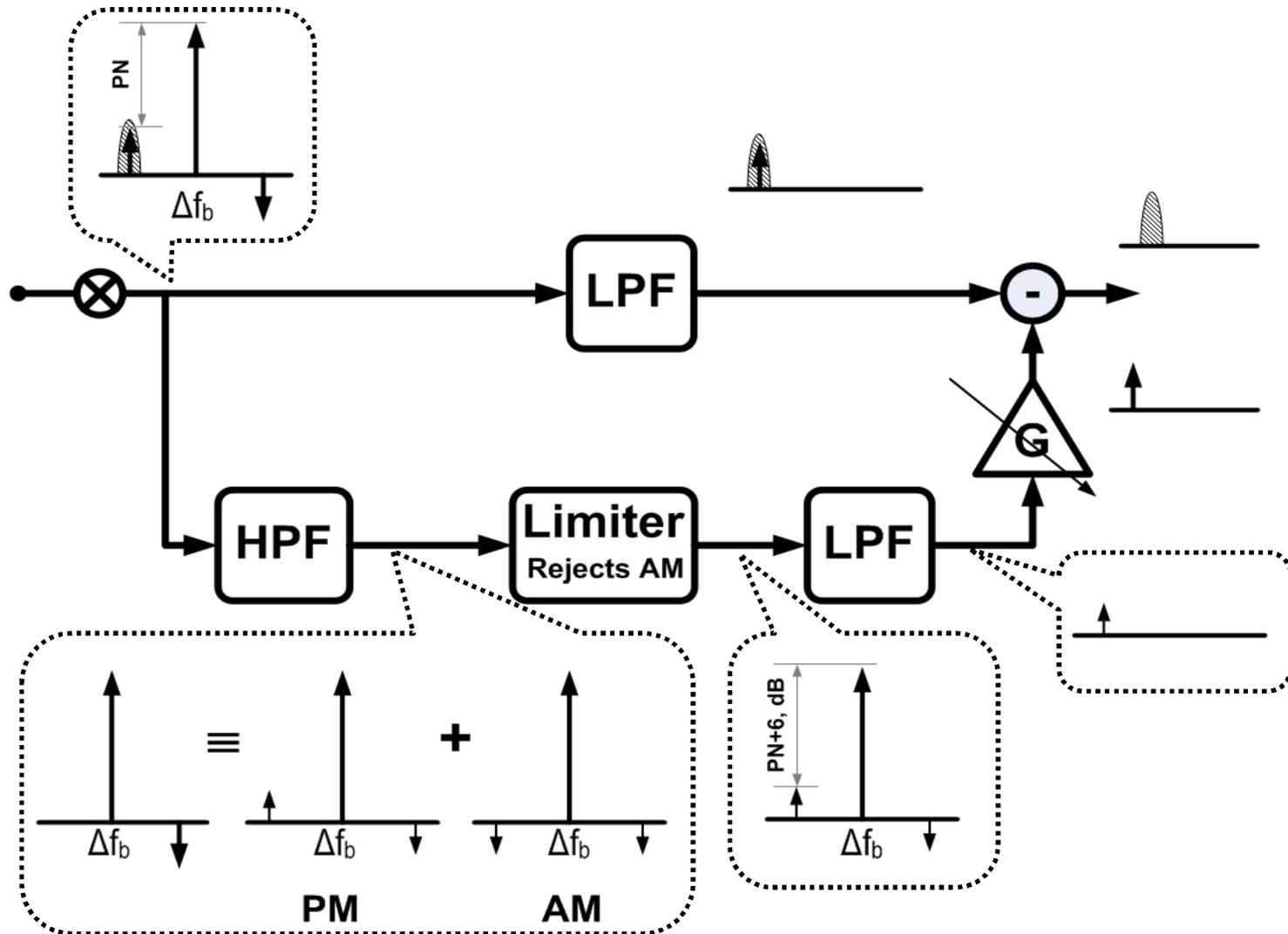


# Noise Aliasing in a Limiter

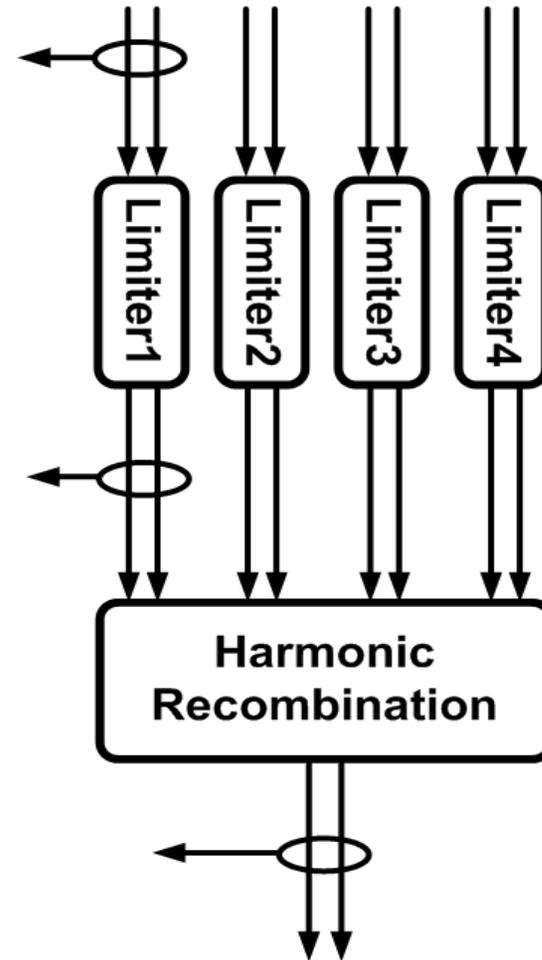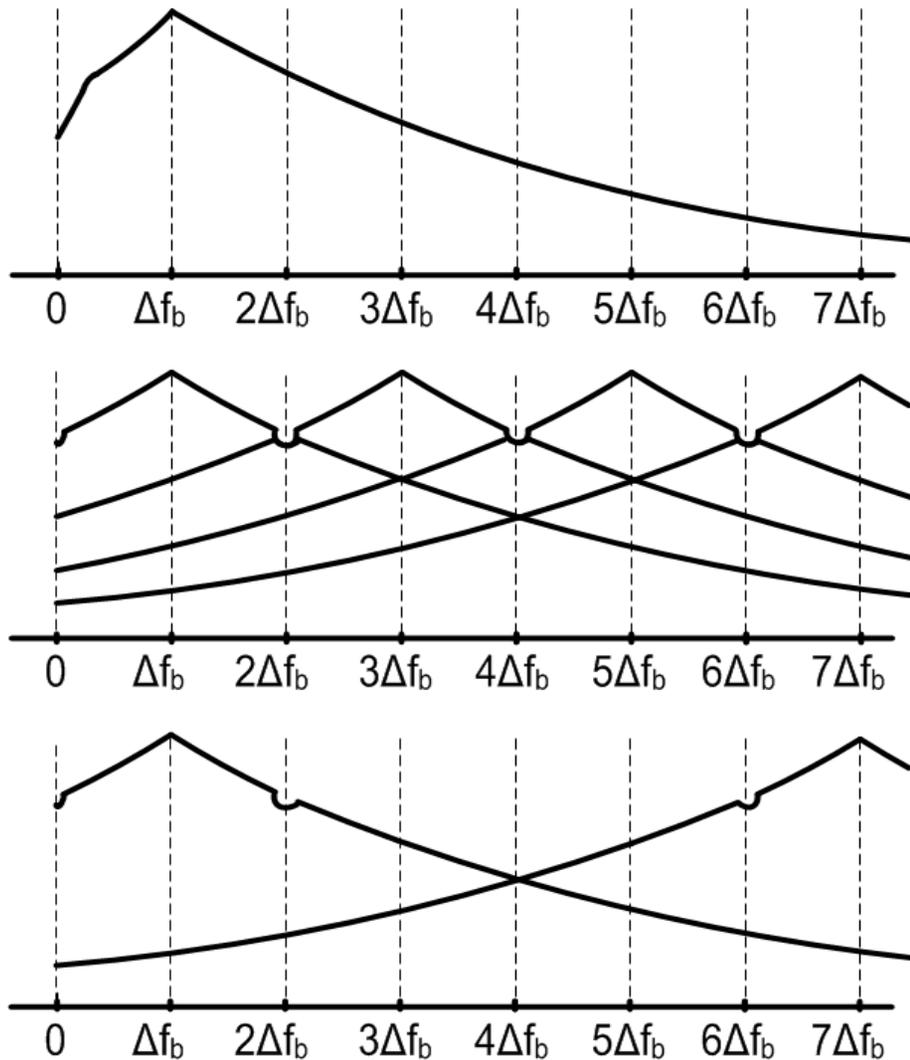

# Prototype RM Cancelling Receiver

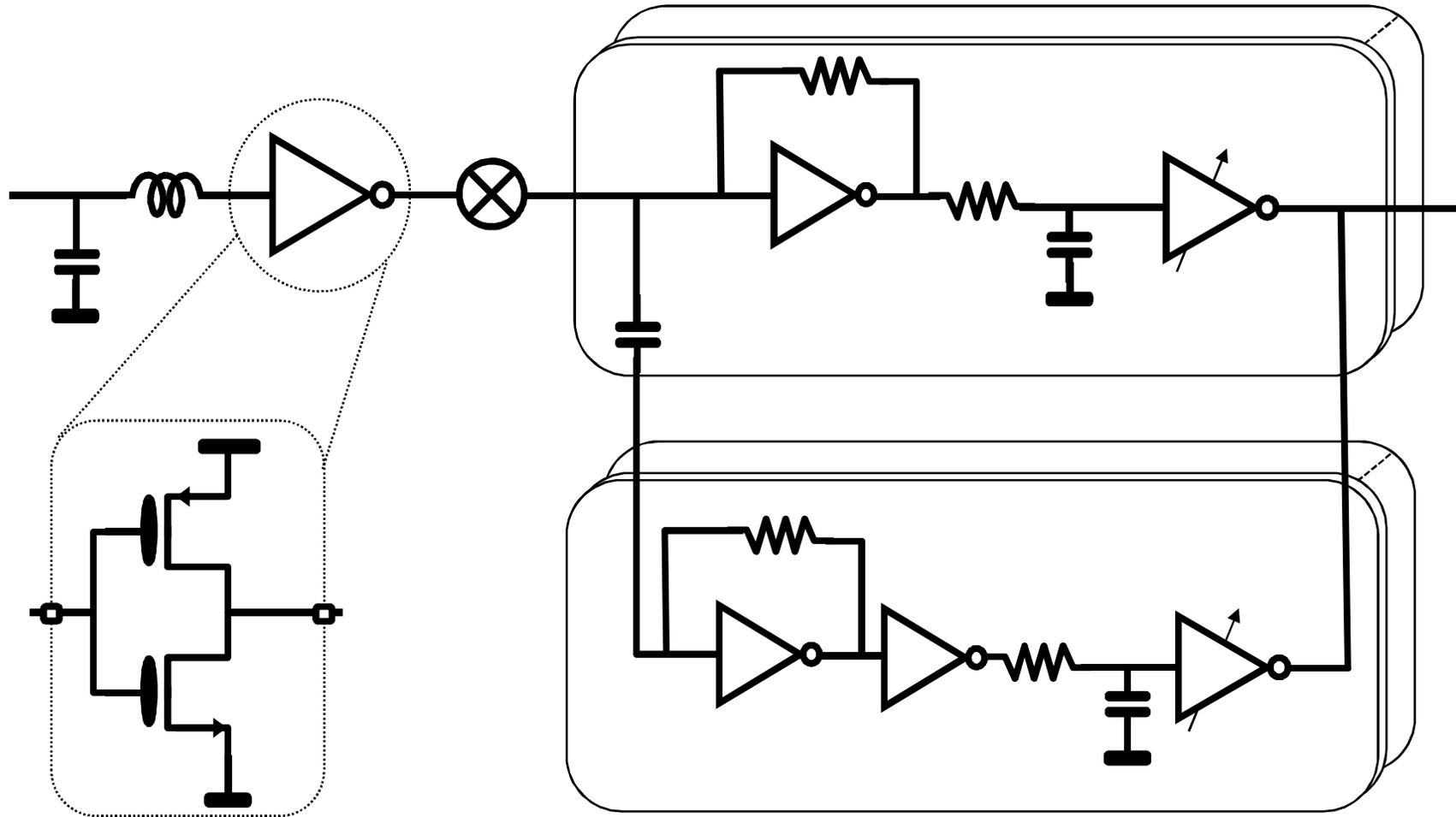


# Measured Blocker Noise Figure

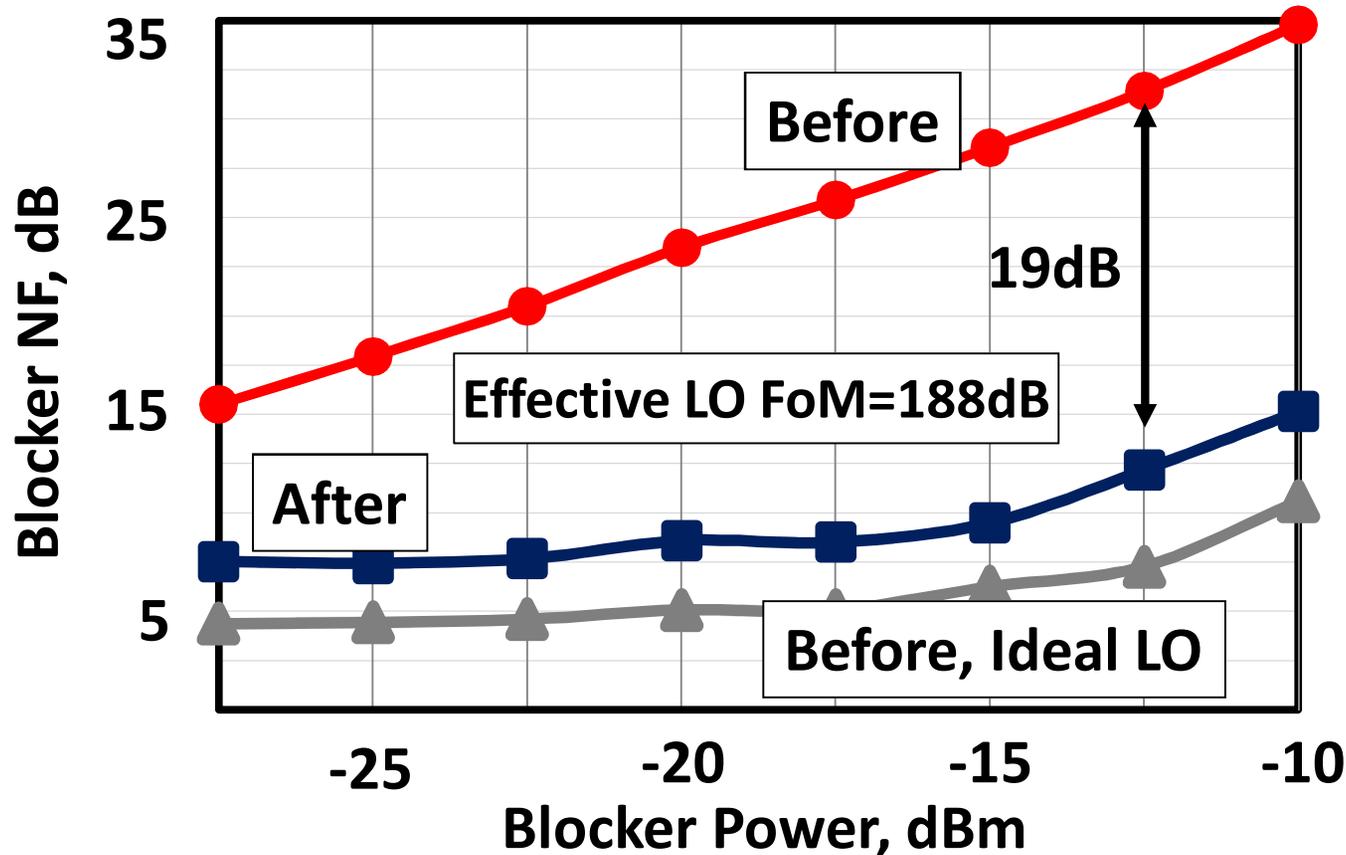

- Blocker offset as low as 10MHz
- SS NF of about 2.4dB


# RM Cancelling RX Die Photo

---

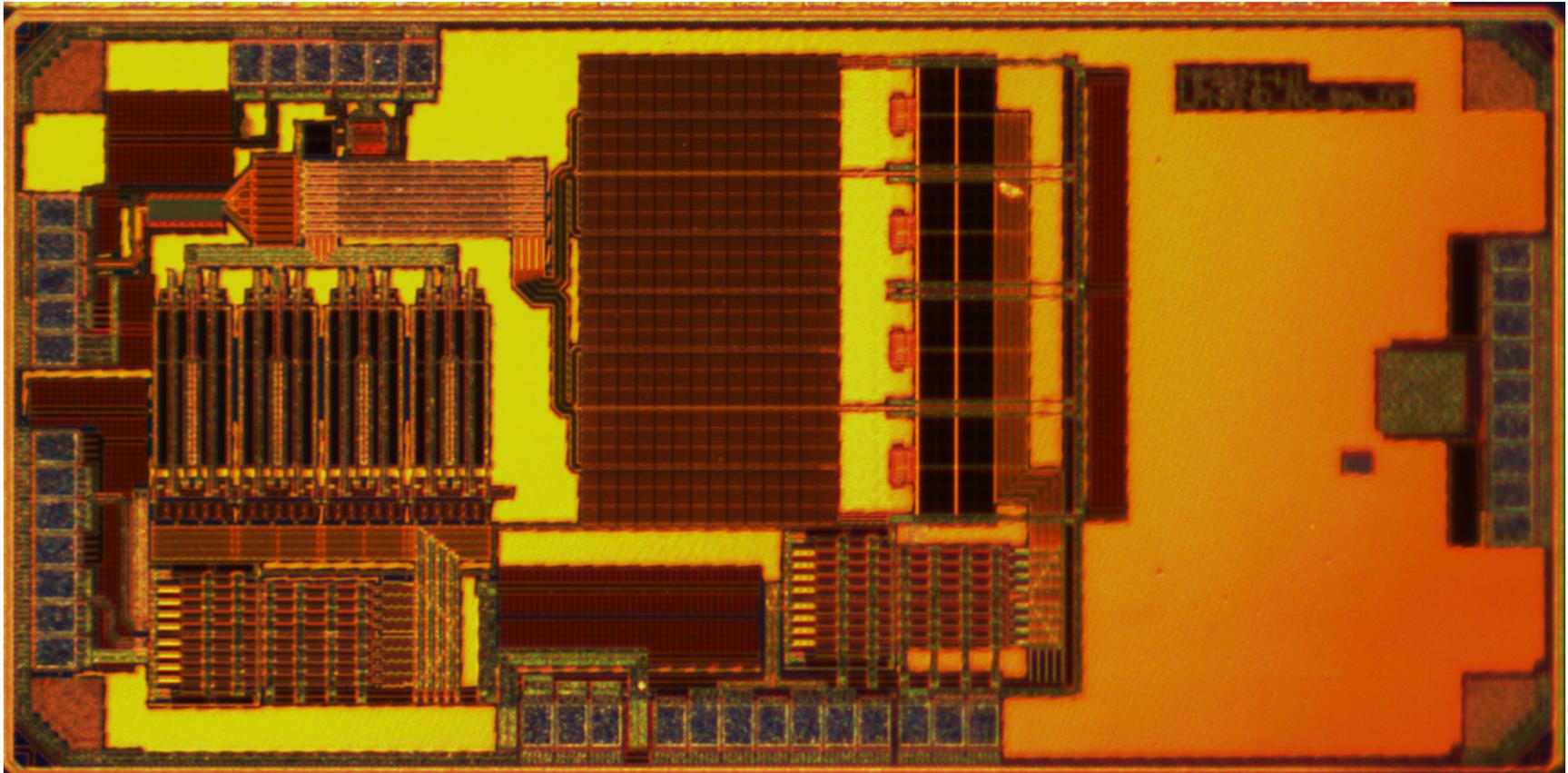

- 40nm CMOS, 1.4mm<sup>2</sup>


# Receiver Architecture for Coexistence

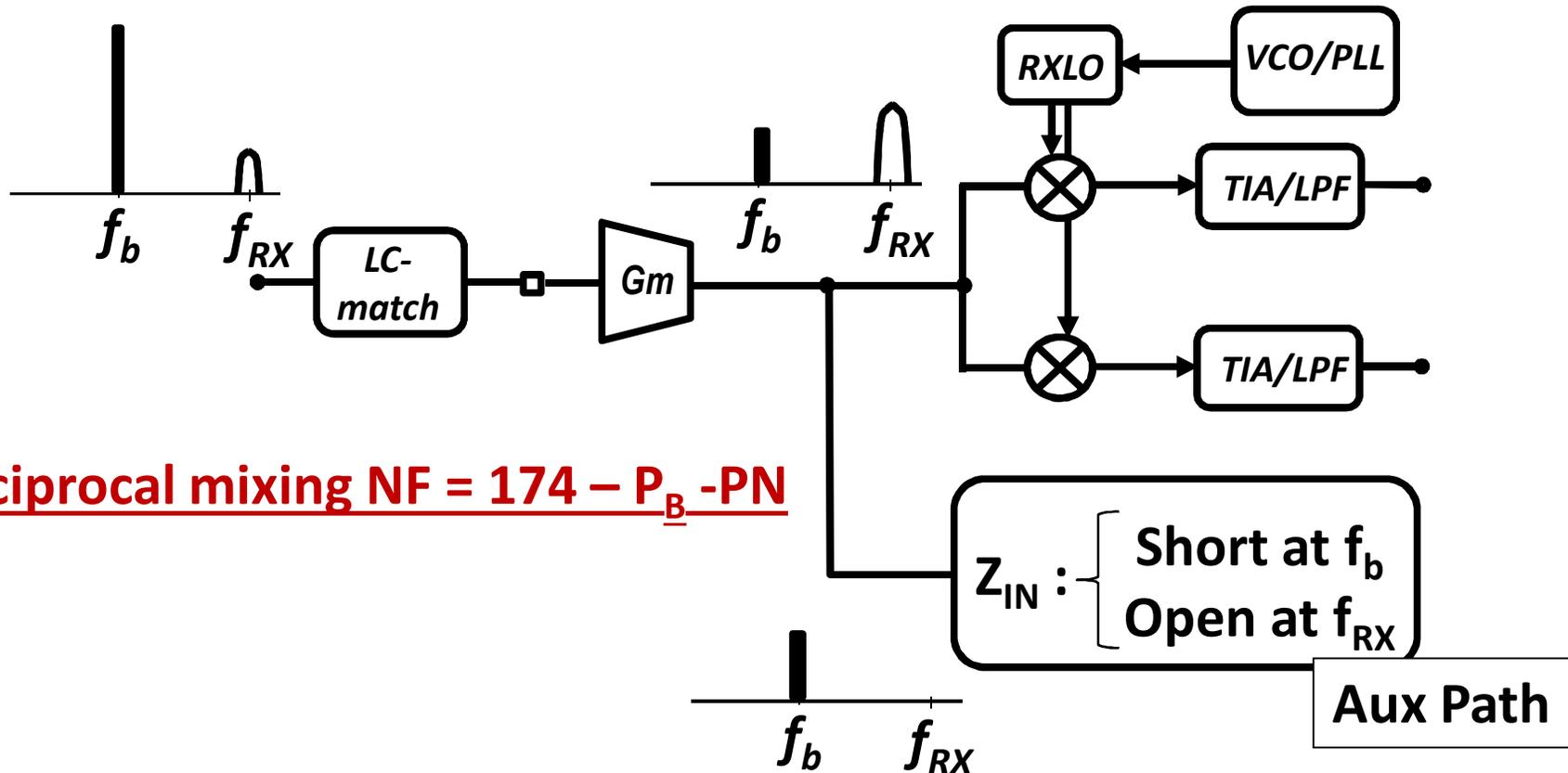

Reciprocal mixing  $NF = 174 - P_B - PN$


- Second path to divert blocker away
- Relaxes noise and linearity of main receiver

# N-Path Impedance Implementation

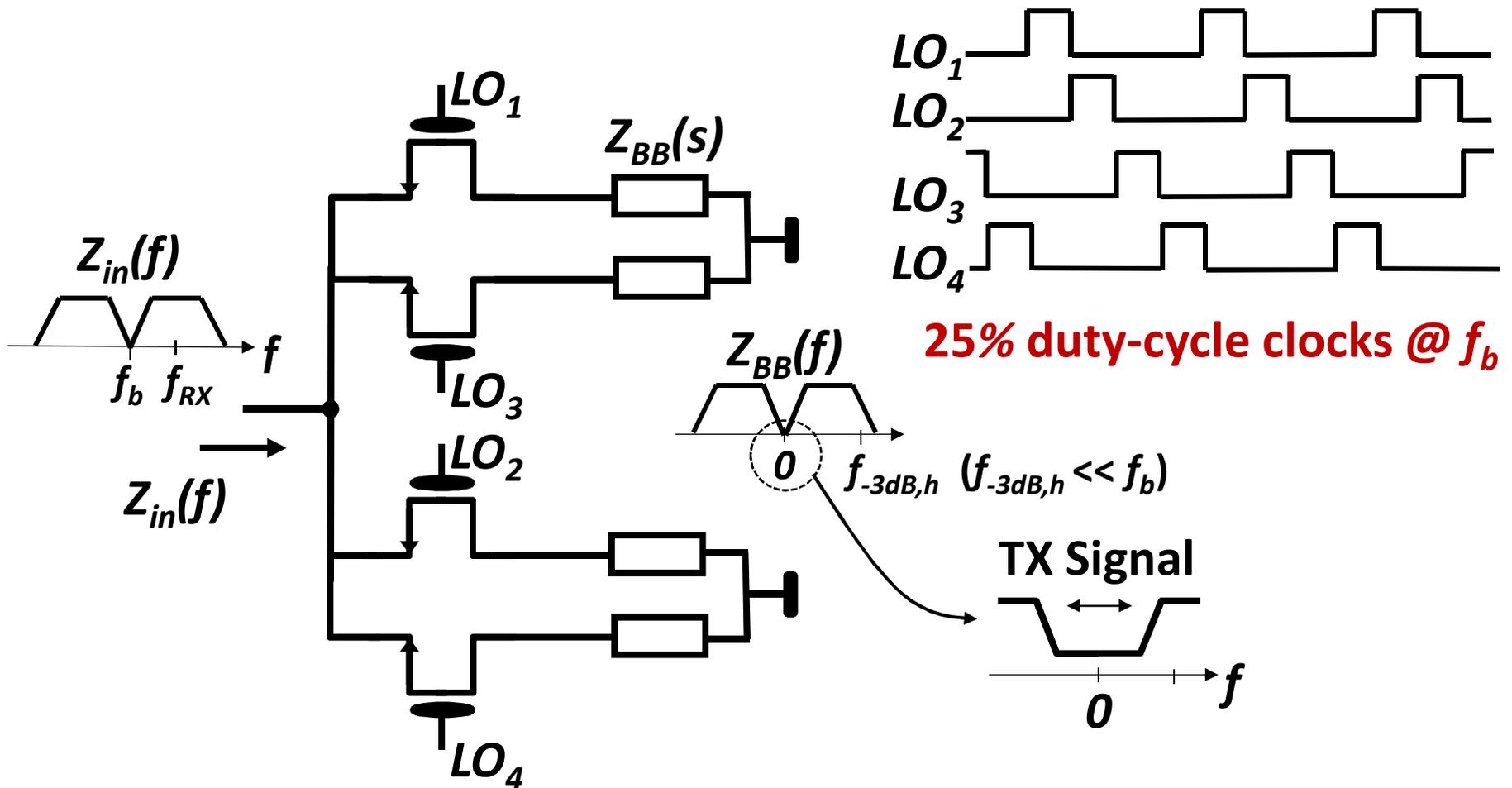


- Clocked by the aggressor TX LO

# Coexistence Receiver Architecture

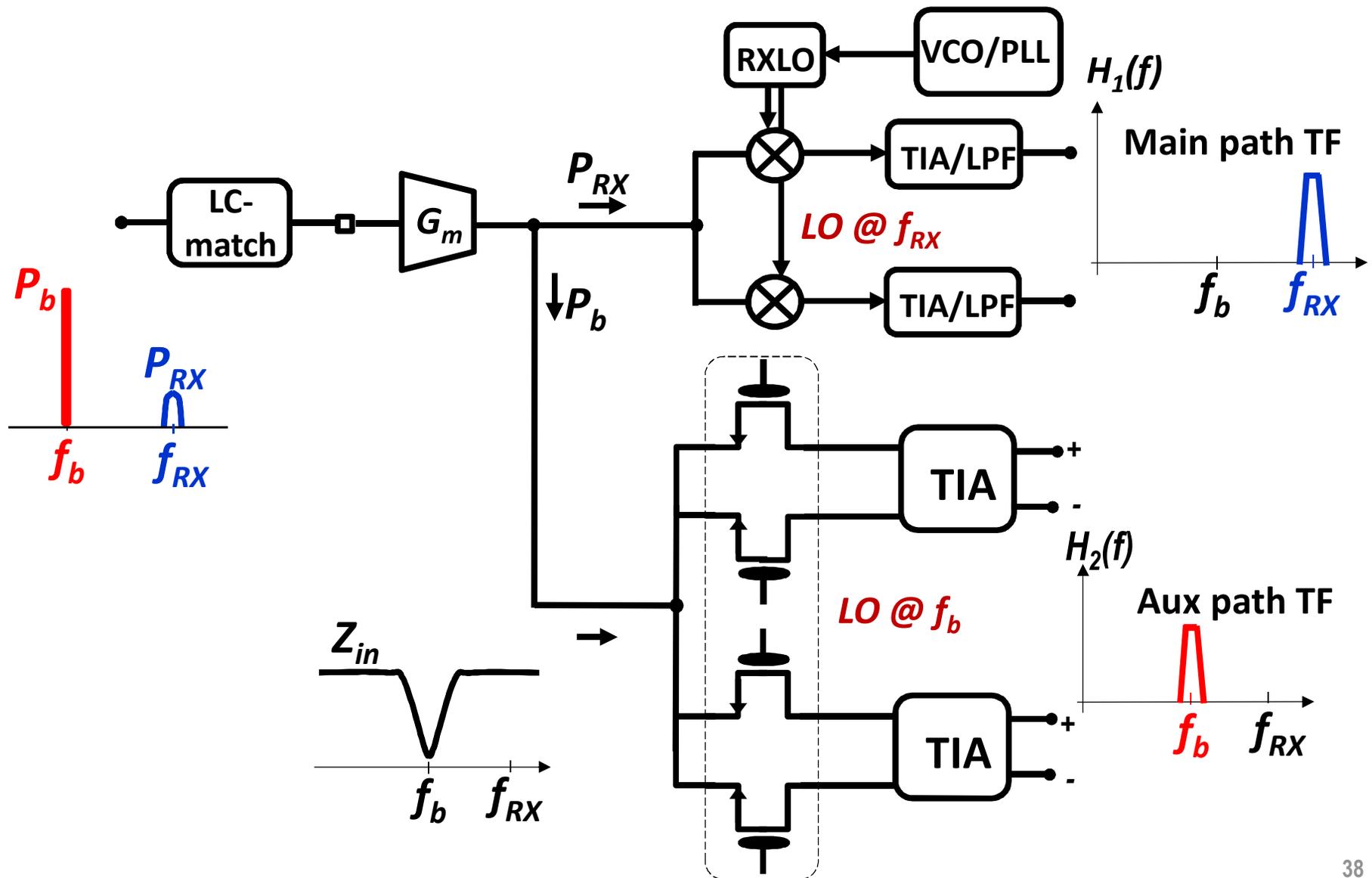

# Measured Blocker Noise Figure

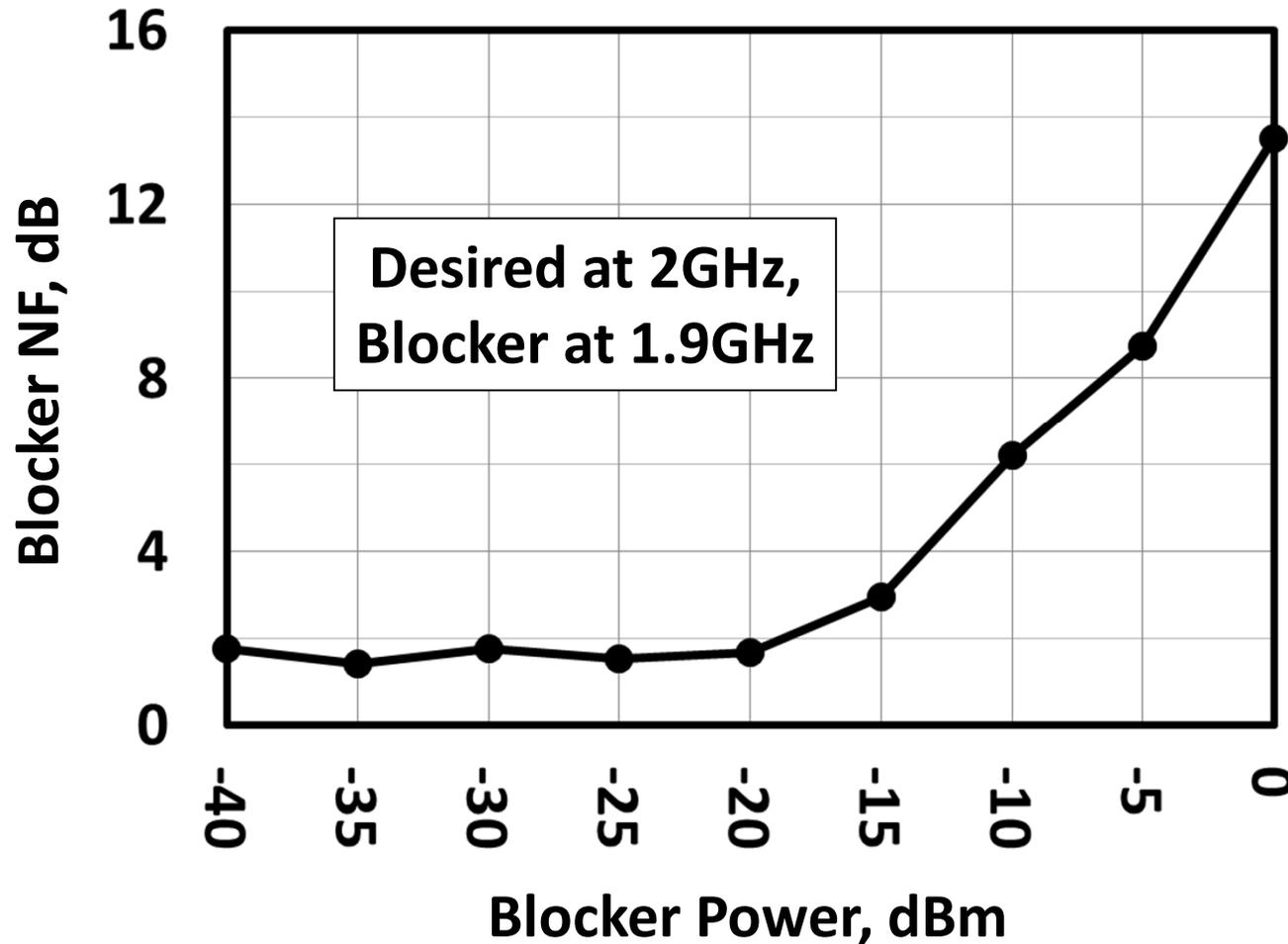

- $NF > 25\text{dB}$  if Aux path de-activated

# RX Performance Summary

Parameter	[1]	[2]	[3]	This work
NF, dB	2.5	2.5	4	1.7
OB IIP3, dBm	-2.5	-4	-14	-2.5
OB IIP2, dBm	> 50	58	N/A	> 50
0dBm Blocker NF, dB	N/A			13.5
Battery Current, mA	65	44	46	10
Total RX Area, mm <sup>2</sup>	6.7	3.4	2.2	0.93
Technology	130nm	90nm	65nm	40nm
Application	Cellular	Cellular	WiFi	Generic


[1] T. Sowlati, et al., "Single-chip multiband WCDMA/HSDPA/HSUPA/EGPRS transceiver with diversity receiver and 3G DigRF interface without SAW filters in transmitter / 3G receiver paths," ISSCC, 2010, pp. 116-117.

[2] M. Nilsson, et al., "A 9-band WCDMA/EDGE transceiver supporting HSPA evolution," ISSCC, 2011, pp. 366-368.

[3] Y. H. Chung, et al., "A 4-in-1 (WiFi/BT/FM/GPS) connectivity SoC with enhanced co-existence performance in 65nm CMOS," ISSCC, 2012.


# Coexistence RX Die Photo

---

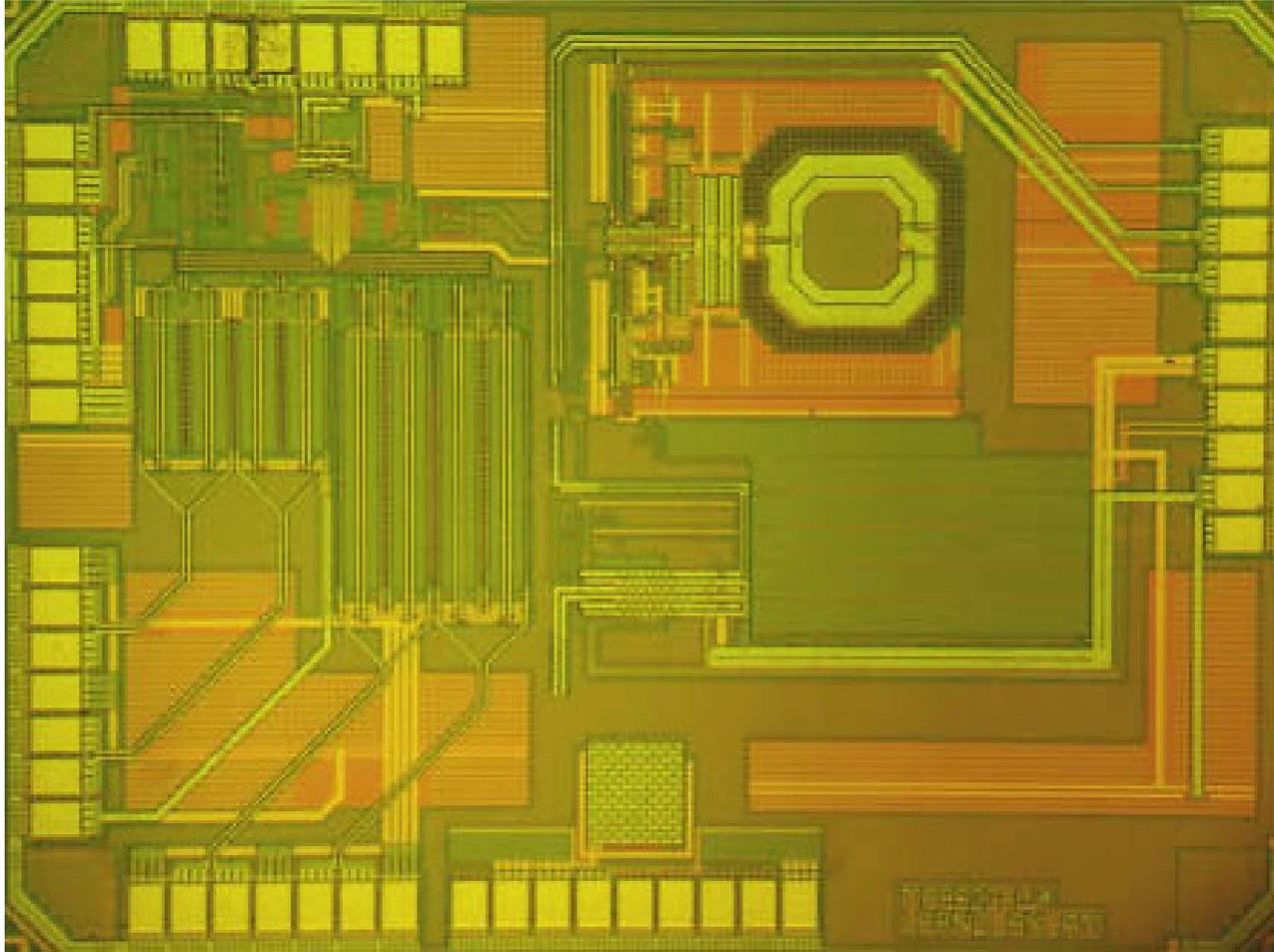

**40nm CMOS with active area of 0.93mm<sup>2</sup>**

# Summary & Conclusions

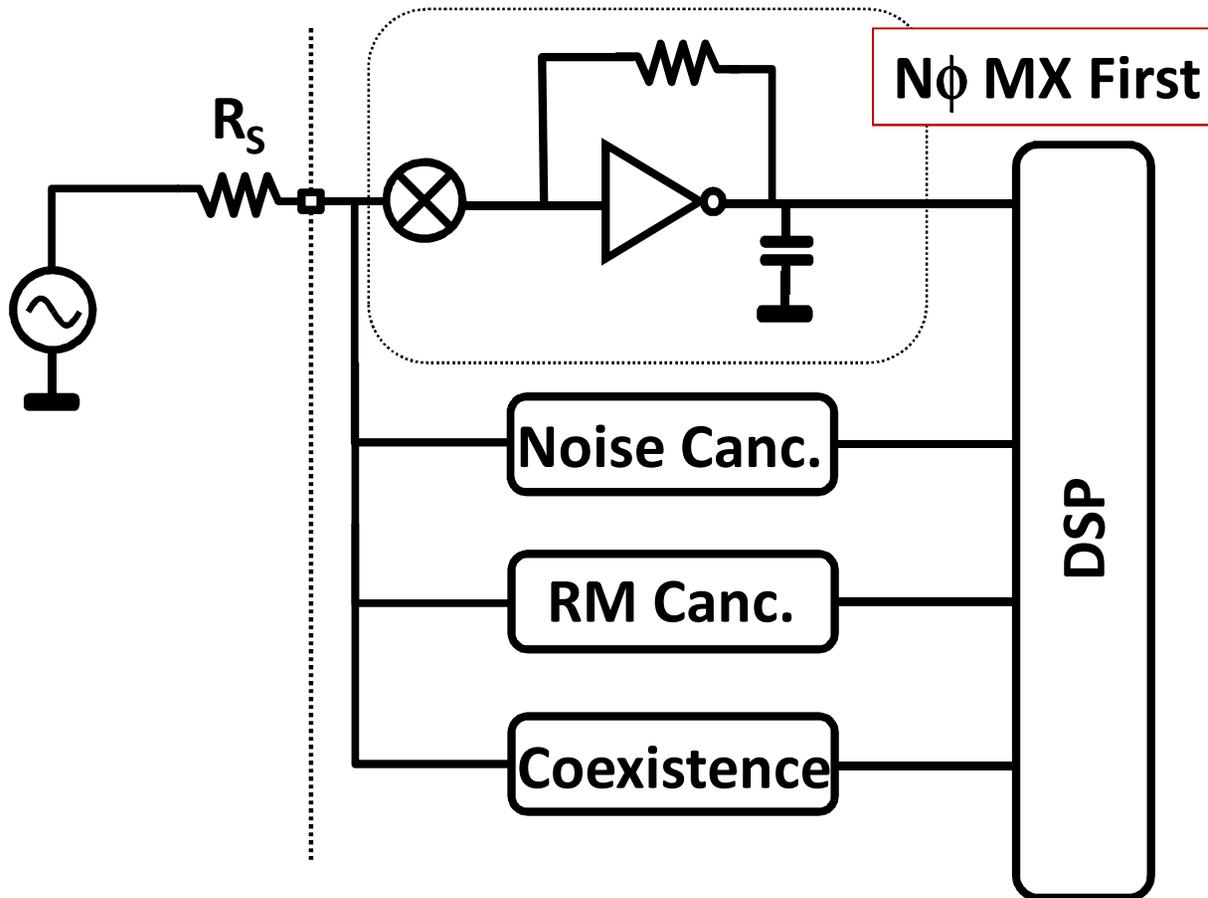

- Scalable
- Immune to large blockers and/or low-power