 


RF ESD Protection Strategies – The Design and Performance Trade-off Challenges



Ph.Jansen, S.Thijs, D.Linten, M.I.Natarajan
V.Vassilev, M.Liu, D.Trémouilles,
S.Decoutere, G.Groeseneken



T.Nakaie, M.Sawada, T.Hasebe



A.Concannon, V.Vashchenko, M.ter Beek

Outline of Presentation

- **Introduction**
- **Key performance parameters**
- **Diode protection with Power Clamp**
- **Inductor protection with Power Clamp**
- **Full circuit – ESD co-design**
- **Partial circuit – ESD co-design**
- **Conclusions**

Introduction: RF circuit design

Integrated RF front-ends @ 5.5 GHz

- 90nm CMOS technology
- BiCMOS technology

Typical design for performance:


- Large gain
- Low noise
- Linearity
- But **ESD protection** is often overlooked

Introduction: RF circuit design

Common issues of ESD protection:

- Extra input capacitance
 - Gain reduction
 - Noise increase
 - ...
- Comparison of advantages and disadvantages of several ESD protection strategies

Introduction: ESD protection

 

- Diode protection with power clamp
- Inductor protection with power clamp
- Distributed protection
- Resonant and cancellation
- Co-design

Key performance parameters

Performance figure	Target Value (@ f_c)
f_c	5.5 GHz
S11	< -10 dB
S22	< -10 dB
S21	> 15 dB
S12	< -30 dB
NF	< 3 dB
IIP3	As high as possible
Ptot	As low as possible
Area	As small as possible
ESD protection level	> 2 kV HBM

Key performance parameters

- **Low-power RF Figure-Of-Merit**

$$FOM_1[mW^{-1}] = \frac{Gain[abs]}{(NF[abs] - 1) \cdot P_{DC}[mW]}$$


- **Brederlow's RF Figure-Of-Merit**

$$FOM_2[GHz] = \frac{Gain[abs] \cdot IIP3[mW] \cdot f_c[GHz]}{(NF[abs] - 1) \cdot P_{DC}[mW]}$$

Diode protection with Power Clamp

BiCMOS LNA


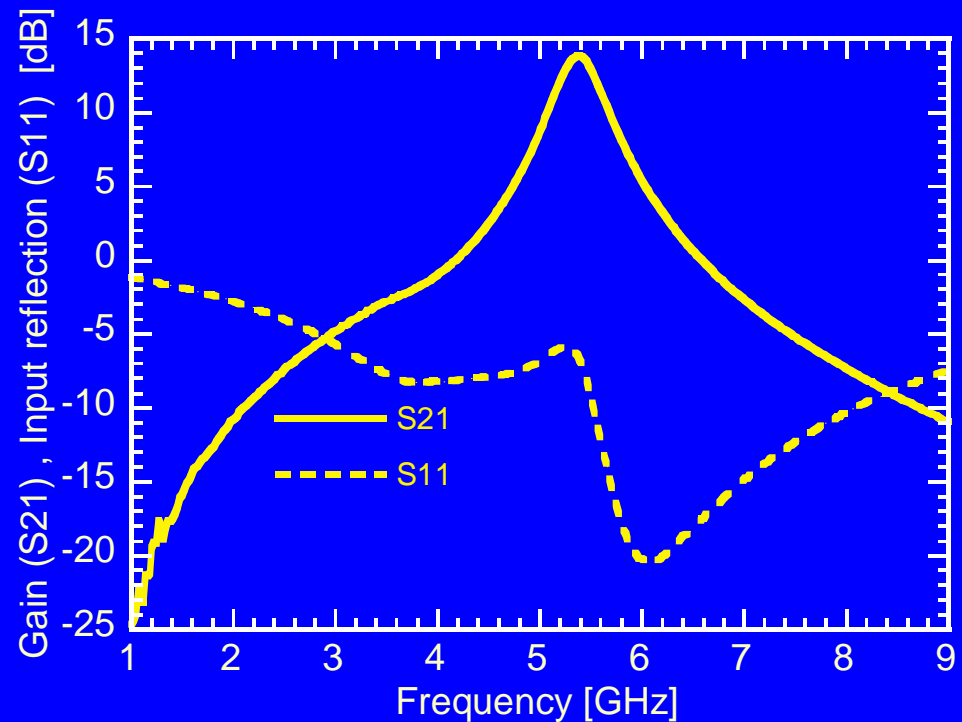
- $F_c = 5.5$ GHz
- Pn and Np diodes of $71\mu\text{m}^2$ ($\sim 100\text{fF}$)
- S21 reduction
- NF: +0.4 dB
- FOM₂ increase
- 50V \rightarrow 3kV HBM




Diode protection with Power Clamp

90nm CMOS LNA

 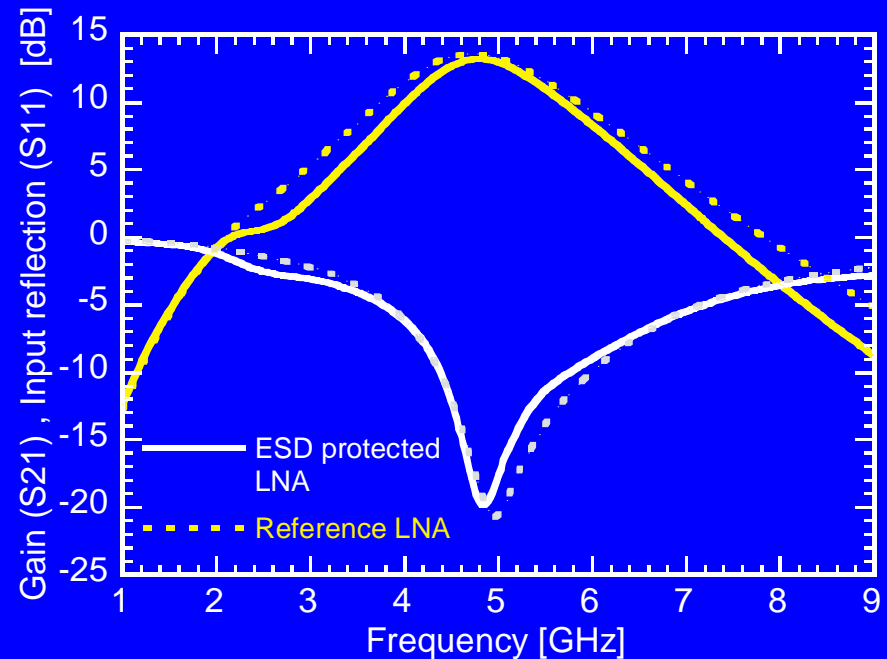- $F_c = 5$ GHz
- Pn and Np diodes of $65\mu\text{m}^2$ ($\sim 100\text{fF}$)
- S21 reduction
- NF: +0.6 dB
- FOM₂ increase
- <50V -> 500V HBM
- Insufficient: Why ?



Diode protection with Power Clamp

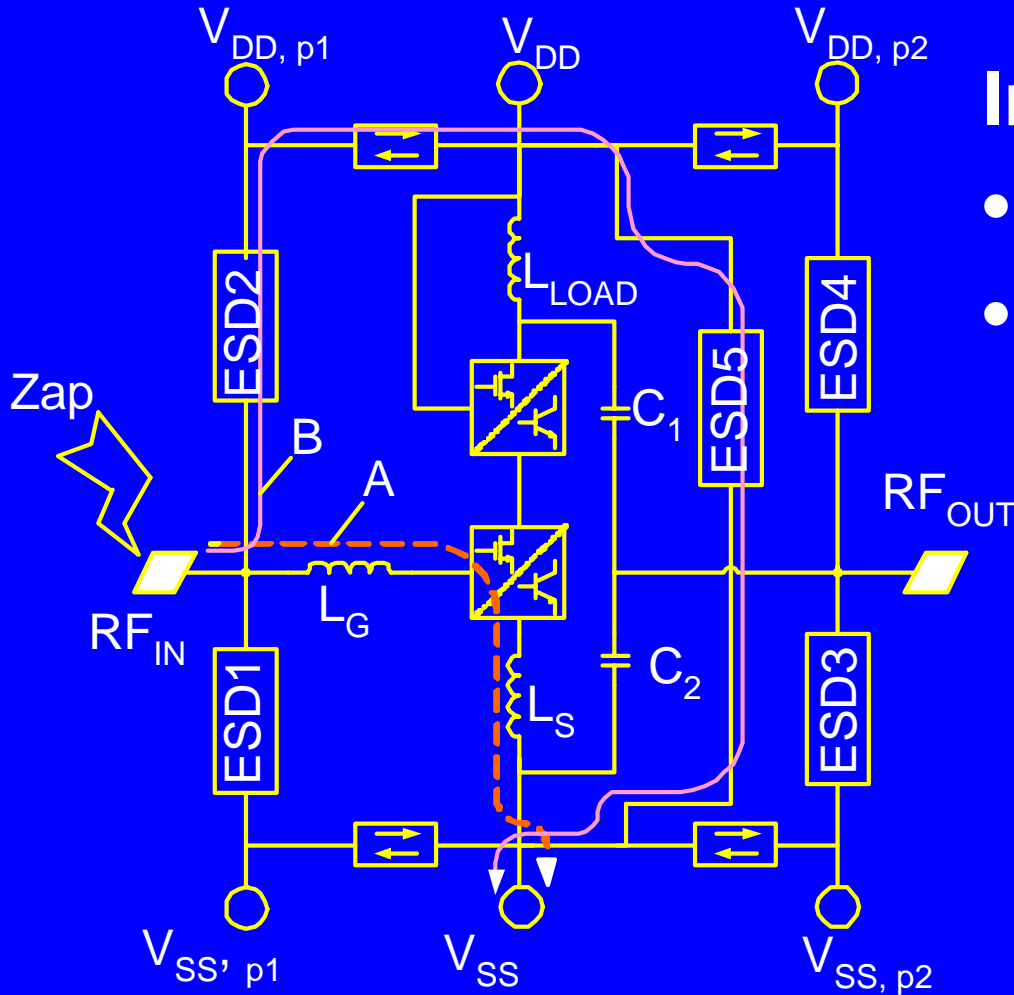

Insufficient protection

- ESD current path B
- Parasitic current path A

Diode protection with Power Clamp


Insufficient protection:

- **BiCMOS LNA: parasitic ESD current flows through L_G , emitter diode and L_S to ground**
- **90nm CMOS LNA: parasitic ESD current loads gate capacitor and builds up over-voltage**

Solutions:

- **On-chip capacitor**
- **Series resistor**

Inductor protection with Power Clamp

 

Inductor protection with Power Clamp


Addition of inductor as “plug-n-play”

- Diverts ESD current to ground
- Is transparent for the RF signal


Inductor selection:

- S11 input **matching**
- **Over-voltage** at the gate during ESD
- Parasitic **resistance** of the inductor during ESD and in RF operation



Inductor protection with Power Clamp

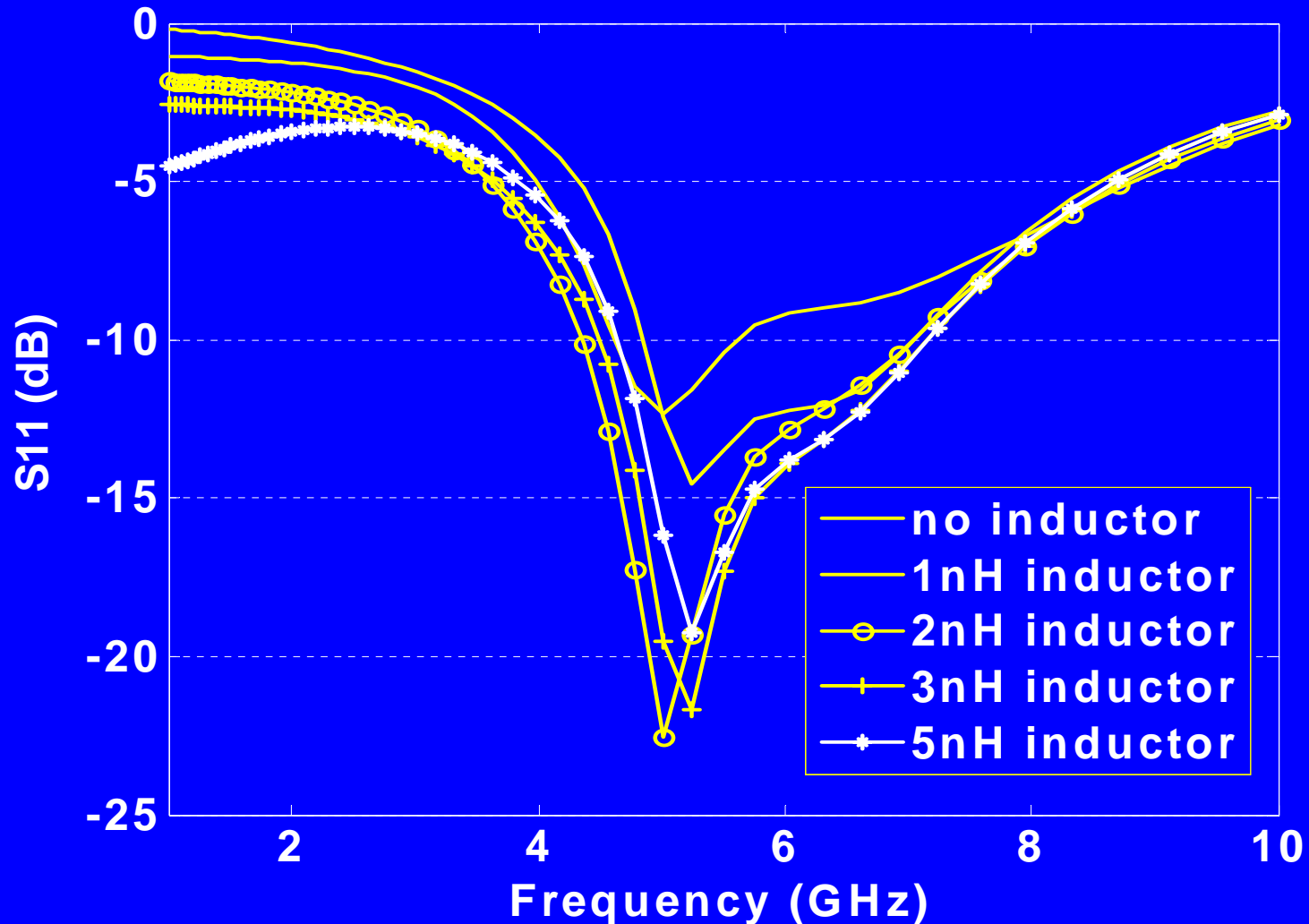

Inductor protection with Power Clamp


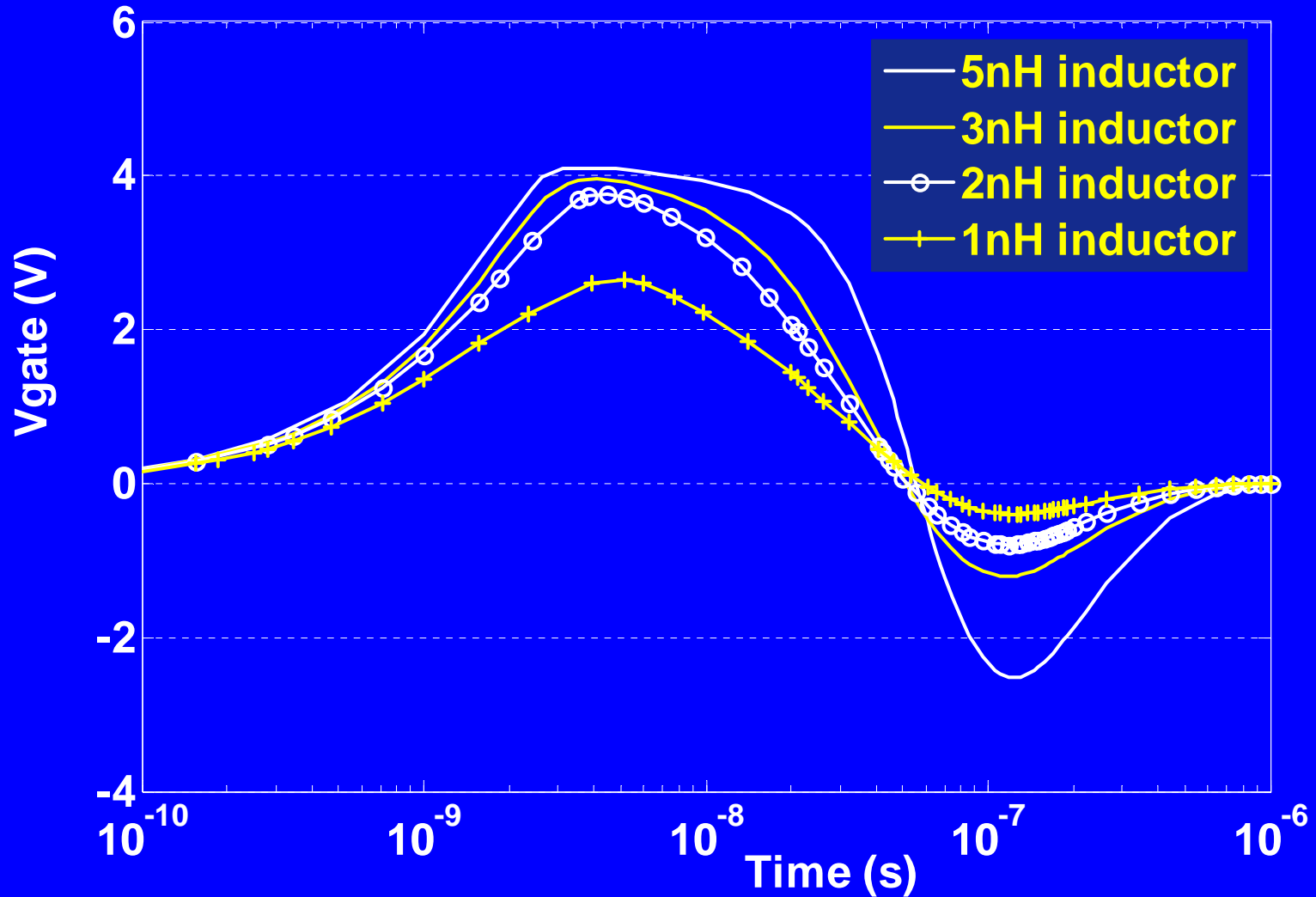


Inductor protection with Power Clamp

  

Inductor protection with Power Clamp

- Measurement results

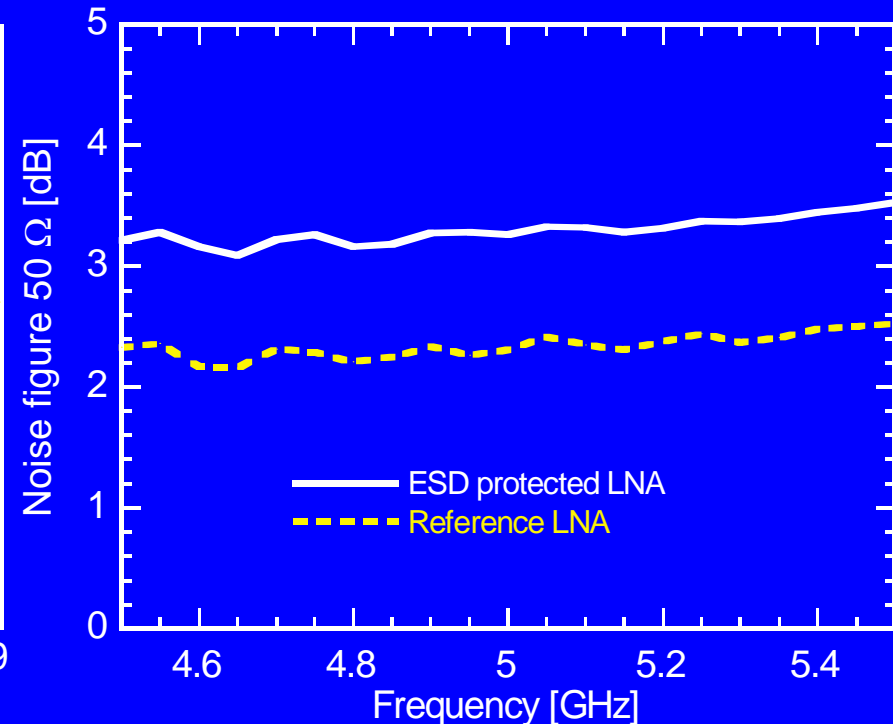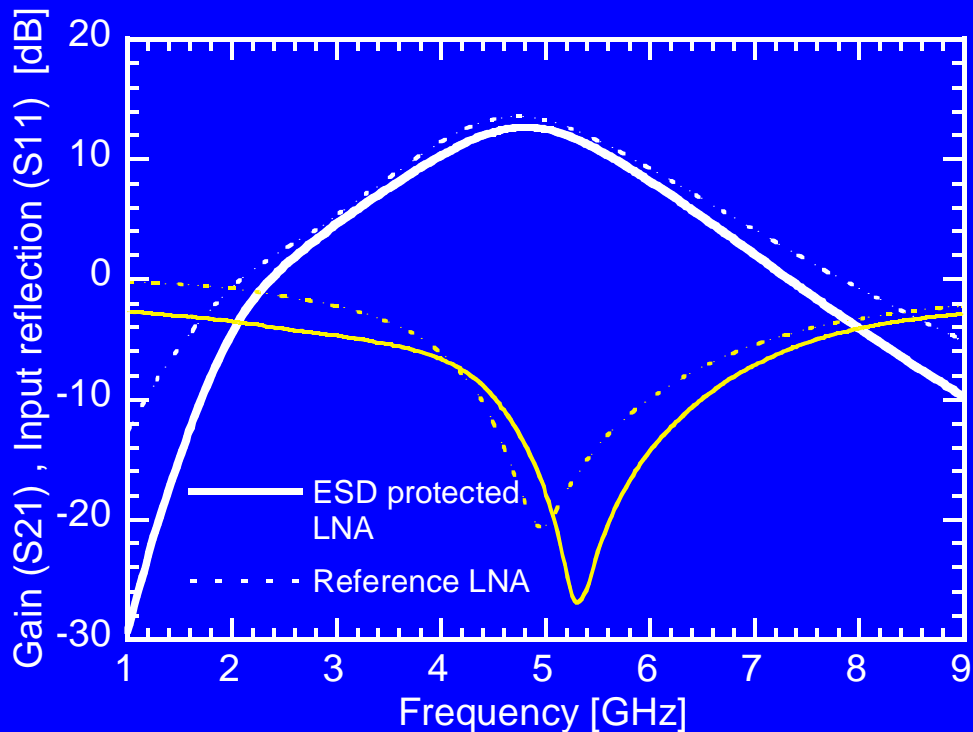


Inductor protection with Power Clamp

Gate over-voltage protection

- Add a minimum size **reverse diode** at the gate to block **negative** over-voltage
- Add two minimum size **forward diodes** at the gate, biased at 0.6V to block **positive** over-voltage

These diodes are placed right in front of the gate

Inductor protection with Power Clamp

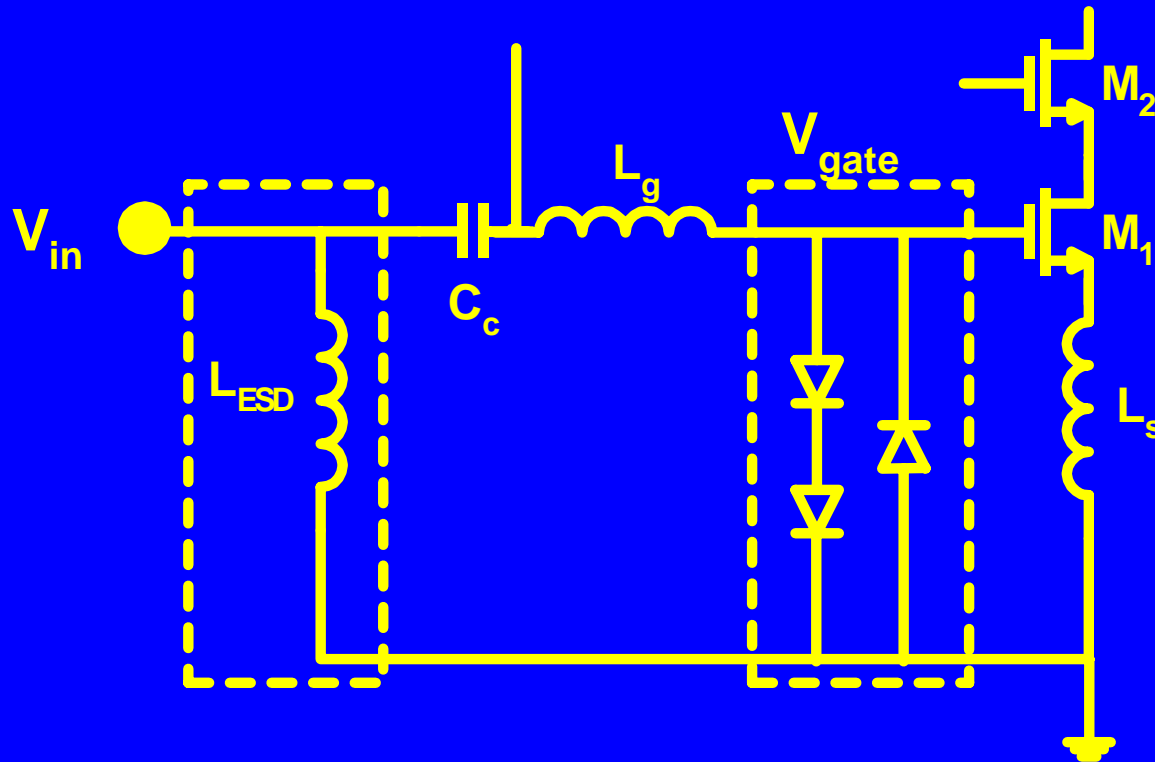



Schematic with additional diodes to clamp the voltage at M1

Inductor protection with Power Clamp

Circuit	LNA	ESD-LNA	ESD-LNA
	no ESD	w/o diodes	with diodes
Vdd [Volt]	1.2	1.2	1.2
Current [mA]	7.5	7.5	7.5
Gain [dB]	13.5	12.6	12
S11 [dB]	-21	-18	-24
S22 [dB]	-11	-14	-14
S12 [dB]	-31	-32	-32
NF [dB]	2.2	3.2	3.4
1dB CP [dBm]	-11.5	-10.5	-9.6
IIP3 [dBm]	-1	-0.5	0.4
TLP [A]	-	2.2	4
HBM [kV]	0.009	2.5	5.5
MM [V]	-	225	350


Inductor protection with Power Clamp

- Measurement results

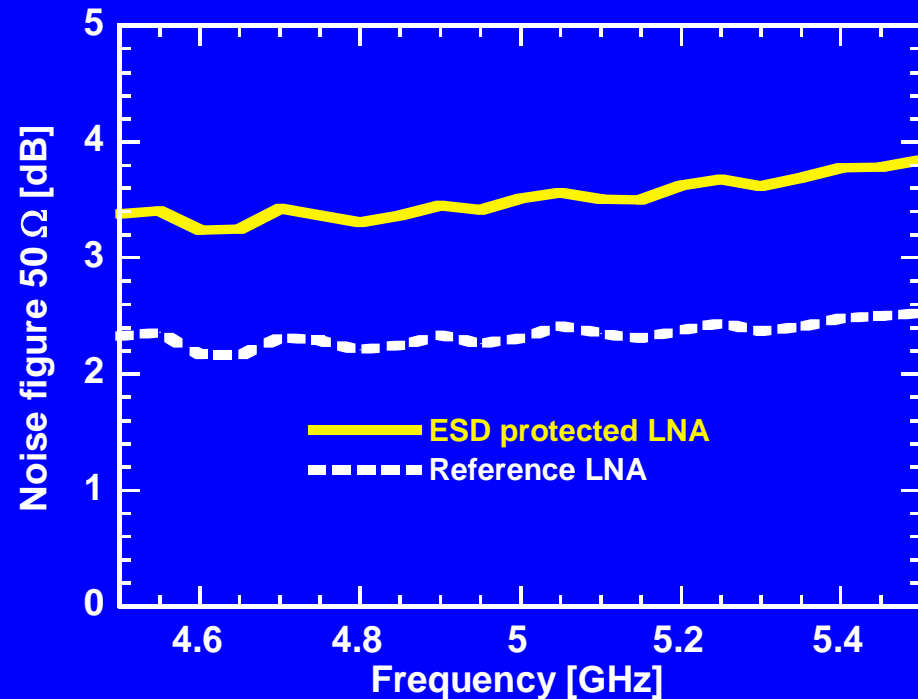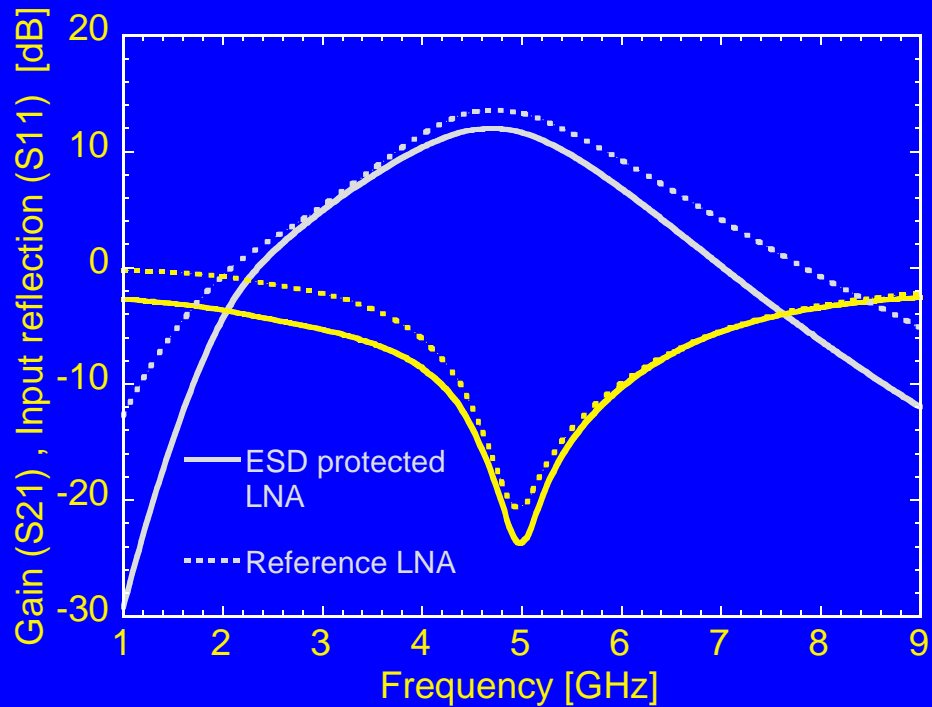


Full circuit – ESD co-design

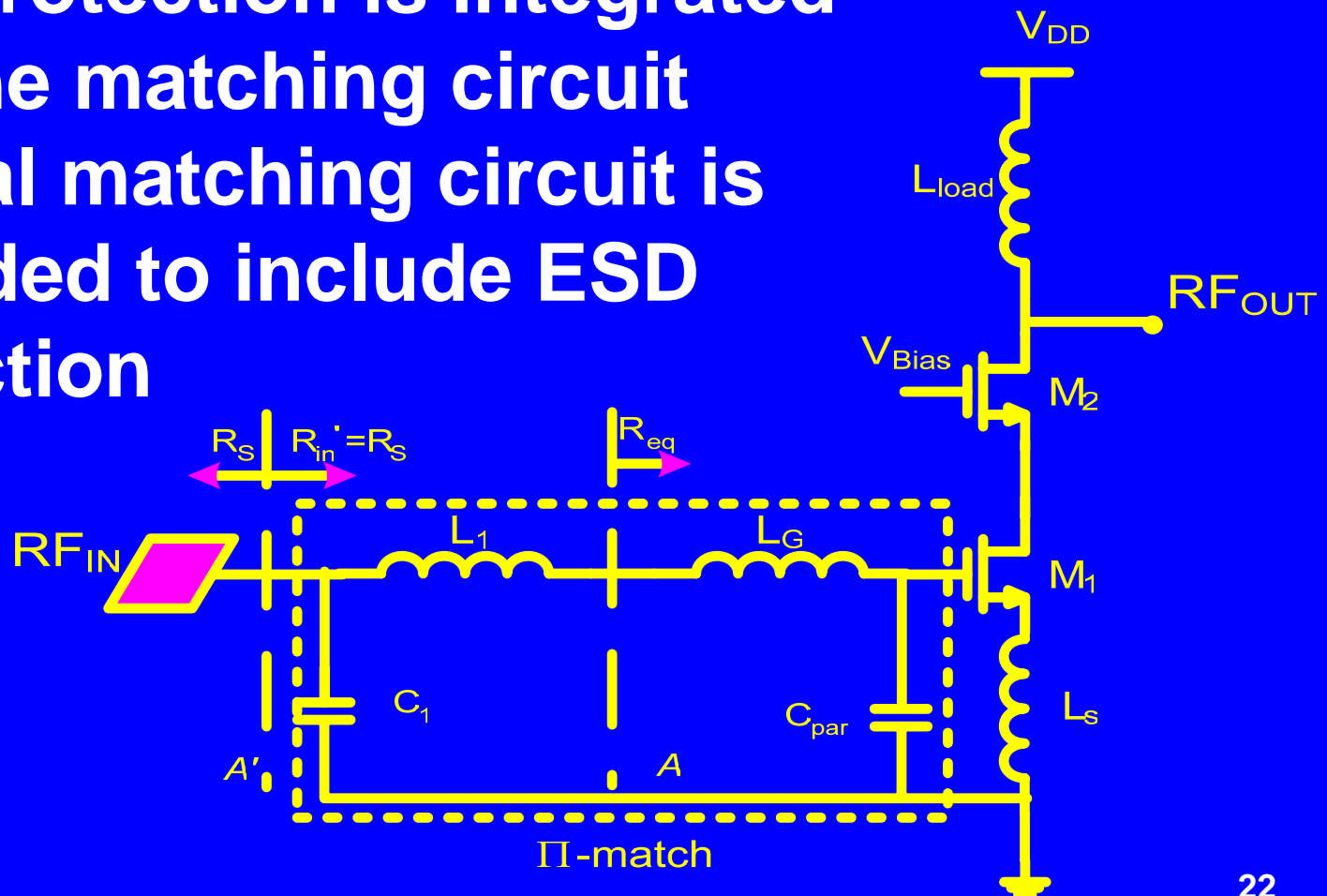- ESD protection is integrated into the matching circuit
- Typical matching circuit is extended to include ESD protection



Full circuit – ESD co-design

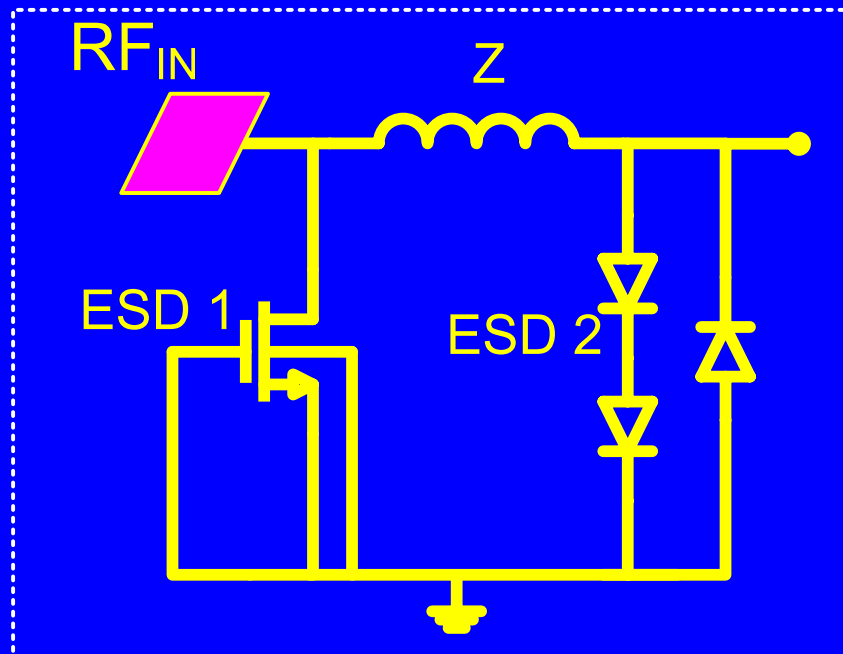



Schematic including the ESD protection into the matching circuit

Full circuit – ESD co-design

Circuit	LNA no ESD	ESD-LNA Co-design
Vdd [Volt]	1.2	1.2
Current [mA]	7.5	7.5
Gain [dB]	13.5	16.2
S11 [dB]	-21	-11.5
S22 [dB]	-11	-8
S12 [dB]	-31	-25.4
NF [dB]	2.2	3.5
1dB CP [dBm]	-11.5	-15.4
IIP3 [dBm]	-1	-5
HBM [kV]	0.009	1.9

Full circuit – ESD co-design

- Measurement results

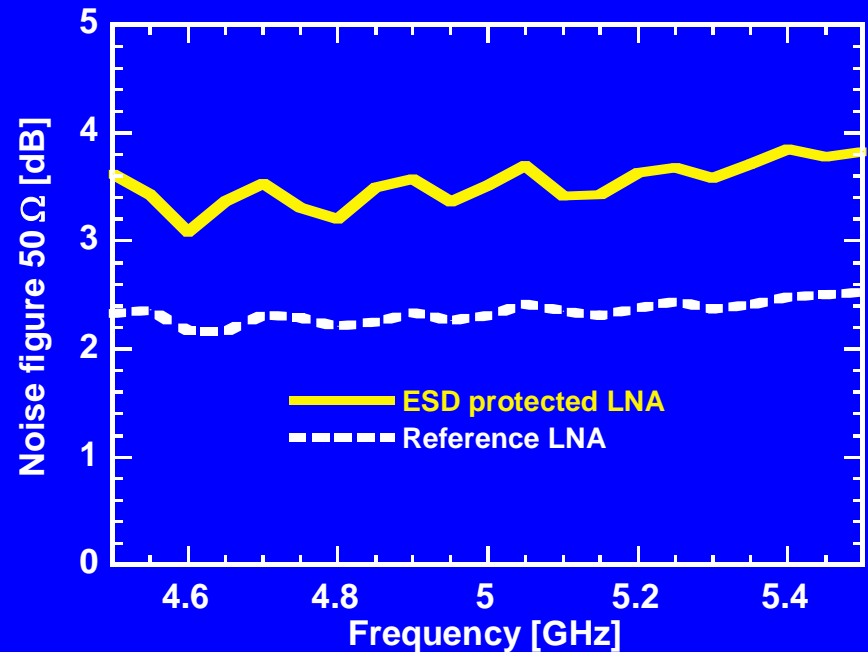 


Partial circuit – ESD co-design

- Determine **parasitic loading** due to the ESD protection and other parasitics
- Take this value into account for input/output **matching**

Opposite to previous methods


- Determine ESD robustness
- Optimize LNA for this robustness

Partial circuit – ESD co-design

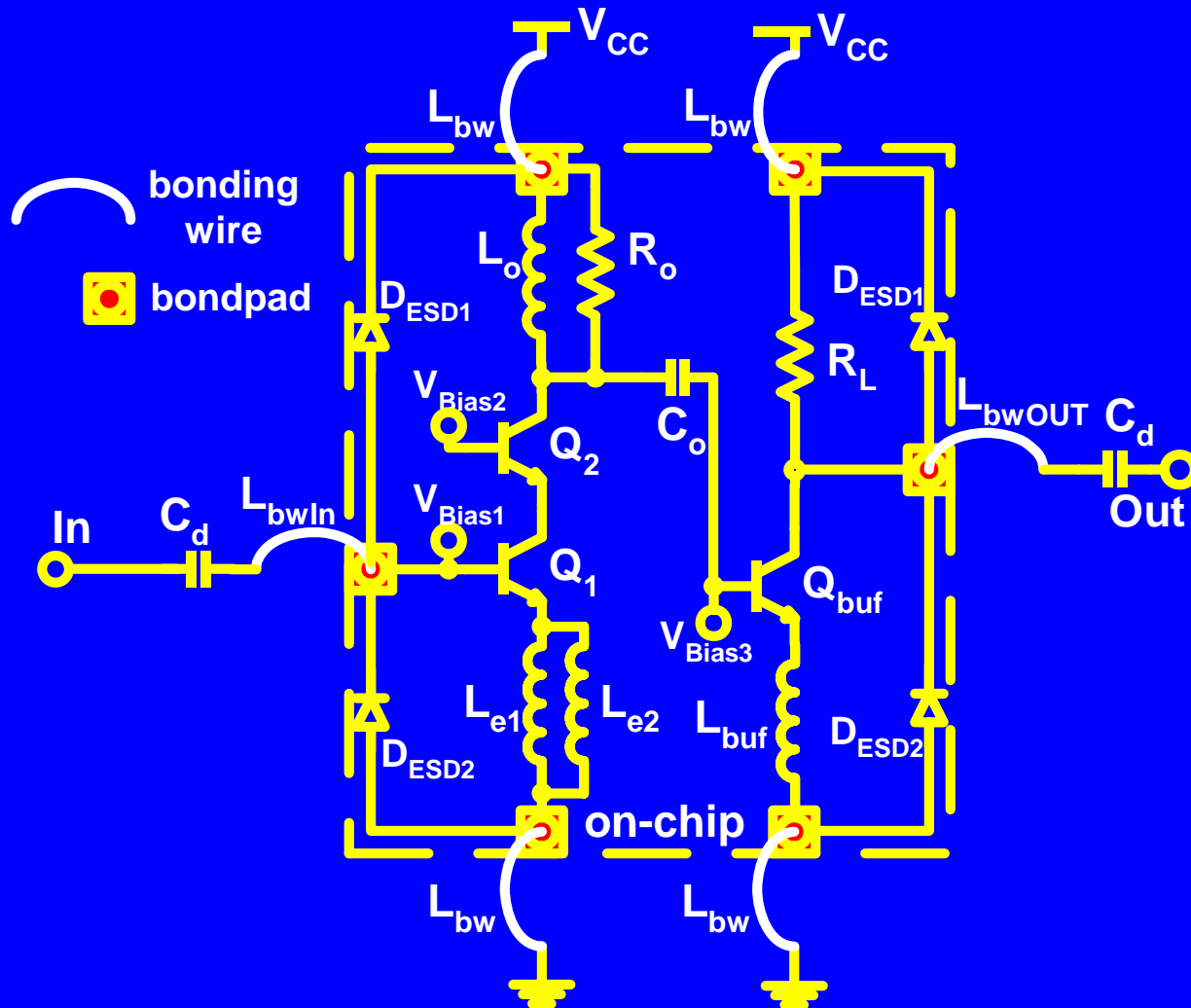

Partial circuit – ESD co-design

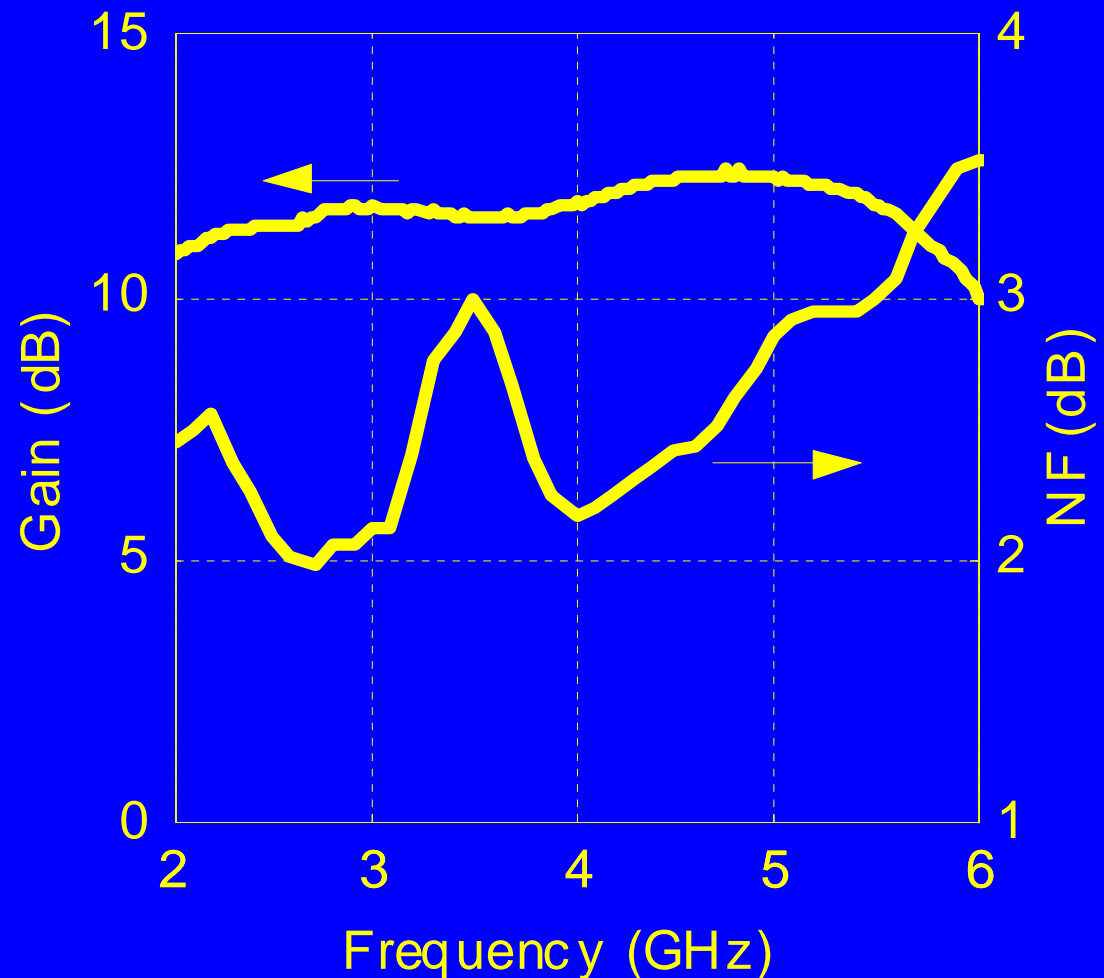- Measurement results for an ultra wideband LNA in 0.35 μm BiCMOS technology



Conclusions

- **Comparison of 4 RF ESD protection strategies with respect to their respective performance trade-offs**
- **Discussion of the limiting factors and proposal of solutions for further improvement**
- **Review of the performance parameters for 90nm CMOS LNA's at 5 GHz**

Conclusions

Circuit	LNA	LNA diodes	ESD-LNA inductor w/o diodes	ESD-LNA inductor with diodes	ESD-LNA co-design
Vdd [V]	1.2	1.2	1.2	1.2	1.2
Current [mA]	7.5	7.5	7.5	7.5	7.5
Gain [dB]	13.5	13	12.6	12	16.2
S11 [dB]	-21	-18	-18	-24	-11.5
S22 [dB]	-11	-14.5	-14	-14	-8
S12 [dB]	-31	-30	-32	-32	-25.4
NF [dB]	2.2	3	3.2	3.4	3.5
1dB CP [dBm]	-11.5	-10.6	-10.5	-9.6	-15.4
IIP3 [dBm]	-1	-0.4	-0.5	0.4	-5
TLP [A]	-	-	2.2	4	-
HBM [kV]	0.009	0.5	2.5	5.5	1.9
MM [V]	-	-	225	350	-