# The Technology Behind the World's Smallest 12V, 10A Voltage Regulator

A low profile voltage regulator achieving high power density and performance using a hybrid dc-dc converter topology

Pradeep Shenoy, Ph.D.

Systems Engineer, DC Solutions



## **Power Delivery System**



#### Intermediate Bus Architecture



# Why Increase Switching Frequency?

Inductors are usually the largest component.



## 1) Smaller size



![](_page_2_Picture_5.jpeg)

Converter Volume: 1,270 mm<sup>3</sup>

Inductor Volume: 232 mm<sup>3</sup> *<* 

Converter Volume: 157 mm<sup>3</sup>

Inductor Volume: 19.2 mm<sup>3</sup>

# 2) Faster Response

# 3) Lower BOM Cost

![](_page_2_Picture_12.jpeg)

# **Current Density Comparison**

![](_page_3_Figure_1.jpeg)

![](_page_3_Figure_2.jpeg)

Conventional Buck: 4.8 mm height

#### Current density of over 60A/cm<sup>3</sup> and power density of 1.25kW/in<sup>3</sup>

![](_page_3_Picture_5.jpeg)

#### **Inductor Size Reduction: 10A Output**

![](_page_4_Figure_1.jpeg)

High frequency operation  $\rightarrow$  15 times smaller inductors!

![](_page_4_Picture_3.jpeg)

### Agenda

- High Frequency Buck Converter
  Limitations
- Series Capacitor Buck Converter
- Sample Experimental Results
- Design Considerations for a Series Cap Buck Converter

Series cap buck converter prototype

![](_page_5_Picture_6.jpeg)

![](_page_5_Picture_7.jpeg)

# High Freq (HF) Buck Converter Limitations

![](_page_6_Figure_1.jpeg)

• High switching loss

$$P_{loss} \propto f_{sw}$$

- High side switch on-time is very short at HF
  - 5 MHz  $\rightarrow$  200ns period
  - 10-to-1 voltage ratio → 20ns high side on-time

#### HF converters on the market today have low conversion ratios (<5-to-1) and low current (<1A)

![](_page_6_Picture_8.jpeg)

# **Series Capacitor Buck Topology**

![](_page_7_Figure_1.jpeg)

Two-phase, series cap buck converter

- ✓Benefits
  - ✓ Single conversion stage
  - ✓ Switching at reduced V<sub>ds</sub>
  - ✓ Series cap soft charge/discharge
  - Automatic current balancing
  - ✓ Duty ratio doubled
- Drawback
  - 50% duty cycle limitation
    - Theoretical:  $V_{IN,MIN} = 4 \times V_{OUT}$
    - Practical:  $V_{IN,MIN} = 5 \times V_{OUT}$

P. S. Shenoy, M. Amaro, J. Morroni and D. Freeman, "Comparison of a Buck Converter and a Series Capacitor Buck Converter for High-Frequency, High-Conversion-Ratio Voltage Regulators," *IEEE Trans. Power Electron.*, vol. 31, no. 10, pp. 7006-7015, Oct. 2016.

![](_page_7_Picture_14.jpeg)

Inductor & series cap currents  $C_t V_{swa} L_a$  $Q_{1a}$ Lb Current (A) Vo  $Q_{2\epsilon}$ Ct 0  $V_{swb}$ L<sub>b</sub>  $Q_{1b}$ -2  $Q_{2b}$ 0.2 0.4 0.6 0 Time (µs) Series cap voltage (differential) Switch node voltages 6.2 V<sub>Ct</sub> 8 6.15 Voltage (V) Voltage (V) 6.1 6.05 5.95 SWA ......V<sub>SWB</sub> 5.9<sup>∟</sup> 0 -2<sub>0</sub> 0.2 0.4 0.6 0.2 0.4 0.6 Time (µs) Time (µs)

#### **Steady-State Operation: Interval 1**

**TEXAS INSTRUMENTS** 

![](_page_9_Figure_0.jpeg)

Steady-State Operation: Interval 2<sub>Inductor & series cap currents</sub>

10 of 30

🤴 Texas Instruments

![](_page_10_Figure_0.jpeg)

# Steady-State Operation: Interval 3<sub>Inductor & series cap currents</sub>

Texas Instruments

![](_page_11_Figure_0.jpeg)

# Steady-State Operation: Interval 4 Inductor & series cap currents

i, **TEXAS INSTRUMENTS** 

# **Reduced Switching Loss**

- Reduced switch voltage/current overlap loss
- Loss due to switch output capacitance reduced by 67%
- Enables higher frequency operation

#### Energy loss per switching cycle

![](_page_12_Figure_5.jpeg)

![](_page_12_Picture_6.jpeg)

# **Measured Efficiency Comparison**

![](_page_13_Figure_1.jpeg)

- Conditions:
  - 12V in, 1.2V out
  - Room temp, no air flow
- Higher efficiency over the load range
- Inductors selected for equivalent DCR

Higher peak efficiency at ~4 times the switching frequency

![](_page_13_Picture_8.jpeg)

# **Auto Current Sharing**

- Series cap forms average current feedback mechanism
  - Inductors charge/discharge cap
  - Charge balance maintained
- Robust to variations in L, DCR

![](_page_14_Figure_5.jpeg)

#### Current Sharing: La ≈ 100nH, Lb ≈ 200nH

![](_page_14_Figure_7.jpeg)

P.S. Shenoy, et al., "Automatic current sharing mechanism in the series capacitor buck converter," in *Proc. IEEE Energy Conversion Conf. Expo.*, Sept. 2015.

![](_page_14_Picture_9.jpeg)

# **High Frequency Controller**

![](_page_15_Figure_1.jpeg)

- Adaptive constant on-time control
  - Fast transient response
  - Internal compensation
- Frequency synchronization by adapting on-time
  - Fixed frequency in steady state
  - Can use external clock or internal oscillator

![](_page_15_Picture_8.jpeg)

### **Reference Design PMP15008**

"Tiny, Low Profile 10 A Point-of-load Voltage Regulator"

![](_page_16_Figure_2.jpeg)

#### **Board Image**

![](_page_16_Picture_4.jpeg)

#### Total solution size is 135mm<sup>2</sup> and 1.25mm tall

![](_page_16_Picture_6.jpeg)

#### **Efficiency and Power Loss**

2 MHz per phase,  $1.2V_{OUT}$ , room temperature, no air flow, two layer board

![](_page_17_Figure_2.jpeg)

Over 90% efficiency at 9V input, less than 3W loss at full load

![](_page_17_Picture_4.jpeg)

### **Thermal Image**

![](_page_18_Figure_1.jpeg)

#### Less than 35 deg. C temp rise at 12V input, 8A output

![](_page_18_Picture_3.jpeg)

## **Load Transient Response**

![](_page_19_Figure_1.jpeg)

#### 2% variation in V<sub>OUT</sub> during 5A load change

![](_page_19_Picture_3.jpeg)

## **High Bandwidth and Ample Phase Margin**

![](_page_20_Figure_1.jpeg)

Bode plot taken with 12V input, 5A output

![](_page_20_Picture_3.jpeg)

## **Inductance Impact on Efficiency**

Inductance equation

![](_page_21_Figure_2.jpeg)

- $K = \Delta I_L / I_L$  where  $I_L$  is current at full load
- K is usually between 0.1 and 0.4

![](_page_21_Figure_5.jpeg)

![](_page_21_Figure_6.jpeg)

- Higher inductance tends to increase
  <u>peak efficiency</u>
- Lower inductance has higher <u>full load</u>
  <u>efficiency</u>

![](_page_21_Picture_9.jpeg)

### **Inductor Size**

- Larger inductors tend to result in higher efficiency
  - Thicker wire
  - Lower winding resistance
  - Benefit seen in mid to high load current range
- Measured results for
  - Same inductance
  - Same vendor
  - Same core material

![](_page_22_Figure_9.jpeg)

![](_page_22_Figure_10.jpeg)

![](_page_22_Picture_11.jpeg)

### **Inductor Vendor**

- Finding the right inductor vendor matters
  - Various core material, construction, etc.
  - Should not judge an inductor by DC resistance alone
- Measured results for
  - Same inductance
  - Same size
- If possible, experimentally test inductors

12  $V_{\text{IN}},$  1.2  $V_{\text{O}}$  , 2MHz/phase

![](_page_23_Figure_9.jpeg)

![](_page_23_Picture_10.jpeg)

## **Series Capacitor Selection**

![](_page_24_Figure_1.jpeg)

![](_page_24_Picture_2.jpeg)

# **DC Voltage and Temp Impact on Capacitance**

- Capacitance varies with temperature
- Capacitance decreases with DC voltage
- Examine capacitance at V<sub>IN</sub>/2

![](_page_25_Figure_4.jpeg)

Select a capacitor taking capacitance variation into account

![](_page_25_Picture_6.jpeg)

# **Series Capacitor Self Heating**

![](_page_26_Figure_1.jpeg)

- Ensure series cap temperature stays within limits
  - Calculate RMS current
  - Check datasheet/online tools

Ex: 10.8V<sub>IN,MIN</sub>, 1.2V<sub>O</sub>, I<sub>L,RMS</sub> = 5.02A  
$$I_{SCAP,RMS} = \sqrt{2 \left(\frac{2V_O}{V_{IN,MIN}}\right)} I_{L,RMS}^2 = 3.34A$$

- 2.2µF cap, 1206 (3.2 x 1.6 x 1.15mm)
- Result: **15.8°C temp rise**
- X7R capacitors with 125°C operating temperature rating recommended

### **Total Solution Size**

![](_page_27_Figure_1.jpeg)

The total solution size is 65% smaller in volume than just the inductor on a competitor's 10A evaluation module!

![](_page_27_Picture_3.jpeg)

### **SUMMARY**

- High frequency (HF) operation of switching converters enables size reduction and performance improvements
- Buck converters have fundamental limitations that limit HF operation
- The series capacitor buck converter has unique properties that support HF operation
- Design recommendations for an HF series cap buck converter demonstrate the ease of implementation

![](_page_28_Picture_5.jpeg)

### **Additional Resources**

![](_page_29_Figure_1.jpeg)

- View the <u>TPS54A20 product</u> page.
- View the reference design "<u>Tiny</u>, <u>Low Profile 10A Point-of-load</u> <u>Voltage Regulator</u>."
- Download the application note <u>"Introduction to the Series</u> <u>Capacitor Buck Converter</u>."
- Watch the video training series
  "<u>Designing with TI's Series</u>
  <u>Capacitor Buck Converter</u>."

![](_page_29_Picture_6.jpeg)