

Residential Battery Storage: The cornerstone of the Nanogrid and distributed power systems

Antonio Ginart Santa Clara, California

Power System Centralized vs. Distributed



EEE

IICS SOCIET



Distributed Paradigm Shift - Renewables

Disadvantages

- □ More complex technologies
- □ More expensive in many cases
- Less centralized control
- Potential for a less reliable grid
- Need of new technology and regulations
- Potential for greater power quality issues





Advantages

- □ Potential for better local resource use
- Consumers have greater independence
- □Environmentally friendlier
- Potential for a more robust and reliable grid (non-single collapse point)

 - □Natural disaster
- Potential for more economically sound macro-analysis

Minimum-cost of Electrification Electrification Model (REM)



400,000 non-electrified buildings in the Vaishali district of Bihar, India.



Grid extension (low-voltage lines)
 Stand alone system (Nanogrid)
 Microgrid



MIT News (January 2016)



Nanogrid Operation Mode





Power Quality Issues (Back up Mode)



Line voltages under A/C 5 TON system start up

		¹ /2 cycle 8.3ms	1 cycle 16.6ms	3600 cycles 60 s	>3600 cycles > 60 s
1	Transients				
2	Sag and swell				
3	Noise				
4	Harmonics				
5	Under and over Voltages				

The standard IEEE 1100

- Short term voltage variations (sag ,swell, and transients)
- Long term voltage variations (over and under voltages, harmonics and noise)

Residential Nanogrid DC-AC



- 12V- 400V
- Advantages
 - More efficient
 - Easy control, stable
- Disadvantages
 - Large investment required
 - Difficult interruption (protection, fire)

AC Nanogrid

- Advantages
 - Required no additional investment
 - Easy retrofit
- Disadvantages
 - Control and stability are more difficult
 - Region dependent
 - 200-230V 50Hz
 - 120/240V 60 Hz US

Basic DC and AC Nanogrids: Solar and Energy Storage

DC Nanogrid



IEEE POWER ELECTRONICS SOCIETY Powering a Sustainable Future

AC Nanogrid



DC Residential Nanogrid





DC Residential Nanogrid- Control







AC Residential Nanogrid





Control

Droop ControlVoltages and Frequency

Load Handling and Criticality





Residential Load



Droop AC control (Inverter)





The Bode plots of the output impedance of Inverters L-inverter (with L = 7 mH, $R = 0.1 \mathbf{Q}$, and $C_o = 0 \mu \text{F}$) R-inverter (with L = 7 mH, $R = 8\mathbf{Q}$, and $Co = 0 \mu \text{F}$) C-inverter (with L = 7 mH, $R = 0.1 \mathbf{Q}$, and $Co = 161 \mu \text{F}$).



Droop AC control





 $P = \left(\frac{EV_o}{Z_o}\cos\delta - \frac{V_o^2}{Z_o}\right)\cos\theta + \frac{EV_o}{Z_o}\sin\delta\sin\theta,$ $Q = \left(\frac{EV_o}{Z_o}\cos\delta - \frac{V_o^2}{Z_o}\right)\sin\theta - \frac{EV_o}{Z_o}\sin\delta\cos\theta.$ Assuming $\delta \sim 0$ and Inductive $\frac{\pi}{2}$ $P \sim \frac{EV_0}{Z_0} \delta \qquad Q \sim \frac{EV_0}{Z_0} - \frac{V_0^2}{Z_0}$ $P \sim \delta$ $Q \sim E$



Universal Droop Control of Inverters

 v_r

Droop controllers for L-, R-, C-, RL-, and RC-inverters.

Inverter type	θ	Input-output/Droop relationship	Droop controller	
Т	$\frac{\pi}{2}$	$P \sim \delta$	$E = E^* - nQ$	
L-		$Q \sim E$	$\omega = \omega^* - mP$	
р	0°	$P \sim E$	$E = E^* - nP$	
K-		$Q\sim-\delta$	$\omega = \omega^* + mQ$	
C	$-\frac{\pi}{2}$	$P \sim -\delta$	$E = E^* + nQ$	
C-		$Q \sim -E$	$\omega = \omega^* + mP$	
R _C -	$(-\frac{\pi}{2},0)$	Coupled	Depends on θ	
R _L -	$(0, \frac{\pi}{2})$	Coupled	Depends on θ	









Fundamentals Back up battery storage



Energy Storage (Why Battery & Capacitor?

Air CompressorHydraulics

Thermal (Molten Salt)

Inertia Wheels

Magnetics

Capacitor (Super)

Battery

General Flow Batteries



Dynamic Power Compensation (very fast – few milliseconds)

□Sized according its nanogrid

Able to regulate the nanogrid

UWeather prediction via internet







Fast Energy Storage





Batteries: State-of-the-Art

- Lead Acid
- Nickel–Cadmium
- Lithium-ion
 - Lithium cobalt oxide LiCoO2 (metal oxide)
 - Lithium manganese oxide LiMn2O4 (tunneled structure)
 - Lithium iron-phosphate LiFePO4 (olivine structure)







IOXUS super capacitor



2.70V Cylindrical cells (-40°C to +85°C)						
2.85V Cylindrical cells (-40°C to +65°C) 2.70V Pouch cells (-20°C to +65°C)						 High energy density High power density Low ESR
Cylindrical	100F	385F	1250F	2000F	3000F	 1M cycles Multiple patents
Pouch	160F 210F	445F	600F	1245F	1600F	



Batteries

- Basic structure
 - Battery cell
 - Cell arrangements
 - Balancing circuits
- Modeling
- Life and modeling
 - Cycles
 - Current dependence
 - Temperature dependence

- Positive electrode
- Negative electrode (carbon-graphite)
- Electrolyte and separator





Modeling

10¹

(a)

Frequency (Hz)

10⁰

10²

10³

10-2

10-2

10-1



75

100

10-2

r r r r nul

10-1

10⁰

a roud

Frequency (Hz)

10¹

(b)

10²

a cond

10³

T I I I IIII

10⁴

1.1.1111

10⁵

T TITUL T TITU

10⁵

10⁴



Life Model- Charge capacitace

Capacity loss as a function of charge and discharge bandwidth.





https://www.nrel.gov/docs/fy13osti/58550.pdf

Nissan Leaf case



both electrodes

500

140

120

Life model _Impedance Real Part and Aging





Battery dimensioning Charge and discharge



Solar – storage relation



Peak demand (other aspect)



Battery Spec Temperature Charge and Discharge





$$OC = \int_{V_1}^{V_2} I(t) dt$$



DC/AC





Battery Specs Temperature Charge and Discharge Energy storage





Energy and Power Arrangement

3 ampere-hours, 3.2 V 14x16

Energy = kW/h

Power= kW





Battery system in a nanogrid go from 4kw/h to 16 kW/h



Inverters Fundamentals

Solar Inverter Evolution





98

97

* Kouro, S. Leon, J.I.; Vinnikov, D.; Franquelo, L.G. "Grid-Connected Photovoltaic Systems: An Overview of Recent Research and Emerging PV Converter Technology" Industrial Electronics Magazine, IEEE Volume:9, Issue: 1 P:47 - 61 March 2015 32

IEEE

RONICS SOCIETY

a Sustainable Future

DWER

Average weight

3-4

4-5

PV Inverter with DC Power<6.5kW

-Transformerless

-HF-Transformer





Bi-directional Inverter (Voltages based)

- Inverter Topology Type (Basic topologies and their advantages and disadvantages)
- Inverter Connection Type
 - Low-frequency transformer:
- The basic structure consists of one or more H-bridges Single H-bridge, high PWM
 - Center tap
 - Multiple H-bridges with interleaving
- The course contains some design examples.
 - High-frequency transformer
- The isolation is accomplished by high-frequency switching on the DC side using a highfrequency core, traditionally ferrite. Recent developments in low-cost and low-loss materials are challenging ferrite use.
 - Topology and Design examples, including inverter and magnetic parts
 - Use of new semiconductors GaN and SIC
 - Transformerless

Eliminating the transformer reduces cost and significantly improves efficiency. This course analyzes the topologies that can achieve transformerless operation

Voltages Based Bi-directional inverter Sustainable Future





Low Frequency Bi-directional inverter



 $V_{RMS} = 4.44 f B_{\text{max}} A.N$

Low Frequency Bi-directional inverter interleaving







HF Inverter _Hard Switch





High frequency ZCS



S1

t₁

t₂

t₃

(a)





Vicor solution





Xiaoyan Yu and Paul Yeaman, "A new high efficiency isolated bidirectional DC-DC converter for DC-bus and battery bank interface



Transformerless Design _Motivation

- Cost reduction with additional weight and size reduction
- Efficiency increase and low cost

Average Parameter Comparisons for PV Inverters up to 6.5kW



	Transformerless	<u>LF-</u> <u>Transformer</u>	HF- Transformer
Avg. Efficiency (%)	95.7	94.5	94.1
Avg. Power per Weight (kW/kg)	0.213	0.0753	0.168
Avg. Power per Volume (kW/m ³)	115.2	84.7	80.2



EXAMPLE OF TRANSFORMERLESS INVERTER



INVERTER DEVICE, ENERGY STORAGE SYSTEM AND METHOD OF CONTROLLING AN INVERTER DEVICE Publication number: 20170077836



With interleaving



7KW 2- Split phase system 240/120V



PRINCIPLE OF OPERATION 3-LEVEL



Reverse energy transfer







DC/DC basic operation





TRANSFORMERLESS OPERATION



nт

(b)

m



Ground current for 1uF total parasitic capacitance





Evaluation Ground Current UL 1741



UL 1741 Ground Fault Detection Specifications vs. Inverter DC Rating

Inverter DC Rating (kW)	Maximum Ground Fault Current (Amps)
0-25	1
25-50	2
50-100	3
100-250	4
>250	5

Note: kW = kilowatts





Current Based Bi-directional inverter





AC-link and bidirectional switches



SOFT SWITCHED HIGH FREQUENCY AC-LINK CONVERTER

ANAND KUMAR BALAKRISHNAN



Inverter tied-grid control



Generalized d,q control



POWER RELATION BETWEEN A BATTERY SYSTEM

$$P_{DC} = I_{DC} \cdot V_{DC} = \eta \cdot I_{RMS} \cdot V_{RMS} = P_{AC}$$

$$I_{DC}(t) = 2I_{DC} \sin^{2}(\omega t)$$

$$V_{DC}I_{DC} = V_{RMS} \sqrt{2} \sin(\omega t) I_{RMS} \sqrt{2} \sin(\omega t) \Rightarrow$$

$$V_{DC}I_{DC} = 2V_{RMS}I_{RMS} \sin^{2}(\omega t)$$

$$I_{DC} = \frac{1}{\pi} \int_{0}^{\pi} I_{p} \sin^{2}(\alpha) d\alpha = \frac{1}{2}I_{p}$$

$$I_{RMS} = \sqrt{\frac{1}{\pi}} \int_{0}^{\pi} I_{p}^{2} \sin^{4}(\alpha) d\alpha} = \frac{\sqrt{3}}{2\sqrt{2}}I_{p}$$





Inverter Control





Stand Alone





GUI





GUI and Weather Prediction





Energy Storage Prices

• 10,000 cycles and/or 10 years, 80% charge



http://eupd-research.com/



Nanogrid-Energy Storage: Why Now?

□ Renewables Intermittence (generate "the need")

□Price (large price reduction)

□ Regulation (zero export to the grid)

Tariffs (peak demand)

UWeather Prediction via Internet

Power grid reliability and safetySmart Grid

Technology Conversion To Availability and Affordability



Fault Diagnosis for Robust Inverter Power Drives

Power drives are used for induction motor control, uninterruptible power supplies, and in electrical vehicles. The increasing penetration of power drives makes their reliability, robustness, and early diagnosis a central point of attention especially in planning, designing, and financing. This book explores fault diagnosis of inverter drives to enable early diagnosis and robust design for efficient long life operation.

Fault Diagnosis for Robust Inverter Power Drives focuses on early diagnosis, prognosis, and intrinsic reliability of inverter power drives and their applications. Topics include material degradation, materials, semiconductors, inverter topologies, and early diagnosis as well as fault tolerant software strategies.

This work is highly relevant to researchers, power electronics professionals, and system designers in aerospace, hybrid and electrical cars, and power systems.

About the Editor

Antonio E. Ginart Antonio E. Ginart is principal R&D engineer at SmartWires. He serves as Affiliate Faculty Member of the College of Engineering of the University of Georgia and Adjunct professor at Kennesaw State University. He has over 30 years of experience in power electronics, inverter drives design and motors control which has led to over 70 publications and patents.







The Institution of Engineering and Technology

Fault Diagnosis for Robust Inverter Power Drives

Edited by Antonio Ginart



Thanks! Questions?