Switched-Capacitor Converters: Big & Small

Michael Seeman Ph.D. 2009, UC Berkeley SCV-PELS April 21, 2010



Outline

- Problem & motivation
- Applications for SC converters
- Switched-capacitor fundamentals
- Power conversion for energyharvesting sensor nodes
- SC converters for microprocessors
- Conclusions



Problem & Motivation

- Inductor-based Converters:
 - Cannot be integrated
 - The inductor is often the largest and most expensive component
 - Causes EMI issues
 - + Efficient at arbitrary conversion ratios
- Switched-capacitor (SC) converters:
 - + Can easily be integrated
 - + No inductors
 - + EMI well controlled
 - Efficient at a single (or a few) conversion ratios



Applications

Existing:



RS-232 Interfaces









Microprocessors



Motor Drive



And more...



Switched-Capacitor Fundamentals

Simple 2:1 converter:



- The flying capacitor C1 shuttles charge from V_{IN} to V_{OUT} .
 - Fixed charge ratio of 2:1
- A voltage sag on the output is necessary to facilitate charge transfer
- Fundamental output impedance:



Switched-Capacitor Losses

Capacitor Losses:

Charge transfer loss:

$$P_{SSL} = I_{OUT}^2 \sum_{caps} \frac{a_{c,i}^2}{C_i f_{sw}}$$

Switch Losses:

Resistive loss:

$$P_{FSL} = 2I_{OUT}^2 \sum_{switches} a_{r,i}^2 R_i$$

Contributes to R_{OUT}, V_{OUT}

Bottom plate loss:

$$P_{CAP} = f_{sw} \sum_{caps} \alpha C_i V_i^2$$

Parasitic loss:

$$P_{SW} = f_{sw} \sum_{switches} C_{GS,i} V_{GS}^2 + C_{DS,i} V_{DS}^2$$



No direct R_{OUT} contribution

[1] Seeman, Sanders, "Analysis and Optimization of Switched-Capacitor Converters," IEEE TPEL, Mar. 2008.

Performance Optimization



Performance Optimization



Comparison vs. Boost



1 V to 3 V Boost: 1A out

1:3 SC Ladder: 6 Switches Top 4: 1 V, 1 A Bottom 2: 1 V, 2 A

1:3 Boost: 2 switches Each: 3 V, 3 A



Comparison vs. Boost



Wireless Sensor Node Converters



- Distributed, inexpensive sensors for a plethora of applications
- Batteries and wires increase cost and liability
- Low-bandwidth and aggressive duty cycling reduces power usage to microwatts
- Miniaturization expands
 application space

Node Structure



Environmental Energy

| Power Source | | | Power [µW/cm ³] | | Notes | |
|--------------------|----------|-----------------------------------|-----------------------------|-------|-------------------------------|---------------------------------------|
| Solar (outside) | | | 15,000 | | (per square cm) | |
| Solar (inside) | | | 30 | | (per square cm) | |
| Temperature | | | 40-5,000 | | (per square cm, 5 K gradient) | |
| Air flow | | | 380 | | (5 m/s, 5% efficiency) | |
| Pressure variation | | | 17 | | | |
| Vibrations | | | 375 | | AC appliances vibrate | |
| | | | | | at multin | ples of 60 Hz! |
| | Vibratio | | n Source | Frequ | uency [Hz] | Peak Acceleration [m/s ²] |
| | | Clothes Dryer | r | | | 3.5 |
| | | Small Microwave Oven | | 121 | | 2.25 |
| | | HVAC vents in offi | 60 | | 0.2-1.5 | |
| | | Wooden Deck (with people walking) | | 385 | | 1.3 |
| | | External Windows | 100 | | 0.7 | |
| FORM | | Refrigerator | 240 | | 0.1 | |

S. Roundy, et. al., "Improving Power Output for Vibrational-Based Energy Scavengers," IEEE Pervasive Computing, Jan-Mar 2005, pp. 28-36.

Energy Harvesters



Voltage

0.6V/cell (outdoors) 0.1V/cell (indoors)

Considerations

Efficiency drops inside due to carrier recombination and spectrum shift

1-100V (macro) 10mV-1V (MEMS) Resonance must be tuned to excitation frequency for maximum output, sensitive to variation

1-3 μV/K / junctionRequires large gradient and
heat output; low output
voltage unless thousands of
junctions used

Ultra-compact Energy Storage



- Commercial LiPoly batteries only get down to ~5mAh; 300mg
- Printed batteries and supercapacitors allow flexible placement and size
- Li-Ion and AgZn batteries under development



Example: PicoCube TPMS

A wireless sensor node for tire pressure sensing:



Synchronous Rectifier



Converter Designs



- Native 0.13µm NMOS devices used for high performance
- 30 MHz switching frequency using ~1nF on-chip capacitors
- Hysteretic feedback used to regulate output voltage by varying converter switching frequency
- Novel gate drive structures used to drive triple-well devices

Seeman, et. al. An ultra-low-power Power Management IC for energy-scavenged Wireless Sensor Nodes. IEEE PESC 2008.

Power Circuitry Performance

Power Conditioning: Power Conversion: Synchronous Rectifier Switched-Cap Converters 0.9 Matched Load $R_1 = R_s$ 0.8 Ideal diode rectifier ($V_D=0$) 0.8 This chip, \leq 1 kHz input Regulated 0.7 This chip, 10 kHz input Output Power [mW] 9.0 0.6 $V_{\rm D}$ = 0.5V diode rectifier Efficiency 0.4 Peak efficiency of 88% (max possible 92%) 0.3 Unregulated 0.2 0.2 0.1 3:2 step-down (0.7V) 1:2 step-up (2.1V) 0.5 1.5 2 2.5 3 3.5 1 4 10⁻³ 10^{-2} 10^{-1} 10° Input Voltage Amplitude [V] Output Power Level [mW] V_{DD} = 1.1 V NiMH; 2.1 k Ω source

SC Converters for Microprocessors



Intel Atom (2008) 45nm, 25mm² 2.5W TDP

April 21, 2010

- Power-scalable on-die switchedcapacitor voltage regulator (SCVR) to supply numerous on-die voltage rails
- Common voltages: 1.05V, 0.8V, 0.65V, 0.3V
 - From a 1.8V input
- Small cells are tiled to provide necessary power for each rail

This work was partially supported by Intel Corp.

Also, see "Le, Seeman, Sanders, Sathe, Naffziger, Alon. A 32nm fully integrated reconfigurable switched-capacitor DC-DC converter delivering 0.55W/mm² at 81% efficiency, ISSCC 2010



SCVR: Topology

For low-voltage rails, add an additional 2:1 at the output

| Switch | 3:2 | 2:1 | 3:1 | S1° S2° |
|--------|-----|-----|-----|-------------|
| S1 | Ф1 | Ф1 | Ф1 | |
| S2 | Ф2 | Ф2 | Ф2 | |
| S3 | Φ1 | Ф1 | | |
| S4 | — | Ф2 | Ф2 | |
| S5 | Φ1 | Φ1 | | \$5° \$6° |
| S6 | — | Ф2 | Ф2 | C2 |
| S7 | Φ1 | Φ1 | Φ1 | - S8 - S7 - |
| S8 | Ф2 | Ф2 | Ф2 | <u>+</u> |
| S9 | Ф2 | | Φ1 | |

 V_{IN}

SCVR: Performance



SCVR: Performance Tradeoffs



Improving SCVR Efficiency

- Improving switch conductance/capacitance
- Improving capacitor technology
 - Higher capacitance density
 - Lower bottom plate capacitance ratio
- Parasitic reduction schemes
 - Charge transfer switches
 - Resonant gate/drain
- Control tricks can help for power backoff



Regulation with SCVRs

- Regulation is critical to maintain output voltage under variation in input and load.
- No inductor allows ultra-fast transient response
 - Given ultra-fast control logic
- Regulation by ratio-changing and R_{OUT} modulation:



Regulation and Efficiency



Example Transient Response



Conclusions

- Switched-capacitor converters exhibit significant advantages over inductor-based converters in many applications
- SC converters can be easily modeled using relatively simple analysis methods
- SC converters and CMOS rectifiers make ideal sensor node power converters
- Modern CMOS technology allows for highpower-density on-chip power conversion

